


Lecture # 5

# ECEN 438/738 Power Electronics

Spring 2025 Semester




**Dr. Prasad Enjeti,**  
Electrical & Computer Engineering  
Texas A&M University  
<http://enjeti.tamu.edu>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

1

## ECEN 438/738 Power Electronics

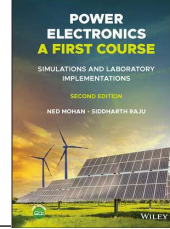

### Power Electronics A First Course: 2<sup>nd</sup> Edition

Free Textbook Online Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

### Chapter 1

#### Power Electronics: An Enabling Technology

Copyright © 2012 by John Wiley & Sons, Inc. All rights reserved.

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

2

## ECEN 438/738 Power Electronics

Free Textbook Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

O'REILLY Explore Skills Start Learning Featured

Power Electronics, A First Course, 2nd Edition

By Ned Mohan, Siddharth Baku



TIME TO COMPLETE: 2h 47m

LEVEL: Beginner

SOURCE: Electrical Engineering

PUBLISHED BY: Wiley

PUBLICATION DATE: January 2023

PRINT LENGTH: 552 pages

[Add to playlist](#)

Power Electronics, A First Course, 2nd Edition

By Ned Mohan, Siddharth Baku

94% of users complete

Approx. 7 hours left

Cover: 92% complete

Title Page: 100% complete

Copyright: 100% complete

Dedication: 100% complete

LIST OF SIMULATION AND HARDWARE IMPLEMENTATION EXAMPLES AND FIGURES: 100% complete

PREPARE: 100% complete

ACKNOWLEDGMENT: 100% complete

ABOUT THE COMPANION WEBSITE: 100% complete

CHAPTER 1 POWER ELECTRONICS: AN ENABLING TECHNOLOGY

**Click Here to Access Book Chapters online and Download**

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

3

## DC - DC Buck Converter → 0 < D < 1

**1**  $V_o = D V_{in}$

**2**  $\Delta I_L = \frac{V_o (1-D) T}{L}$

**3**  $L_{min} = \frac{(1-D) R}{2f}$

**4**  $I_L = I_O = \frac{V_o}{R}$   
 $T = \frac{1}{f}$



**5**  $(\text{Input Power}) V_{in} I_{in} = V_o I_o (\text{Output Power})$   
 $I_{in} = \frac{V_o}{V_{in}} I_o = D \cdot I_o = D I_L$

**Where the duty cycle is 0 < D < 1**

**2** Where  $\Delta I_L$  is inductor current ripple (peak to peak)

Where  $L_{min}$  is the minimum (critical) inductance required to maintain continuous conduction

**6**  $\frac{V_o}{V_{in}} = D$

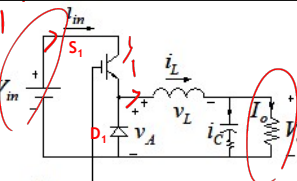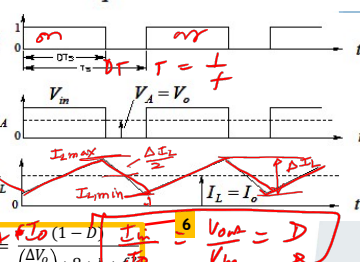Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

4

### DC - DC Buck Converter -Design Example # 2

Input voltage  $V_{in}$  = 7.5V to 36V  
 Output voltage  $V_o$  = 3.3V ; voltage ripple not to exceed 2%  
 Output current  $I_o$  = 0.5A *Full load 100%*  
 Switching Frequency  $f$  = 300kHz

a) Specify the inductor value such that continuous conduction is achieved from 25% load to 100% load  
 b) Find the capacitor value  $C$  that meets the specification.  
 c) Also determine the required  $rms$  current ratings of the MOSFET and the Diode

**Solution: # 1 Input voltage = 7.5V**

$$D = \frac{3.3}{7.5} = 0.44$$

25% load,  $I_o = 0.5 \cdot 5 = 0.125A$

$$\text{Load resistance } R_{25\%} = \frac{3.3}{0.125} = 26.5 \text{ ohms}$$

$$L_{min-\text{at } 25\% \text{ load}} = \frac{(1 - 0.44) \cdot 26.5}{2 \cdot 300,000} = 24.6 \text{ micro-H}$$

**Input voltage = 36V** *Pick the largest L = 40 micro-H*

$$D = \frac{3.3}{36} = 0.0917$$

$$L_{min-\text{at } 25\% \text{ load}} = \frac{(1 - 0.0917) \cdot 26.5}{2 \cdot 300,000} = 40 \text{ micro-H}$$

**Capacitor value:**

$$C = \frac{(1 - D)}{\left(\frac{\Delta V_o}{V_o}\right) \cdot 8 \cdot L \cdot f^2} = 1.58 \text{ micro-f}$$

**rms current ratings:**

MOSFET:  $I_{L,rms} = I_o = 0.5A$   
 Diode:  $I_{D,rms} = \sqrt{1 - D} \cdot I_{L,rms} = \sqrt{1 - 0.0917} \cdot 0.5 = 0.44A$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

5

### DC - DC Buck Converter -Design Example # 2

Input voltage  $V_{in}$  = 7.5V to 36V  
 Output voltage  $V_o$  = 3.3V ; voltage ripple not to exceed 2%  
 Output current  $I_o$  = 0.5A *Full load 100%*  
 Switching Frequency  $f$  = 300kHz

a) Specify the inductor value such that continuous conduction is achieved from 25% load to 100% load  
 b) Find the capacitor value  $C$  that meets the specification.  
 c) Also determine the required  $rms$  current ratings of the MOSFET and the Diode

**Solution: # 1 Input voltage = 7.5V**

$$D = \frac{3.3}{7.5} = 0.44$$

25% load,  $I_o = 0.5 \cdot 5 = 0.125A$

$$\text{Load resistance } R_{25\%} = \frac{3.3}{0.125} = 26.5 \text{ ohms}$$

$$L_{min-\text{at } 25\% \text{ load}} = \frac{(1 - 0.44) \cdot 26.5}{2 \cdot 300,000} = 24.6 \text{ micro-H}$$

**Input voltage = 36V** *Pick the largest L = 40 micro-H*

$$D = \frac{3.3}{36} = 0.0917$$

$$L_{min-\text{at } 25\% \text{ load}} = \frac{(1 - 0.0917) \cdot 26.5}{2 \cdot 300,000} = 40 \text{ micro-H}$$

**Capacitor value:**

$$C = \frac{(1 - D)}{\left(\frac{\Delta V_o}{V_o}\right) \cdot 8 \cdot L \cdot f^2} = 1.58 \text{ micro-f}$$

**rms current ratings:**

MOSFET:  $I_{L,rms} = I_o = 0.5A$   
 Diode:  $I_{D,rms} = \sqrt{1 - D} \cdot I_{L,rms} = \sqrt{1 - 0.0917} \cdot 0.5 = 0.44A$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

6

### DC - DC Buck Converter

Input voltage  $V_{in}$  = 19V  
 Output voltage  $V_o$  = 1.1V; voltage ripple not to exceed 2%  
 Output current  $I_o$  = 50A  
 Switching Frequency  $f$  = 500kHz

**Let us only consider diode conduction losses**

Silicon diode = 0.7 V forward drop  
 Conduction loss =  $0.7 \cdot 50 \cdot (1 - D) = 33 \text{ watts}$   
 Output power  $P_o = 1.1 \cdot 50 = 55 \text{ watts}$   
 Efficiency =  $55 / (55 + 33) = 62.5\%$

Schottky diode = 0.2 V forward drop  
 Conduction loss =  $0.2 \cdot 50 \cdot (1 - D) = 9.42 \text{ watts}$   
 Efficiency =  $55 / (55 + 9.42) = 85.4\%$

What we need is the efficiency to be in 90% range. How can we achieve this?

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

7

### DC - DC Buck Converter

Input voltage  $V_{in}$  = 19V  
 Output voltage  $V_o$  = 1.1V; voltage ripple not to exceed 2%  
 Output current  $I_o$  = 50A  
 Switching Frequency  $f$  = 500kHz

**Let us only consider diode conduction losses**

Silicon diode = 0.7 V forward drop  
 Conduction loss =  $0.7 \cdot 50 \cdot (1 - D) = 33 \text{ watts}$   
 Output power  $P_o = 1.1 \cdot 50 = 55 \text{ watts}$   
 Efficiency =  $55 / (55 + 33) = 62.5\%$



Schottky diode = 0.2 V forward drop  
 Conduction loss =  $0.2 \cdot 50 \cdot (1 - D) = 9.42 \text{ watts}$   
 Efficiency =  $55 / (55 + 9.42) = 85.4\%$

What we need is the efficiency to be in 90% range. How can we achieve this?

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

8
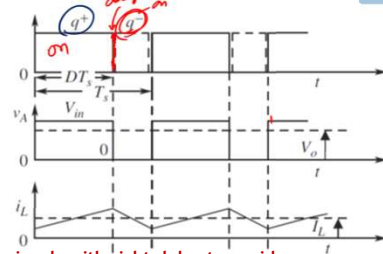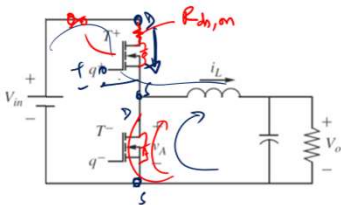
## DC - DC Buck Converter - Synchronous Rectifier for Low output voltage and higher efficiency



- Diode is replaced by a MOSFET
- The MOSFETs are driven by complementary gating signals with slight delay to avoid shoot through
- When the upper MOSFET is off, the inductor current flows through the channel, from the source to the drain, of the lower MOSFET
- This configuration is suitable for low output voltages - say 1V and also yields higher efficiency

Reverse conduction of GaN MOSFETs <https://www.youtube.com/watch?v=QNHzaWCUEf>

Gan System FAQ: <https://gansystems.com/gan-transistors/faq/#toggle-id-39>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

9


## DC - DC Buck Converter - Synchronous Rectifier for Low output voltage and higher efficiency

Input voltage  $V_{in}$  = 19V  
Output voltage  $V_o$  = 1.1V ; voltage ripple not to exceed 2%  
Output current  $I_o$  = 50A  
Switching Frequency  $f$  = 500kHz

$$\text{Conduction Loss} = I_L^2 * R_{DS(on)} = 50^2 + 1.45 * 10^{-3} = 3.625 \text{ watts}$$

$$\text{Efficiency} \sim \frac{55}{55 + 3.625} * 100 = 93.8\%$$

Now we are in the ball park of 90% efficiency once we add switching losses, losses in the inductor/capacitor etc.

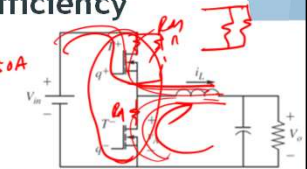

EPC2035 - Enhancement Mode Power Transistor

$V_{DS}$ , 30 V	$R_{DS(on)}$ , 1.45 mΩ
$I_D$ , 50 A	Pulsed $I_D$ , 590 A
$T_J$ , 150°C	RoHS 6/6, Halogen Free

- Applications:
- DC-DC Converters
  - Motor Drive
  - Industrial Automation
  - Synchronous Rectification
  - Inverter Pre-drivers
  - Broad-band SWP / Converters
- Benefits:
- Higher Switching Frequency - Lower switching losses and lower drive power
  - Higher Efficiency - Lower conduction and switching losses, lower thermal recovery losses
  - Smaller Footprint - Higher power density
  - Lower  $R_{DS(on)}$  - Higher current operation

<https://epc-co.com/epc/Products/eGaNfETsandCs/EPC2035.aspx>


Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

11

## DC - DC Buck Converter -Design Example # 3

Input voltage  $V_{in}$  = 35V  
Output voltage  $V_o$  = 5V ; voltage ripple not to exceed 2%  
Output current  $I_o$  = 1A  
Switching Frequency  $f$  = 500kHz

- Specify the inductor value such that the peak-to-peak variation in inductor current  $\Delta I_L$  does not exceed 40% of the average value ( $I_L$ ).
- Find the capacitor value  $C$  that meets the specification.
- Also determine the required rms current rating of the inductor and the capacitor.

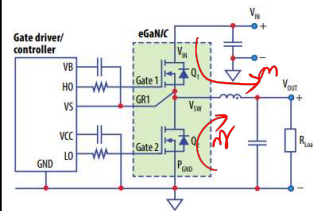

EPC2035 - Enhancement Mode Power Transistor

$V_{DS}$ , 60 V	$R_{DS(on)}$ , 45 mΩ
$I_D$ , 1.7 A	Pulsed $I_D$ , 24 A
RoHS 6/6, Halogen Free	

- Applications:
- DC-DC Converters
  - Wireless Power Transfer
  - LED/High Power Applications
- Benefits:
- Higher Switching Frequency - Lower switching losses and lower drive power
  - Higher Efficiency - Lower conduction and switching losses, lower thermal recovery losses
  - Smaller Footprint - Higher power density

<https://epc-co.com/epc/Products/eGaNfETsandCs/EPC2035.aspx>

$$\text{Conduction loss} = I^2 * R_{DS(on)} = 1 * 1 * 0.045 = 45mW$$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu


12

12
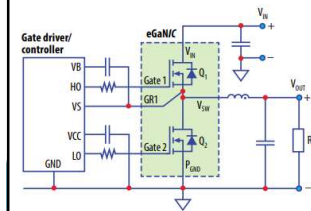
## DC - DC Buck Converter -Design Example # 3

Input voltage  $V_{in}$  = 35V  
Output voltage  $V_o$  = 5V ; voltage ripple not to exceed 2%  
Output current  $I_o$  = 1A  
Switching Frequency  $f$  = 500kHz

- Specify the inductor value such that the peak-to-peak variation in inductor current  $\Delta I_L$  does not exceed 40% of the average value ( $I_L$ ).
- Find the capacitor value  $C$  that meets the specification.
- Also determine the required rms current rating of the inductor and the capacitor.



From the data sheet

$$t_r = 1.3 \text{ ns}$$

$$t_f = 1.8 \text{ ns}$$

Switching Losses:

$$P_{sw} = \frac{1}{2} V_{in} I_o (t_{c,on} + t_{c,off}) f_s$$

$$t_{c,on} = t_{r1} + t_{f1} = 1.3 + 1.8 = 3.1 \text{ ns}$$

$$t_{c,off} = t_{r2} + t_{f2} = 1.3 + 1.8 = 3.1 \text{ ns}$$

$$P_{sw} = \frac{1}{2} V_{in} I_o (t_{c,on} + t_{c,off}) f_s = 0.5 * 35 * 1 * 6.2 \text{ ns} * 500 \text{ kHz} = 54.25 \text{ mW}$$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

13

13

### DC - DC Buck Converter -Design Example # 3

Input voltage  $V_{in} = 35V$   
 Output voltage  $V_o = 5V$ ; voltage ripple not to exceed 2%  
 Output current  $I_o = 1A$   
 Switching Frequency  $f = 500kHz$

a) Specify the inductor value such that the peak-to-peak variation in inductor current  $\Delta I_L$  does not exceed 40% of the average value ( $I_L$ ).  
 b) Find the capacitor value  $C$  that meets the specification.  
 c) Also determine the required *rms* current rating of the inductor and the capacitor.

**Switching Losses**  $= 0.5 * 35 * 1 * 6.2ns * 500kHz = 54.25 mW$   
**Conduction loss**  $= I^2 * R_{DS(on)} = 1 * 1 * 0.045 = 45mW$

$\eta = \frac{P_{out}}{P_{in}} = \frac{5 * 1}{5 + 0.09925} * 100 = 98.05\%$   
 Compared to 14.3% efficiency with linear regulator

**Gate driver/controller**

**eGaNiC**

**V<sub>DS</sub>, 60 V**  
**R<sub>DS(on)</sub>, 45 mΩ**  
**I<sub>D</sub>, 1.7 A**  
**Pulsed I<sub>D</sub>, 24 A**  
**RoHS 6/6, Halogen Free**

**Applications**

- DC-DC Converters
- Wireless Power Transfer
- LED/High Power Applications

**Benefits**

- Higher Switching Frequency - Linear switching
- Higher Efficiency - Linear conduction and switching
- Smaller Footprint - Higher power density

<https://epc-co.com/epc/Products/eGaNiCandCs/EPC2035.aspx>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

14

### Linear Regulator

#### Dissipative realization

Series pass regulator: transistor operates in active region

**Linear amplifier and base driver**  
 $P_{loss} = 45W$

$V_{in} = 35V$   
 $I = 1.5A$   
 $R = 3.3\Omega$   
 $V_{out} = 5V$   
 $P_{out} = 7.5W$   
 $P_{in} \sim 52.5W$

$\eta = \frac{P_{out}}{P_{in}} = \frac{7.5}{52.5} * 100 = 14.3\%$

**L 7805 - \$0.77 - Qty = 1 or \$0.34 - Qty = 1000**

Input voltage (max) = 35 V  
 Output voltage (fixed) = 5 V  
 Output current (max) = 1.5 A

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

15

### Suggested Problems - for you to solve

#### DC - DC Buck Converter -Problems in the book

1. Problem 3.6, Assume a switching frequency  $f = 400kHz$
2. Problem 3.7

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

16

### DC - DC Buck Converter Effect of Inductor Resistance $r_L$

**Inductor Quality factor :  $Q = \frac{V_o}{r_L I_o}$**

**Inductor Vol-second-balance**  
 $(V_{in} - V_o - i_L * r_L) * D + (-V_o - i_L * r_L) * (1-D) = 0$   
 Solve the above equation to obtain  $V_o$

$V_o = \frac{V_{in} * D}{1 + \frac{r_L}{R}}$

**Efficiency  $\eta = \frac{V_o * I_o}{V_{in} * I_o + I_o^2 * r_L}$  since  $I_L = I_o$  we have**  
 Simplify the above equation to obtain  $\eta$

$\eta = \frac{1}{1 + \frac{r_L}{R}}$


$\frac{r_L}{R}$	$\frac{V_o}{V_{in}}$	$\eta$
0.01	0.99D	99%
0.1	0.91D	90.9%

Repeat the analysis if MOSFET on-resistance and diode forward drop need to be considered

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

17



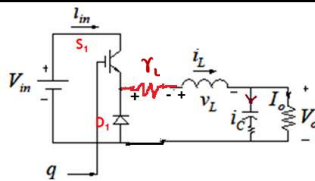


## ECEN 738 Section Course Project

**DC – DC Buck Converter Analysis - effect of inductor resistance  $r_L$ ; Mosfet  $R_{ds(on)}$ ; capacitor ESR on converter performance – steady state and transient – design a feedback loop**

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

19

## DC - DC Buck Converter - Interleaving

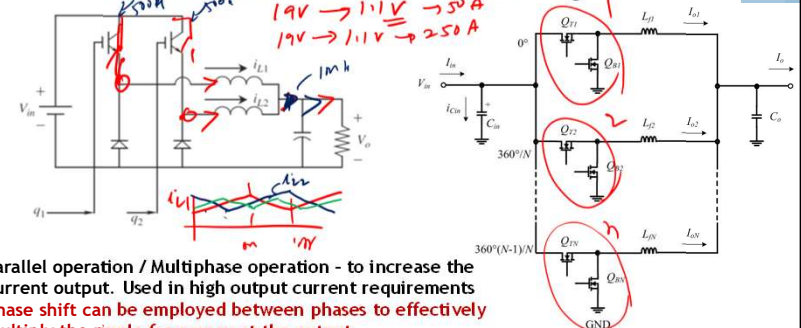

- Parallel operation / Multiphase operation - to increase the current output. Used in high output current requirements
- Phase shift can be employed between phases to effectively multiply the ripple frequency at the output
- Also power dissipation is spread to multiple phases over a wider area
- Offers improved reliability and redundancy against failures

\* Possible course project for 738-section  
 TI-article: Benefits of a multiphase buck converter  
 & <https://www.eetimes.com/benefits-of-multiphase-buck-converters-part-1/>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

20

## Multiphase Buck Converter - link

Course Project for ECEN 738 section - design a 6 phase converter & simulate its performance

### 2 Multiphase Buck Regulator Overview

A multiphase buck regulator is a parallel set of buck power stages as shown in Figure 2-1 and Figure 2-2, each with its own inductor and set of power MOSFETs. Collectively, these components are called a phase. These phases are connected in parallel and share both input and output capacitors. During steady-state operation, individual phases are active at spaced intervals equal to  $360^\circ / n$  throughout the switching period where  $n$  is the total number of phases. Figure 2-2 shows a TPS53679 multiphase controller demonstration board and TI power stages for a six-phase design.

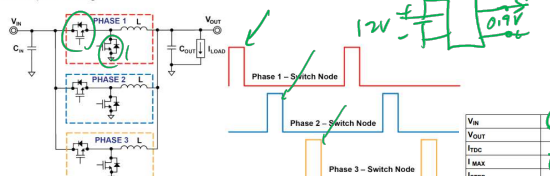


Figure 2-1. Multiphase Regulator Example

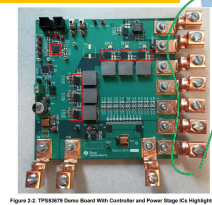


Figure 2-2. TPS53679 Demo Board With Controller and Power Stage ICS Highlighted


Table 5-1. Multiphase Design Targets

$V_{in}$	12 V	Input Voltage
$V_{out}$	0.9 V	Nominal Output Voltage
$I_{TPC}$	200 A	Thermal Design Current
$I_{max}$	240 A	Max Current
$I_{step}$	150 A	Max Load Step
DCLL	0.5 mΩ	DC Load Line
$\Delta V_{OUT(BC)}$	±1%	$V_{OUT}$ DC Ripple
$\Delta V_{OUT(MD)}$	±5%	$V_{OUT}$ Transient Specifications
$\Delta V_{RIPPLE}$	240 mVpp	$V_{IN}$ DC Ripple
$\Delta V_{OVS}$	±360 mV	$V_{IN}$ Overshoot and Undershoot
PMBus with Telemetry	Yes	Requires PMBus interface with $V_{IN}$ , $I_{IN}$ , $V_{OUT}$ , $I_{OUT}$ , and Temp readings

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

21

## DC - DC Buck Converter - Interleaving

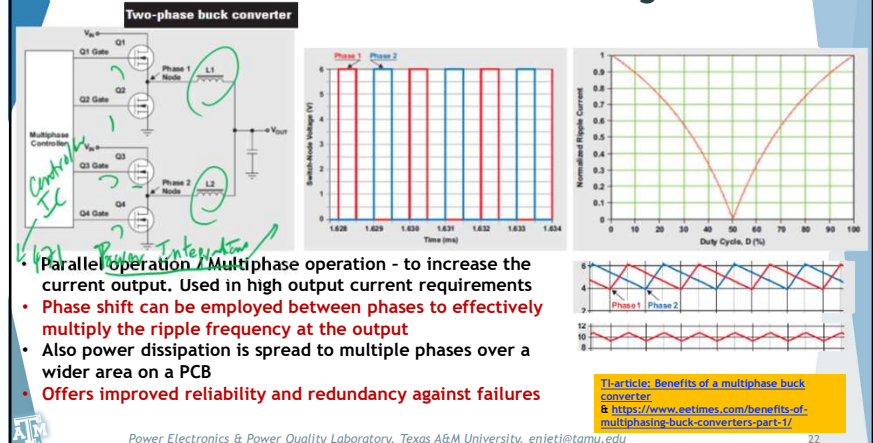

- Parallel operation / Multiphase operation - to increase the current output. Used in high output current requirements
- Phase shift can be employed between phases to effectively multiply the ripple frequency at the output
- Also power dissipation is spread to multiple phases over a wider area on a PCB
- Offers improved reliability and redundancy against failures



TI-article: Benefits of a multiphase buck converter  
 & <https://www.eetimes.com/benefits-of-multiphase-buck-converters-part-1/>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

22
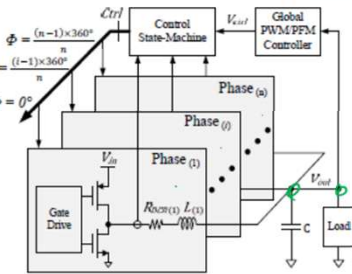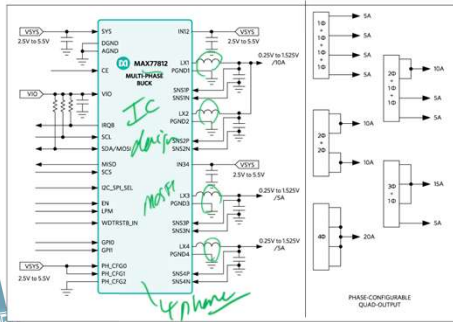
## DC - DC Buck Converter - Interleaving - multiphase

- Each phase is driven by gate drive signals of the same switching frequency  $f_s$  but adjacent phases are phase shift by  $360^\circ/n$ .
- For example, a three-phase converter is driven by gate signals at 0, 120, and 240 degrees.



The MAX77812 is a quad-phase high-efficiency stepdown (buck) converter capable of delivering up to 20A of maximum current

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

23

23

## Additional Design Problems for you to solve

### DC - DC Buck Converter -Problems in the book

#### 1. Problem 3.4

- 3.4. Calculate the critical value of the inductance  $L$  such that this Buck converter remains in the continuous conduction mode at and above  $P_o = 5 \text{ W}$  under all values of the input voltage  $V_{in}$  in a range from 24 V to 50 V. Assume  $V_o = 15 \text{ V}$  and  $f = 400 \text{ kHz}$

Answer: 39.4  $\mu\text{H}$

#### 2. Problem 3.7

- 3.7. A Buck dc-dc converter is to be designed for  $V_{in} = 20 \text{ V}$ ,  $V_o = 12 \text{ V}$ , and the maximum output power  $P_o = 72 \text{ W}$ . The switching frequency is selected to be  $f_s = 400 \text{ kHz}$ . Assume ideal components. Estimate the value of the filter inductance that should be used if the converter is to remain in CCM at one-third the maximum output power.

Answer: 3  $\mu\text{H}$

#### 3. Problem

- For the Buck dc-dc converter in problem 3.4 above, if the resistance of the inductor  $r_L = 2.25 \text{ ohms}$ , calculate the required duty cycle  $D$  for  $V_{in} = 24 \text{ V}$  and  $50 \text{ V}$ . Also calculate the efficiency

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

24

24