

- a) Supply Voltage - $\pm 15V$
- b) Power Consumption - $1mV$
- c) Voltage Gain - $200k$
- d) Power Consumption - $2mW$
- e) Output resistance - 75Ω
- f) Bandwidth - about $1MHz$
- g) Input resistance - $0.3M\Omega$ at 25 celsius
- h) Input offset current - $2nA$
- i) Slew rate - $0.5-V/\mu s$



JOAQUIN SALAS 73100014

2. Voltage Gains for. $\frac{V_{o1}}{V_i}$, $\frac{V_{o2}}{V_i}$, $\frac{V_{o3}}{V_i}$

$$(a) \frac{(0 - V_i)}{R_1} = \frac{0 - V_{o1}}{R_2}$$

$$\rightarrow \frac{V_i}{R_1} = -\frac{V_{o1}}{R_2}$$

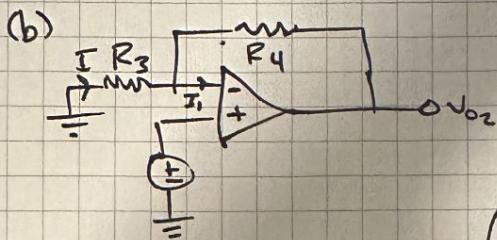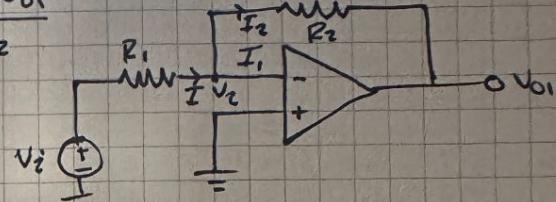
$$\boxed{\frac{V_{o1}}{V_i} = -\frac{R_2}{R_1}}$$



$$\frac{0 - V_i}{R_3} = \frac{V_i - 0}{R_4}$$

$$-V_i \left[\frac{1}{R_3} + \frac{1}{R_4} \right] = -\frac{V_{o2}}{R_4}$$
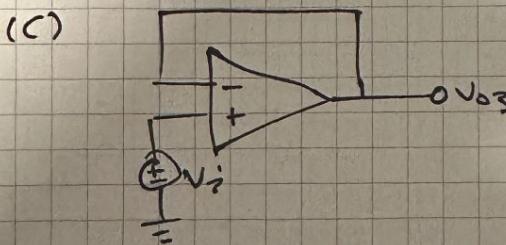
$$\left(\frac{R_3 + R_4}{R_3} \right) = \frac{V_{o2}}{V_i} \Rightarrow \boxed{\frac{V_{o2}}{V_i} = 1 + \frac{R_4}{R_3}}$$



$$\Rightarrow V_{o3} = V_i = V_o$$

$$\boxed{\frac{V_{o3}}{V_i} = 1}$$

3. If $R_1 = R_3 = 10k\Omega$, find R_2 and R_4 . $\frac{V_{o1}}{V_i} = -3$ and $\frac{V_{o2}}{V_i} = 6$

$$(a) R_1 = 10k\Omega \quad \frac{V_{o1}}{V_i} = -3$$

$$-3 = \frac{-R_2}{10k}$$


$$\Rightarrow \boxed{R_2 = 30k\Omega}$$

$$(b) R_3 = 10k\Omega \quad \frac{V_{o2}}{V_i} = 6$$


$$6 = 1 + \frac{R_4}{10k} \Rightarrow \boxed{R_4 = 50k\Omega}$$

Simulations:


Inverting Op-Amp Bode Plot

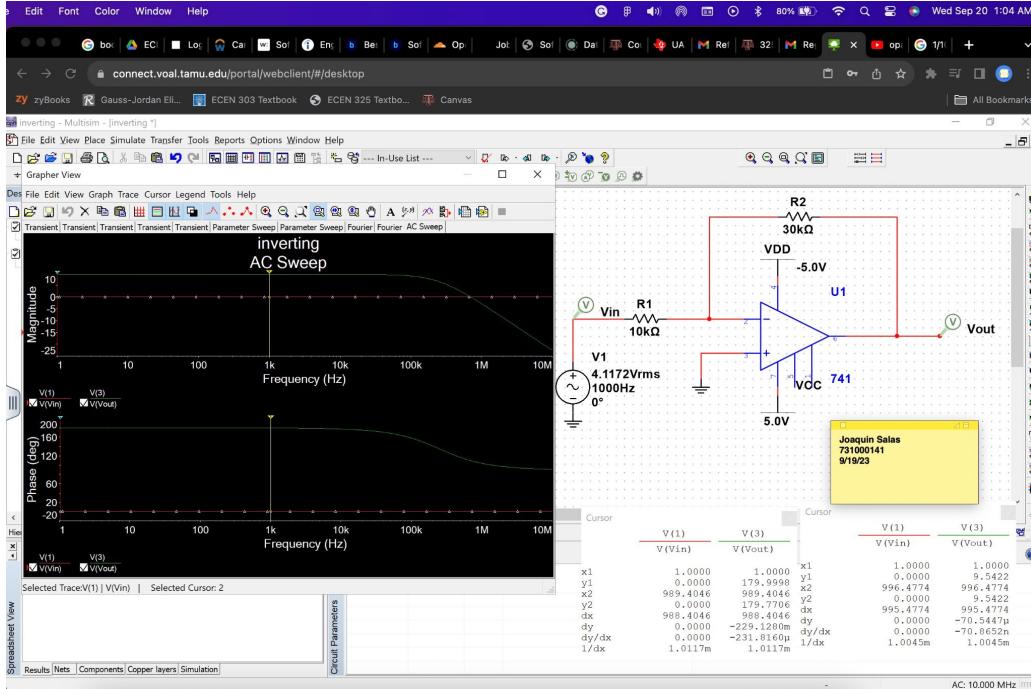


Inverting Op-Amp Transient Analysis

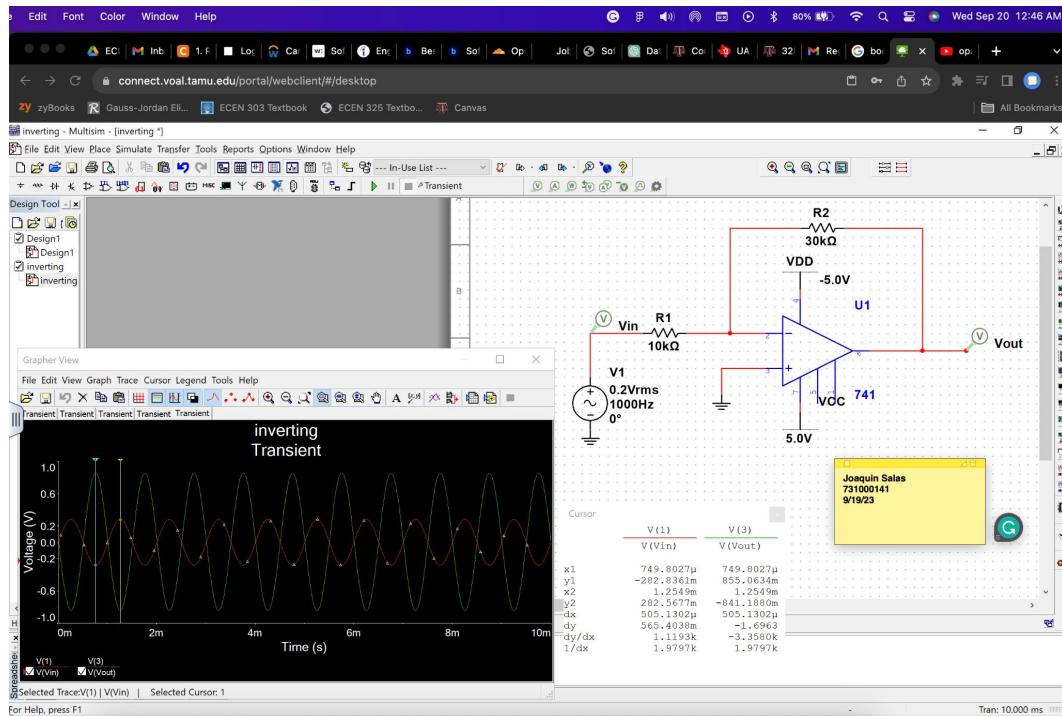


Inverting Op-Amp Parameter Sweep

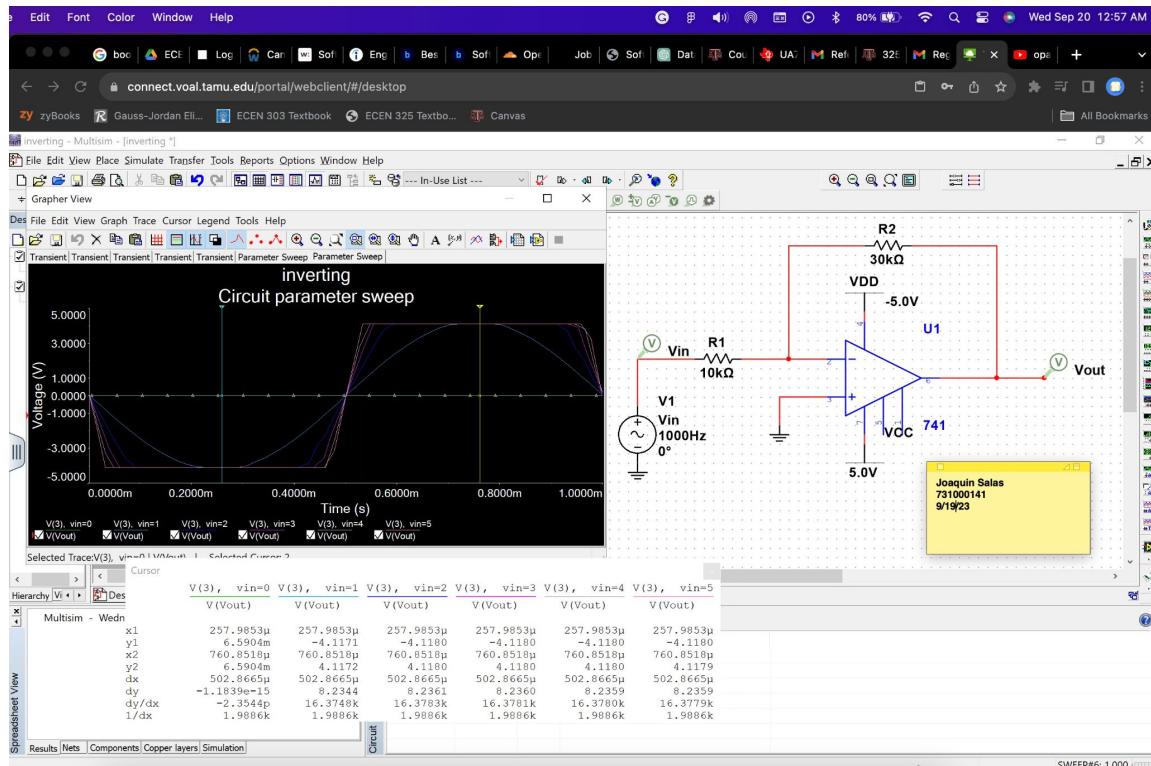


Inverting Op-Amp Fourier Analysis

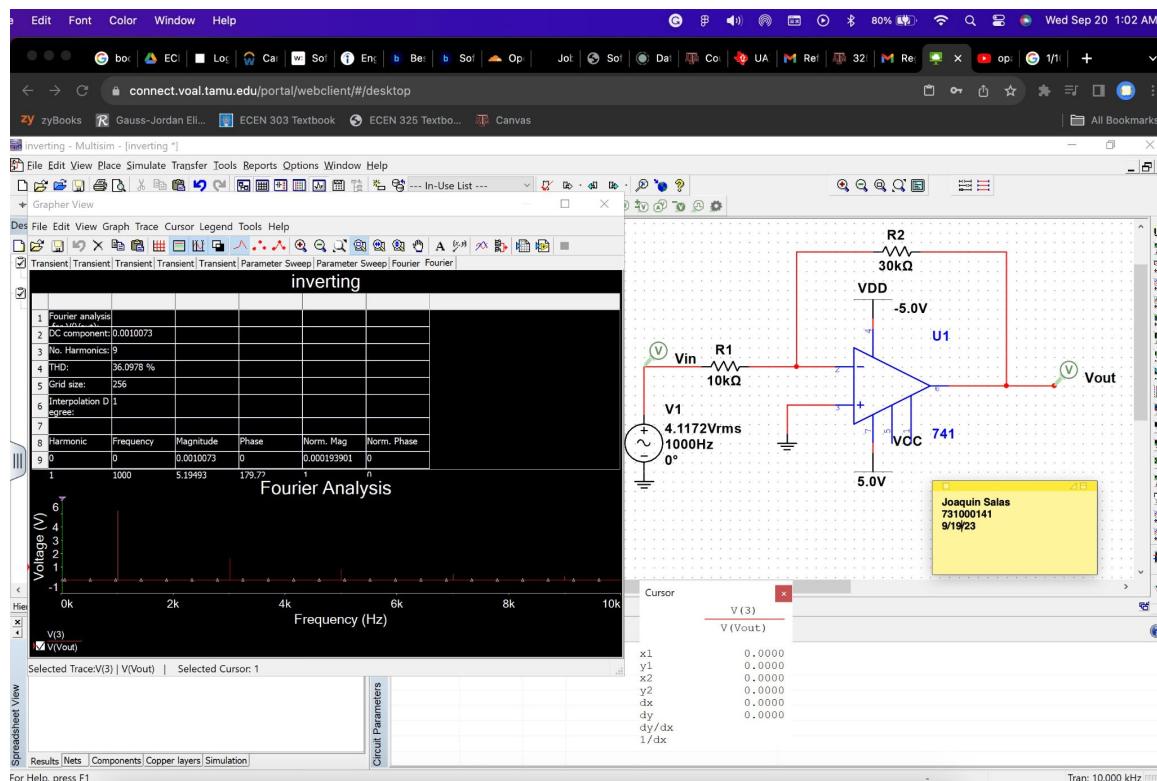


Non-Inverting Op-Amp Bode Plot

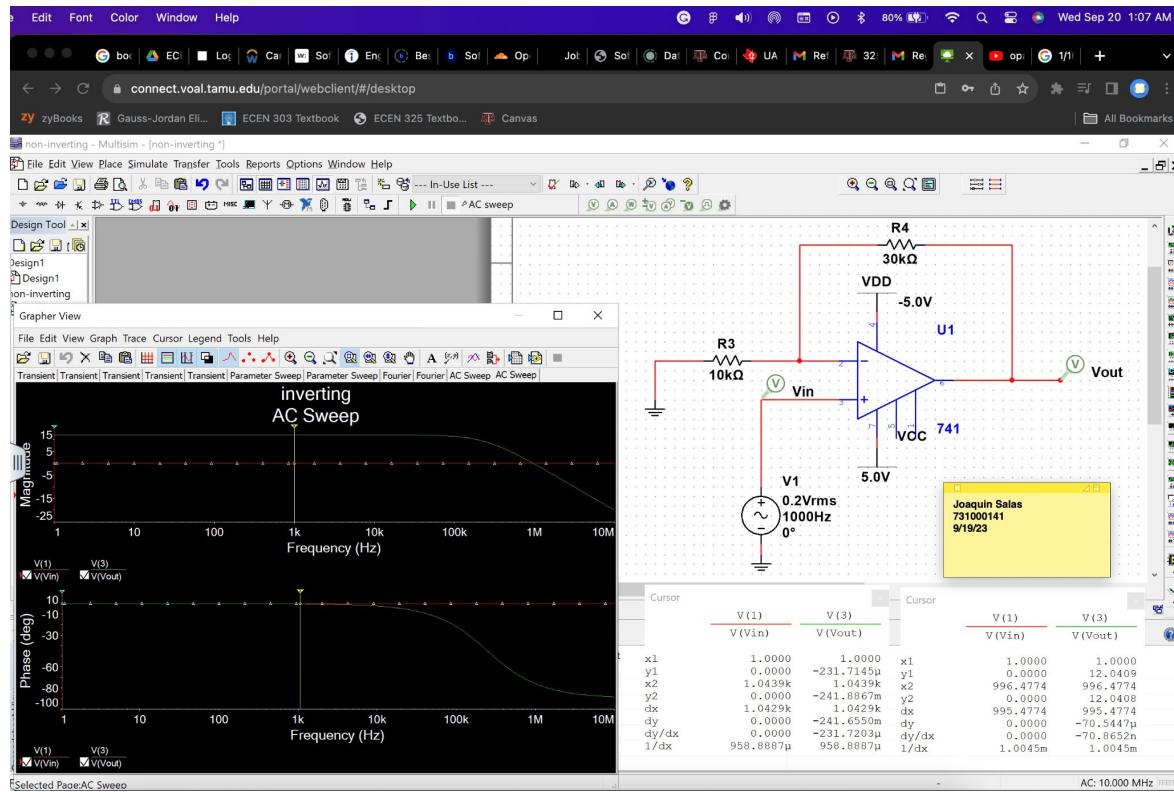


Non-Inverting Op-Amp Transient Analysis

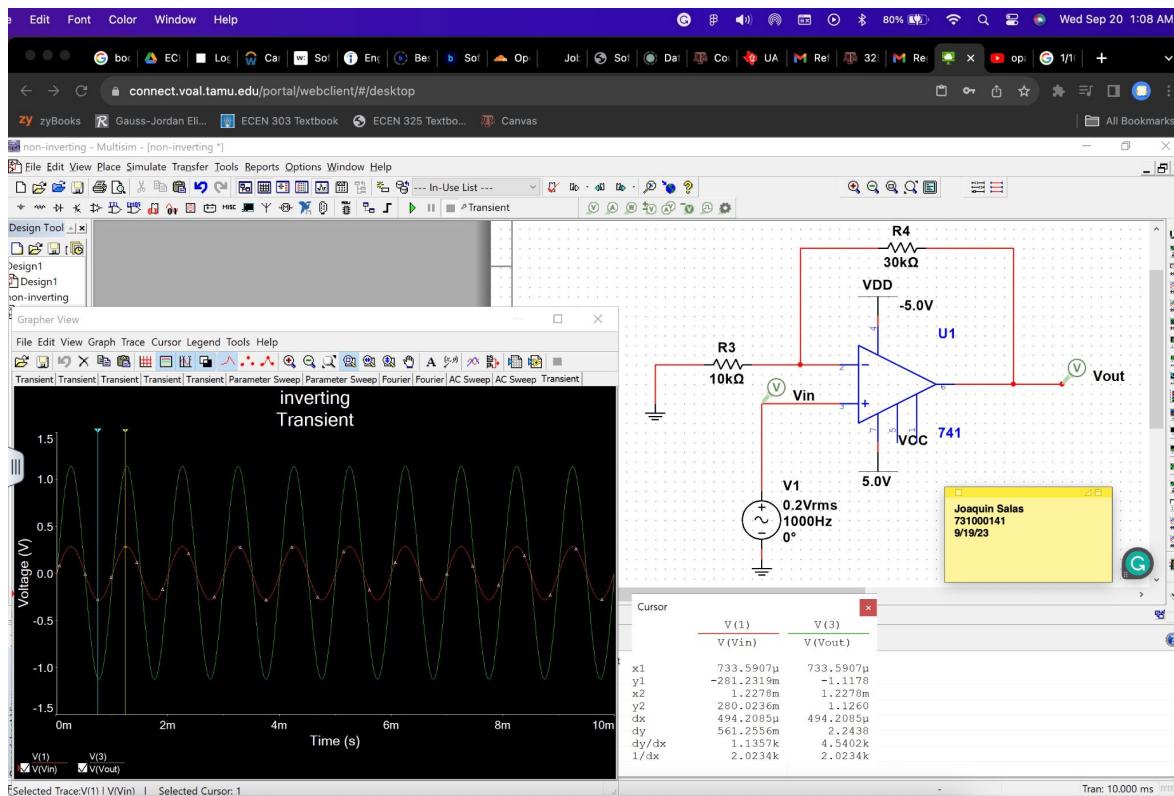


Non-Inverting Op-Amp Parameter Sweep

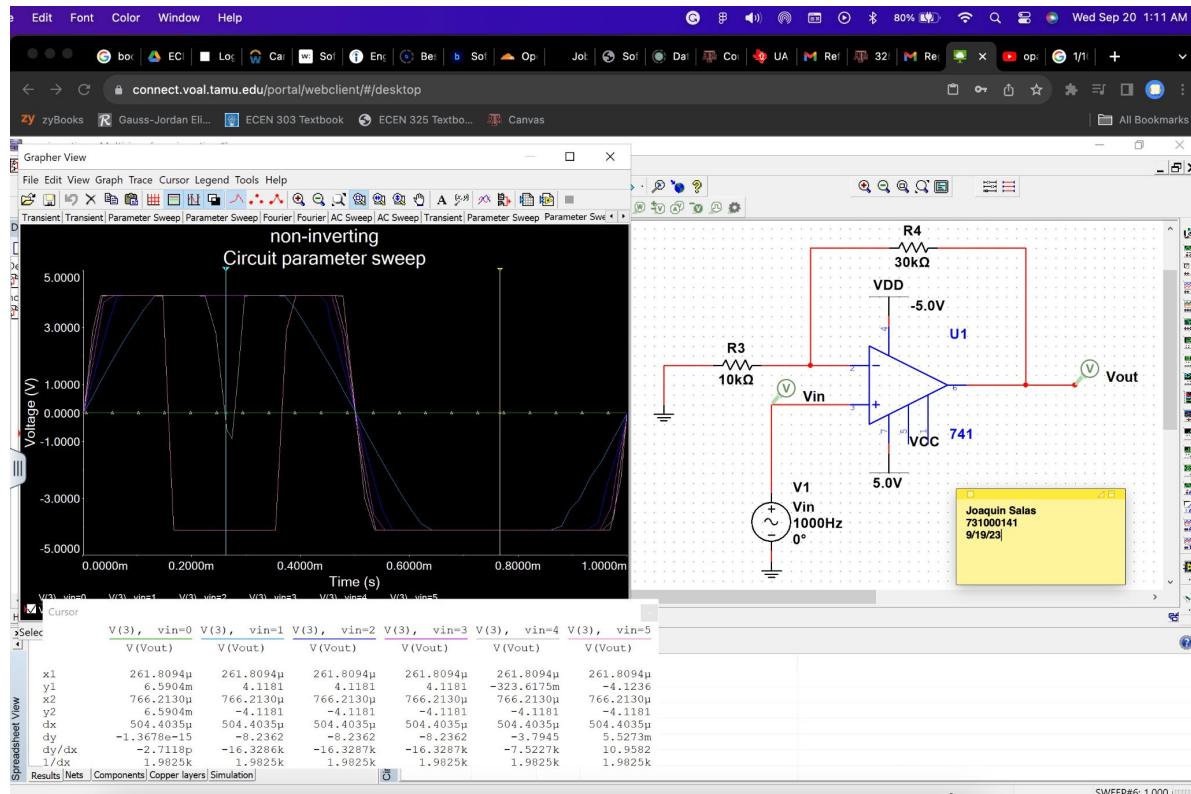


Non-Inverting Op-Amp Fourier Analysis

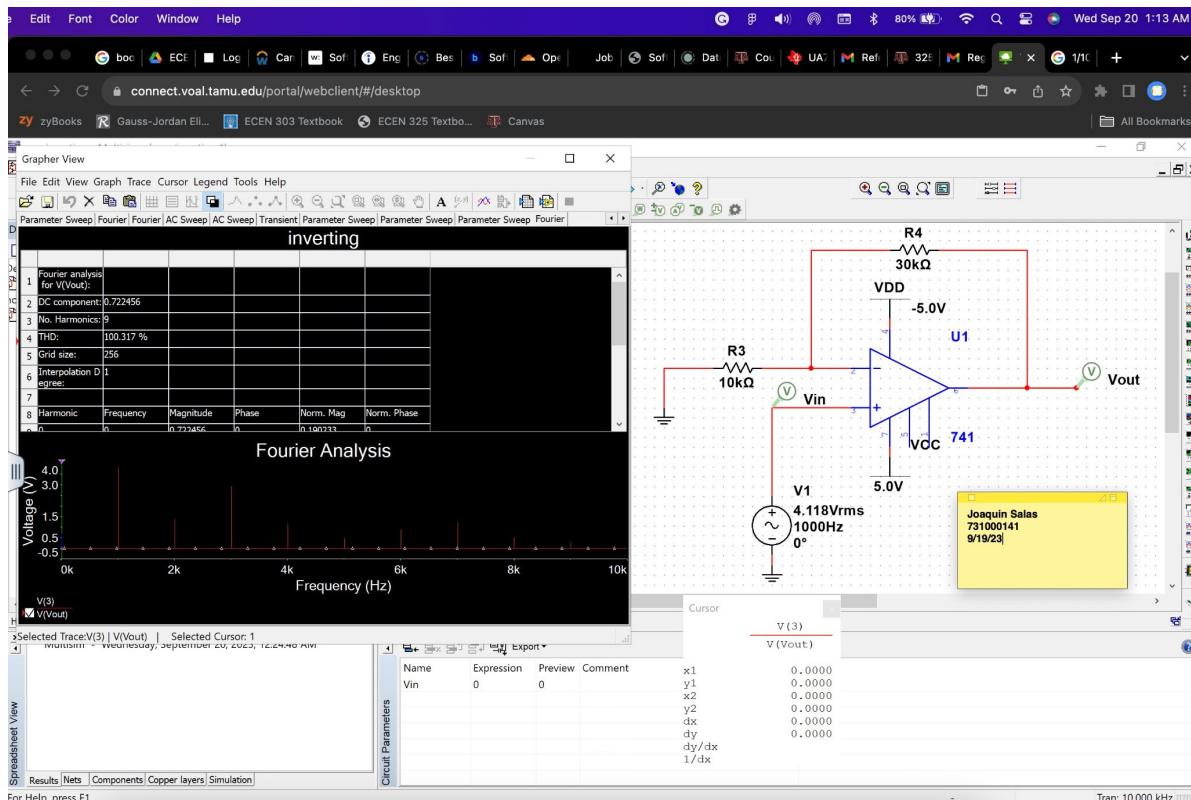


Voltage Follower Op-Amp Bode Plot

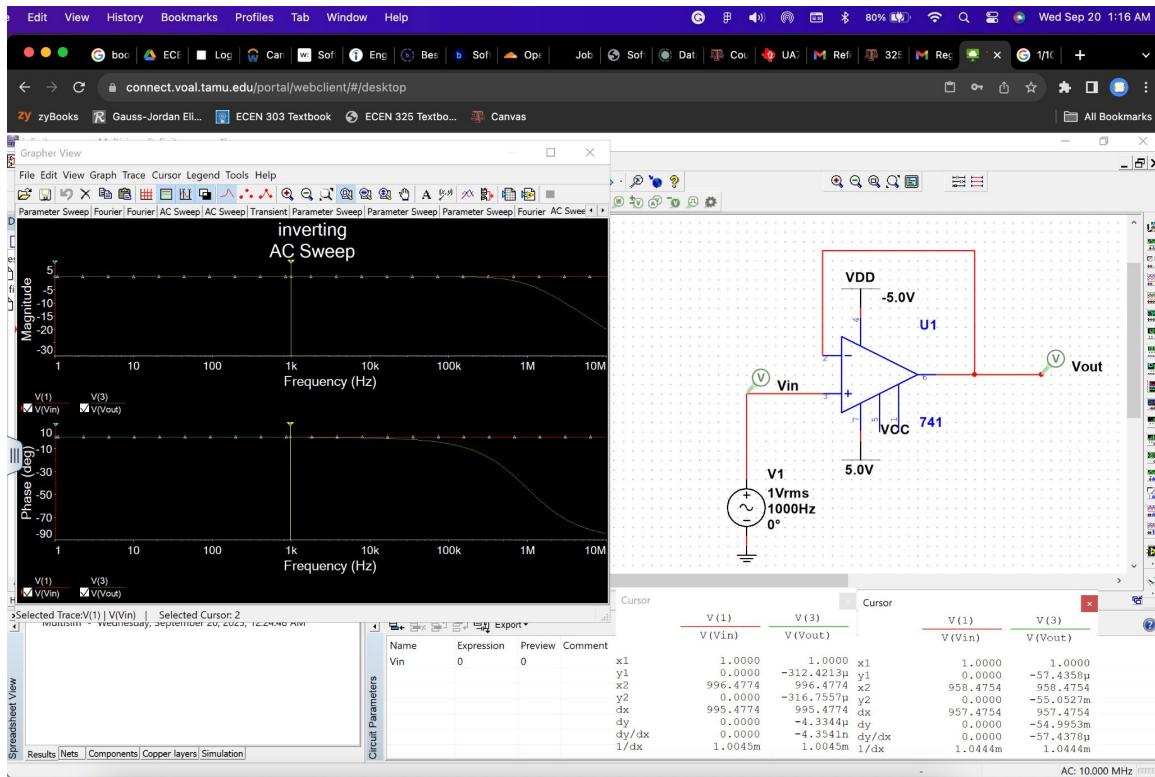

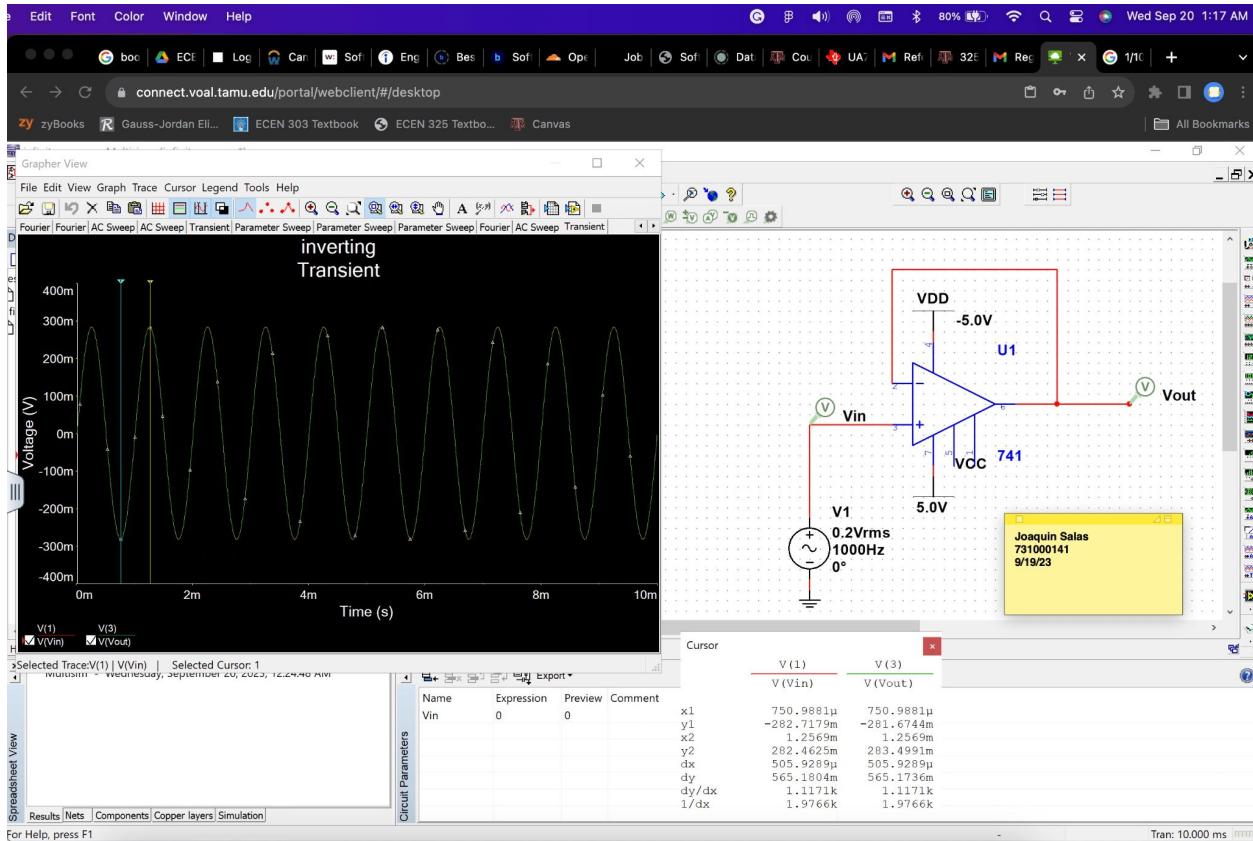Voltage Follower Op-Amp Transient Analysis



Voltage Follower Op-Amp Parameter Sweep

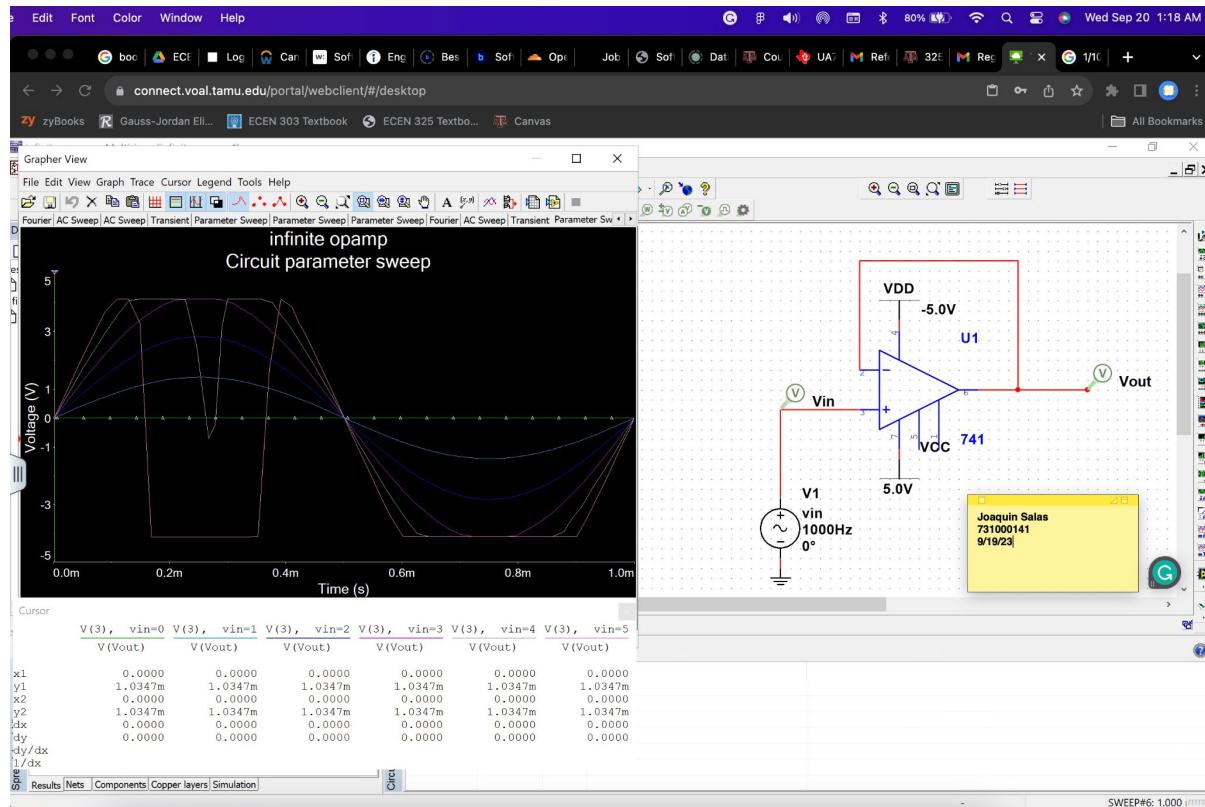

Voltage Follower Op-Amp Fourier Analysis

