


Lecture # 8

ECEN 438/738 Power Electronics

Spring 2025 Semester




Dr. Prasad Enjeti,
Electrical & Computer Engineering
Texas A&M University
<http://enjeti.tamu.edu>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

1

ECEN 438/738 Power Electronics

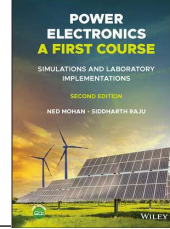

Power Electronics A First Course: 2nd Edition

Free Textbook Online Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

Chapter 5 RECTIFICATION OF UTILITY INPUT USING DIODE RECTIFIERS

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

2

ECEN 438/738 Power Electronics

Free Textbook Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

POWER ELECTRONICS, A FIRST COURSE
SIMULATIONS AND LABORATORY IMPLEMENTATIONS
SECOND EDITION
NED MOHAN, SIDHARTH RAOJI

TIME TO COMPLETE: 9h 07m
LEVEL: Beginner
COURSE: Electrical Engineering
PUBLISHED BY: Wiley
PUBLICATION DATE: January 2023
PAGES: 322 pages
+ Add to playlist

Power Electronics, A First Course, 2nd Edition
by Ned Mohan, Siddharth Raju

94% stress complete Approx. 7 hours left

Cover: 92% complete
Title Page: 100% complete
Copyright: 100% complete
Dedication: 100% complete
LIST OF SIMULATION AND HARDWARE IMPLEMENTATION EXAMPLES AND FIGURES: 100% complete
PREFACE: 100% complete
ACKNOWLEDGMENT: 100% complete
ABOUT THE COMPANION WEBSITE: 100% complete
CHAPTER 1 POWER ELECTRONICS: AN ENABLING TECHNOLOGY

Click Here to Access Book Chapters online and Download

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

3

DC-DC Buck Converter - DC-DC Boost Converter

Buck Converter

$V_o = D V_m$ 1

$\Delta I_L = \frac{V_o (1-D) T}{L}$ 2

$L_{min} = \frac{(1-D) R}{2f}$ 3

$I_L = I_o = \frac{V_o}{R}$ 4

$T = \frac{1}{f}$ 5

(Input Power) $V_m I_m = V_o I_o$ (output)
 $I_m = \frac{V_m}{V_o} I_o = D \cdot I_o = D I_L$

$C = \frac{(1-D)}{\left(\frac{\Delta V_o}{V_o}\right) * 8 * L * f^2}$ 6

$V_o = \frac{V_{in} * D}{1 + \frac{r_L}{R}}$

$\eta = \frac{1}{1 + \frac{r_L}{R}}$

Boost Converter

$V_o = \frac{V_{in}}{1-D}$

$\Delta I_L = \frac{V_{in} * DT}{L}; L = \frac{V_{in} * DT}{\Delta I_L} = \frac{V_{in} * D}{f * \Delta I_L}$

$L_{min} = \frac{D * (1-D)^2 * R}{2 * f}$

$V_{in} * I_L = V_o * I_o$

$I_{Diode} = I_o = \frac{V_o}{R}$

$I_{switch} = I_L * D$

$C = \frac{I_o * DT}{\Delta V_o} = \frac{D}{R * \left(\frac{\Delta V_o}{V_o}\right) * f}$

$\frac{V_o}{V_{in}} = \left(\frac{1}{1-D}\right) * \left(\frac{1}{1 + \frac{r_L}{R(1-D)^2}}\right)$

$\eta = \frac{1}{1 + \frac{r_L}{R(1-D)^2}}$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

4

Question 2 10 pts

In the DC-DC buck converter shown in the figure, the input voltage V_{in} is varying from 6 V to 24 V. The output voltage V_o is regulated to 5 V. The power output P_o is also variable and is in the range 27 watts to 52 watts. The switching frequency is 342 kHz. The inductor resistance $r_L = 0.16 \text{ m}\Omega$. Calculate the required minimum duty cycle to regulate the output voltage at 5 V?

(Assume: continuous conduction mode of operation)

Handwritten notes:

- $D_{min} ?$
- $D_{min} = \left(\frac{V_o}{V_{in}} \right) \left(1 + \frac{r_L}{R} \right)$
- $D_{min} = \frac{5}{24} \left(1 + \frac{0.16}{R_{avg}} \right)$
- $P_o = \frac{V_o^2}{R} \Rightarrow R = \frac{V_o^2}{P_o}$
- $R_{avg} = \frac{5^2}{27}$
- $\frac{V_o}{V_{in}} = \frac{D}{1 + \frac{r_L}{R}}$
- $L = 21 \mu H$
- $L_{min} = \frac{(1-D)R}{2f}$
- $6V \text{ to } 24V$
- $0.16m\Omega$
- $27W \leq P_o \leq 52W$
- $V_o = 5V$

Fig. DC-DC Buck Converter

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

5

Complex Power - ECEN 340

$v(t) = V_p \cos(\omega t + \theta_V)$
 $i(t) = I_p \cos(\omega t + \theta_I)$

Since $V_{RMS} = \frac{V_p}{\sqrt{2}}$
 $I_{RMS} = \frac{I_p}{\sqrt{2}}$
 Where: $\phi = \theta_V - \theta_I$

$P = \frac{V_p I_p}{2} \cos(\theta_V - \theta_I)$ $Q = \frac{V_p I_p}{2} \sin(\theta_V - \theta_I)$

$P = V_{RMS} * I_{RMS} * \cos(\phi)$
 $Q = V_{RMS} * I_{RMS} * \sin(\phi)$

Representing $v(t)$, $i(t)$ as phasors, we have

$\bar{V} = V_{rms} \angle \theta_V$ Complex Power $S = \bar{V} \bar{I}^* = V_{rms} I_{rms} \angle (\theta_V - \theta_I)$
 $\bar{I} = I_{rms} \angle \theta_I$ $S = \bar{V} \bar{I}^* = P + jQ$

Handwritten note: $|S|$ is the magnitude of complex power, $\phi = \theta_V - \theta_I$.

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

6

Complex Power - ECEN 340

Representing sinusoidal voltage and current $v(t)$, $i(t)$ as phasors, we have

$\bar{V} = V_{rms} \angle \theta_V$
 $\bar{I} = I_{rms} \angle \theta_I$

$S = \bar{V} \bar{I}^* = P + jQ$

$(\phi) = \theta_V - \theta_I$

S : Complex power (VA, kVA, MVA)
 $|S|$: Apparent power (VA, kVA, MVA) $= V_{rms} * I_{rms}$

P : Real power (W, kW, MW) $= V_{rms} * I_{rms} * \cos(\phi)$
 Q : Reactive power (Var, kVar, Mvar) $= V_{rms} * I_{rms} * \sin(\phi)$

Power Factor (PF): $\cos(\phi)$

Handwritten note: Power Triangle diagram showing $|S|$, P , Q , and angle ϕ .

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

7

Conservation of Complex Power - ECEN 340

Suppose the two loads in Example # 1 and Example # 2 are connected in parallel.

$\bar{S}_1 = 800 + j600 \text{ VA}$ $\bar{S}_2 = 433 - j250 \text{ VA}$

The Total Power S is: $\bar{S} = \bar{S}_1 + \bar{S}_2 = (800 + 433) + j(600 - 250) = 1233 + j350 \text{ VA}$

Handwritten notes:

- Inductive (for \bar{S}_1)
- Capacitive (for \bar{S}_2)
- Power triangle for \bar{S}_1 : $S_1 = 1000$, $P = 800$, $Q = 600$, angle 36.8°
- Power triangle for \bar{S}_2 : $S_2 = 500$, $P = 433$, $Q = -250$, angle 30°
- Combined Power Triangle: $S = 1282$, $P = 1233$, $Q = 350$, angle 15.847°

The Total Input current I : $\bar{I} = \frac{\bar{S}}{\bar{V}} = \frac{1233 - j350}{100 \angle -10^\circ} = \frac{1282 \angle -15.847^\circ}{100 \angle -10^\circ} = 12.82 \angle -5.847^\circ \text{ A}$

From KVL, Input current: $\bar{I} = \bar{I}_1 + \bar{I}_2 = 10 \angle -26.8^\circ + 5 \angle 30^\circ = 12.82 \angle -5.847^\circ$

This proves the conservation of complex power

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

8

Power Factor / RMS - Fundamentals - Review

$$I = \frac{V}{Z} = \frac{120 \angle 0^\circ}{1.44 + j7.054} = 16.67 \angle -78.46^\circ$$

Complex Power

$$S = V \cdot I^* = (120 \angle 0^\circ) (16.67 \angle +78.46^\circ)$$

$$= 2000 \angle 78.46^\circ$$

$$S = 400 + j1959.6$$


Real Power $P = 400 \text{ W}$; Reactive Power $Q = 1959.6 \text{ VAR}$

Power Factor: $PF = \frac{\text{real power}}{\text{apparent power}} = \frac{P}{V_{rms} \cdot I_{rms}} = \frac{P}{|S|} = \frac{400}{2000} = 0.2$

$$PF = \frac{V \cdot I \cdot \cos(\theta)}{V \cdot I} = \cos(\theta) = \cos(78.46^\circ) = 0.2$$

$$v_s = \sqrt{2} \cdot 120 \cdot \cos(\omega t)$$

$$\omega = 2 \cdot \pi \cdot f$$

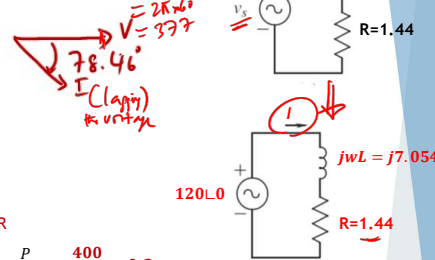

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

9

Power Factor / RMS - Fundamentals - PSIM Simulations


$$P = V \cdot I \cdot \cos(\theta) = 400 \text{ W}$$

$$I = 16.67 \text{ A}$$

If $PF = 1$, i.e. $\theta=0$, then for $V=120$, we need only $I = 3.33 \text{ A}$ for $P = 400 \text{ Watts}$
Q- How can accomplish this?

$$v_s = \sqrt{2} \cdot 120 \cdot \cos(\omega t)$$


$$\omega = 2 \cdot \pi \cdot f$$

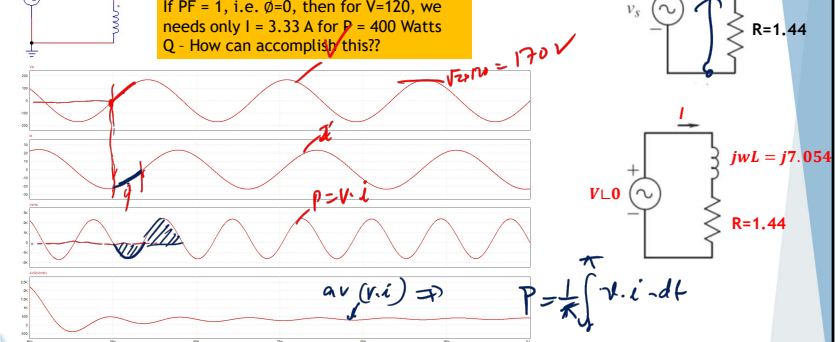

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

10

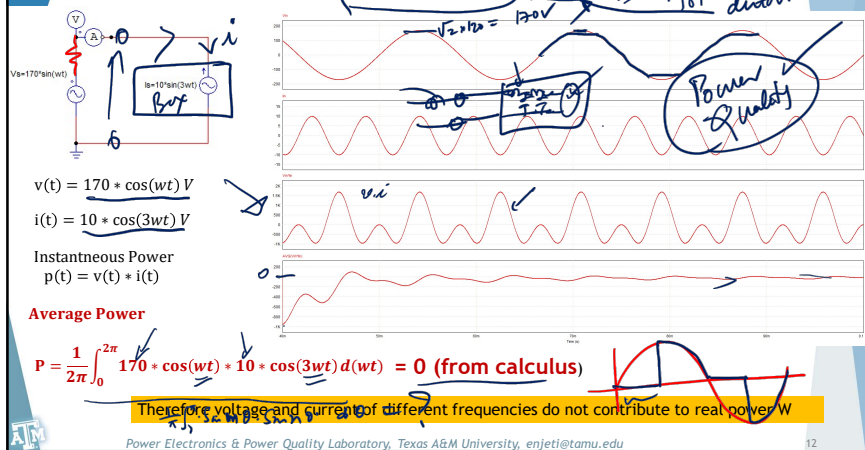Power Factor / RMS - Harmonics - THD - DE



Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

12

Definition of rms

$$v(t) = V_1 \sin(\omega_1 t) + V_2 \sin(\omega_2 t) + \dots$$

$$v(t) = V_1 \sin \omega t + V_2 \sin 3\omega t$$

Then V_{rms} is

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_1 \sin \omega t + V_2 \sin 3\omega t)^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T (V_1^2 \sin^2 \omega t + 2V_1 V_2 \sin \omega t \sin 3\omega t + V_2^2 \sin^2 3\omega t) dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T V_1^2 \sin^2 \omega t dt + \frac{1}{T} \int_0^T 2V_1 V_2 \sin \omega t \sin 3\omega t dt + \frac{1}{T} \int_0^T V_2^2 \sin^2 3\omega t dt}$$

$$V_{rms} = \sqrt{\left(\frac{V_1}{\sqrt{2}}\right)^2 + \left(\frac{V_2}{\sqrt{2}}\right)^2}$$

Therefore V_{rms} is

$$V_{rms} = \sqrt{\left(\frac{V_1}{\sqrt{2}}\right)^2 + \left(\frac{V_2}{\sqrt{2}}\right)^2}$$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

13

Total Harmonics - THD - PF - DF

Power Factor: $PF = \frac{\text{Real Power (watts)}}{\text{Apparent Power (volt. amps)}}$

$v(t) = \sqrt{2}V \cos(\omega t)$ Volts

$i(t) = \sqrt{2}I_1 \cos(\omega t - \phi_1) + \sqrt{2}I_3 \cos(3\omega t + \phi_3) + \sqrt{2}I_5 \cos(5\omega t + \phi_5)$ Amps

Real Power "P" =

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

14

Total Harmonics - THD - PF - DF

Power Factor: $PF = \frac{\text{Real Power (watts)}}{\text{Apparent Power (volt. amps)}}$

$v(t) = \sqrt{2}V \cos(\omega t)$ Volts

$i(t) = \sqrt{2}I_1 \cos(\omega t - \phi_1) + \sqrt{2}I_3 \cos(3\omega t + \phi_3) + \sqrt{2}I_5 \cos(5\omega t + \phi_5)$ Amps

Note: $I_{rms} = \sqrt{I_1^2 + I_3^2 + I_5^2}$

Real Power "P" = $V I_1 \cos(\phi_1)$

Apparent Power = $V * I_{rms}$

Power Factor: $PF = \frac{\text{Real Power (watts)}}{\text{Apparent Power (volt. amps)}} = \frac{V I_1 \cos(\phi_1)}{V * I_{rms}} = \frac{I_1 \cos(\phi_1)}{I_{rms}}$

Power Factor: $PF = \frac{I_1}{I_{rms}} * \cos(\phi_1)$

Distortion Factor (DF) = $\frac{I_1}{I_{rms}}$

Displacement Factor (DPF) = $\cos(\phi_1)$

Power Factor: $PF = DF * DPF$

Handwritten notes: $I_{rms} > I_1$, $0 \leq DF \leq 1$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

15

Total Harmonics - THD - PF - DF

$v(t) = \sqrt{2}V \sin(\omega t)$ Volts

$i(t) = \sqrt{2}I_1 \sin(\omega t - \phi_1) + \sqrt{2}I_3 \sin(3\omega t + \phi_3) + \sqrt{2}I_5 \sin(5\omega t + \phi_5)$ Amps

THD = $\frac{\text{rms of the harmonic components}}{\text{rms of the fundamental component}}$

Note: $I_{rms} = \sqrt{I_1^2 + I_3^2 + I_5^2}$

Therefore rms of the harmonic components = $\sqrt{I_3^2 + I_5^2}$

Not: $\sqrt{I_3^2 + I_5^2} = \sqrt{I_{rms}^2 - I_1^2}$

Therefore THD = $\frac{\sqrt{I_3^2 + I_5^2}}{I_1} = \frac{\sqrt{I_{rms}^2 - I_1^2}}{I_1} = \sqrt{\frac{I_{rms}^2}{I_1^2} - 1} = \sqrt{\frac{1}{DF^2} - 1}$

THD = $\sqrt{\frac{1}{DF^2} - 1}$

Handwritten notes: $DF = \frac{I_1}{I_{rms}}$, $But THD \neq 0$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

16