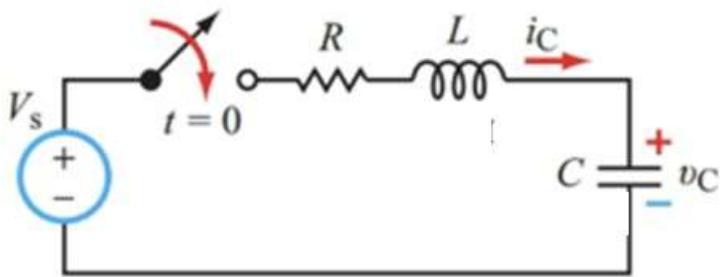


214 Test 3

- 1) For the circuit below, write down the differential equation and any auxiliary equations that are needed to find the current i_C for $t > 0$, and find the value of R that makes it critically damped.



For the circuit to be critically damped $\alpha = \omega_0$.

$$2L \cdot \frac{R}{2L} = \frac{1}{\sqrt{LC}} \cdot 2L$$

$$R = 2\sqrt{\frac{L}{C}}$$

- 2) For the circuit below, write down all the equations (including any auxiliary ones) needed to find the initial ($t = 0+$) values of both voltage and current on each element: capacitor, inductor and resistor.

For this circuit:

$$V_s = R i_c + L \frac{di_c}{dt} + v_c \quad \Rightarrow \quad i_c = C \frac{dv_c}{dt}$$

When $t > 0$:

$$\frac{d^2 v_c}{dt^2} + \frac{R}{L} \left(\frac{dv_c}{dt} \right) + \frac{1}{LC} v_c = \frac{V_s}{LC}$$

And:

$$v_c(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_c(\infty)$$


where s_1 and s_2 -

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

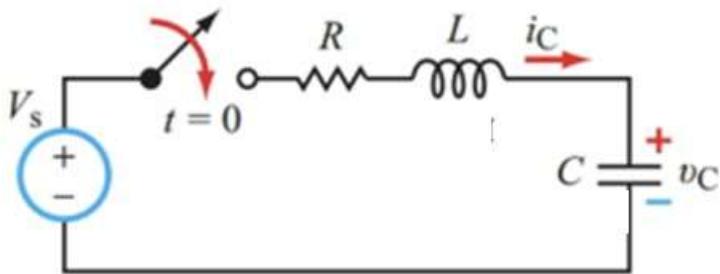

$$v_c(t) = [A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_c(\infty)]$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


$$A_1 = \frac{\frac{1}{C} i_c(0) - s_1 [v_c(0) - v_c(\infty)]}{s_1 - s_2}$$

$$A_2 = \frac{\left[\frac{1}{C} i_c(0) - s_2 [v_c(0) - v_c(\infty)] \right]}{s_1 - s_2}$$

$$i_c(t) = C \frac{dv_c}{dt}$$

214 Hemmer sections -- Test 3 -- Name _____

- 3) For the circuit below, write down all the equations needed to find the current i_C when the source voltage is $|V_s| \angle 0^\circ$ and the switch has been closed for a long time. Then evaluate i_C at the frequency where the circuit is critically damped.
Hint: Use equations from problem 1 to complete the second part.

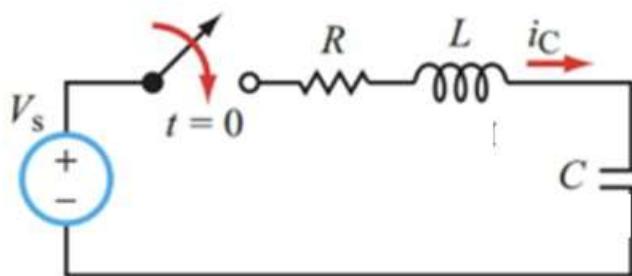

$$|V_s| < 0^\circ = V_s, X = |V_s| \cos(\theta), Y = |V_s| \sin(\theta)$$


$$\text{when } t=0, V_c(0) = V_c(0^+) = 0 \text{ AND } V_c(\infty) = V_s$$

$$B_1 = V_c(0) - V_c(\infty) \quad B_2 = \frac{1}{C} \dot{V}_c(0) + \alpha [V_c(0) - V_c(\infty)]$$

$$V(t) = (B_1 + B_2 t) e^{-\alpha t} + V_c(\infty)$$

$$\begin{aligned} i_L &= C \left[-\alpha V_s e^{-\alpha t} - \cancel{\alpha} \cancel{(V_s - \alpha V_s t)} e^{-\alpha t} \right] \\ &= C \underline{\underline{[\alpha^2 V_s t e^{-\alpha t}]}} \end{aligned}$$

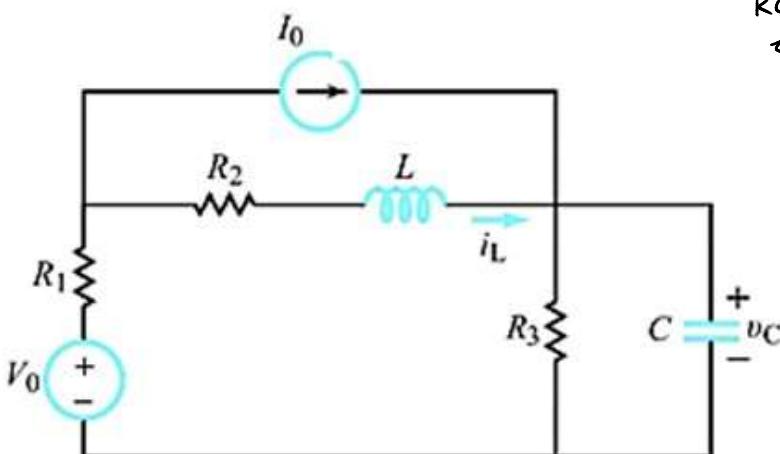- 4) At $t = 0^+$ for the circuit below, write down all the equations needed to find v_C and i_L . Hint: Be sure to identify the procedure needed to find a differential equation with only one variable, also write down any auxiliary equations that are needed.



KCL at node 2 leads to
 $\dot{i}_c(0) = I_0 + \dot{i}_L(0) - \dot{i}_{R_3}(0)$


Determine $V_L(0)$

$$\dot{i}_L(0) = I_0 + \dot{i}_c(0)$$

KVL around lower left loop

$$V_L(0) = V_0 - R_1 \dot{i}_1 - R_2 \dot{i}_L - V_{R_3}$$

Redraw -

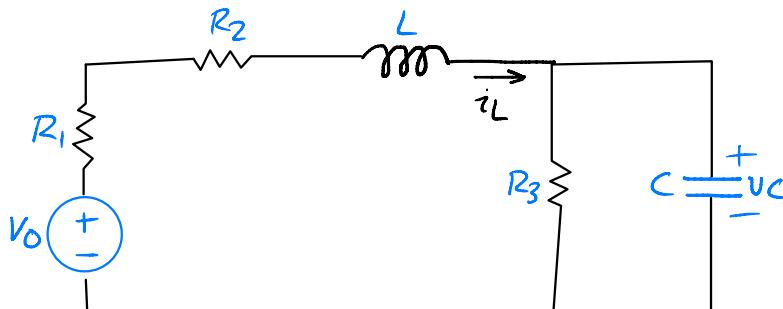

Since $\dot{i}_c(0^-) = 0$

$$\dot{i}_L(0^-) = \frac{V_0}{R_1 + R_2 + R_3}$$

$$\dot{i}_{R_3}(0^-) = \dot{i}_L(0^-)$$


$$V_c(0^-) = \dot{i}_L(0^-) R_3$$

$$V_c(0) = V_c(0^-)$$

$$\text{Next: } \dot{i}_{R_3}(0) = \frac{V_c(0)}{R_3}$$

214 Hemmer sections -- Test 3 -- Name _____

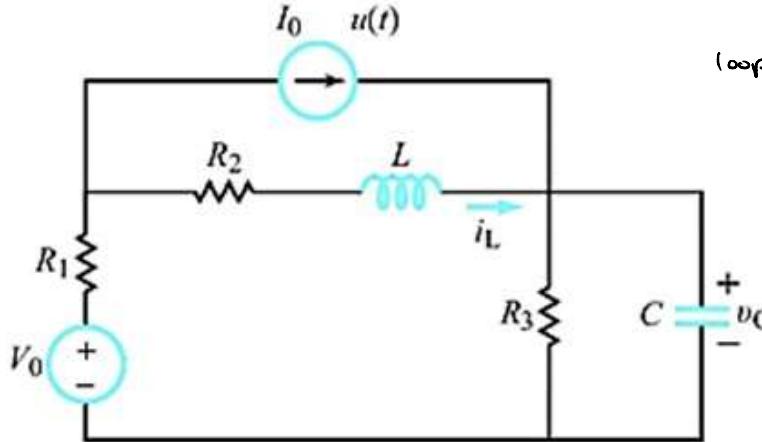- 5) At $t = 0^+$ for the circuit below, write down all the equations needed to find the initial currents and voltages on both the inductor and capacitor. Hint: Do not forget any auxiliary equations.



At $t = \infty$:


The mesh Equation for loop 1 is
 $-V_0 + R_1 i_1 + R_2 (i_1 - i_2) + R_3 i_1 = 0$

for loop 2,
 $i_2 = I_0$

This leads to ...

 $i_L(\infty) = i_1 - I_0$
 $v_C(\infty) = i_1 R_3$

- 6) For the circuit below, write down all the equations needed to find the current v_C and i_L when the voltage is a cosine function $|V_s| / 0^\circ$ and current source is $|I_0| / 90^\circ$ and the switch has been closed for a long time. *Polar form*

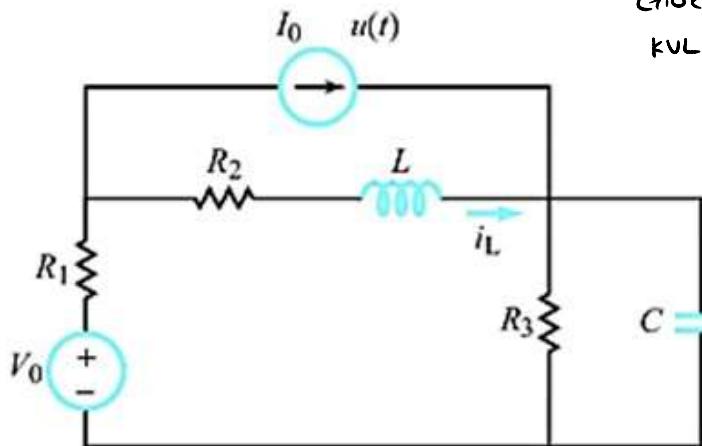

Given $|V_s| < 0^\circ = V_s$, $|I_0| < 90^\circ = I_0 j = I_0 \sqrt{-1}$
 KVL for loop 1:

$$-V_s + R_1 I_1 + R_2 (i_1 - i_2) + R_3 i_1 = 0$$

And at loop 2

$$i_2 = I_0 \sqrt{-1}$$

$$\frac{V_s}{i_1} = R_1 + R_2 - \frac{R_2 i_2}{i_1} + R_3$$

$$\frac{R_2 i_2}{i_1} + \frac{V_s}{i_1} = R_1 + R_2 + R_3$$

$$i_1 = \frac{V_s + R_2 i_2}{R_1 + R_2 + R_3}$$


for $t = \infty$.

$$i_C(\infty) = i_1 - I_0 \sqrt{-1}$$

$$v_C(\infty) = i_1 R_3$$


214 Hemmer sections -- Test 3 -- Name _____

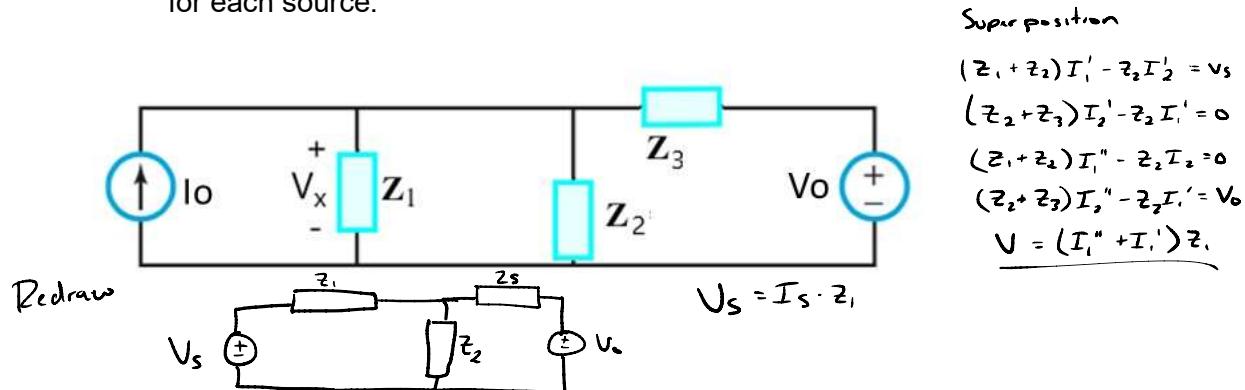- 7) For the circuit below use superposition to find the contribution to V_x from both the current and the voltage sources. Hint: Be sure to write down separate equations for each source.




6.8.3

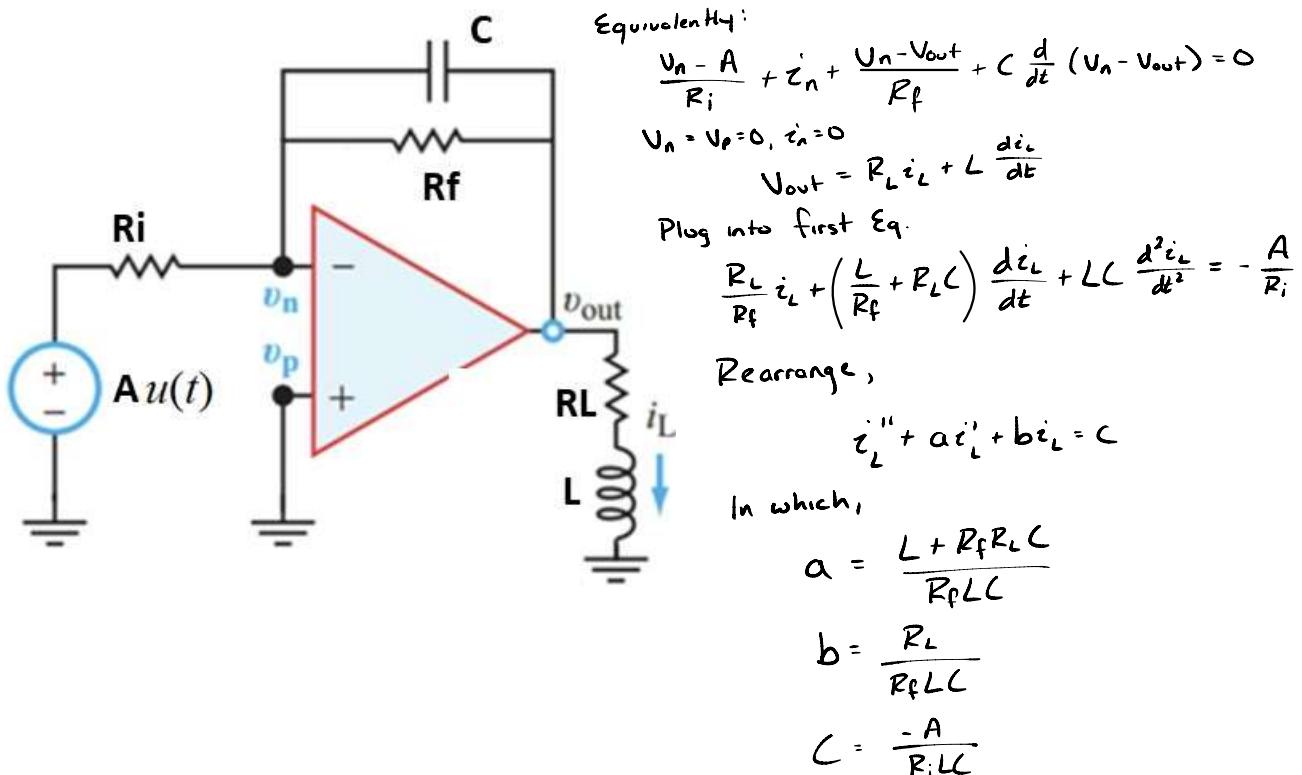- 8) At $t = 0^+$ for the circuit below, write down all the equations (differential and auxiliary) needed to find i_L . Hint: Be sure to identify the procedure needed to find a differential equation with only one variable.



214 Hemmer sections -- Test 3 -- Name _____

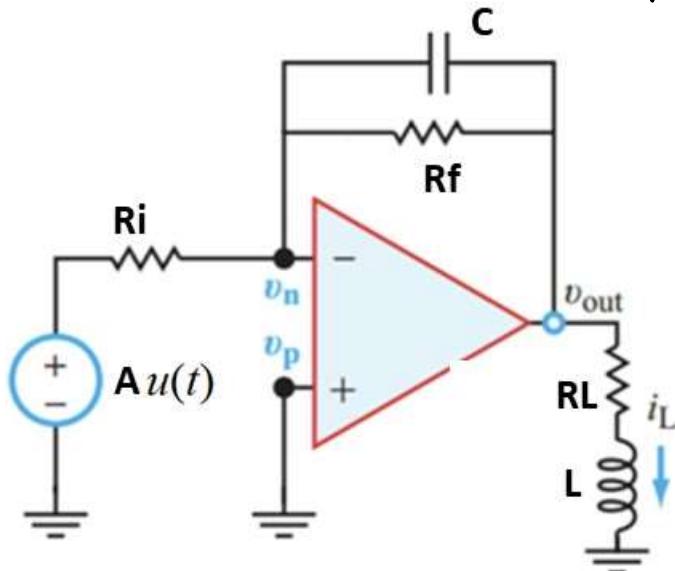- 9) For the circuit below, write down all the equations (including any auxiliary ones) needed to find the initial ($t = 0+$) values of both voltage and current on the capacitor and the inductor.



The damping behavior of i_L is determined by how the magnitude of α compares with ω_0

$$\alpha = \frac{a}{2} \text{ and } \omega_0 = \sqrt{b}$$

$$i_L(t) = [A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_L(\infty)] u(t).$$

$$\text{where, } s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$\text{At } t = \infty, V_{out}(\infty) = -\frac{R_f}{R_i} A.$$


$$\text{And } i_L(\infty) = \frac{V_{out}(\infty)}{R_L} = -\frac{R_f A}{R_i R_L}$$

The charge can not change immediately
Inductor acts as an open circuit at $t=0$.
 $V_{out}(0)=0, V_L(0)=0$ and $i_L'(0) = \frac{1}{L} V_L(0) = 0$

$$A_1 = \frac{i_L'(0) - s_2 [i_L(0) - i_L(\infty)]}{s_1 - s_2} \quad \text{AND} \quad A_2 = -\frac{[i_L'(0) - s_2 [i_L(0) - i_L(\infty)]]}{s_1 - s_2}$$

- 10) For the circuit below, write down all the equations needed to find the current i_L when the source voltage is a cosine with $|A| \angle 0^\circ$ and has been on for a long time ($t > 0$).

Given

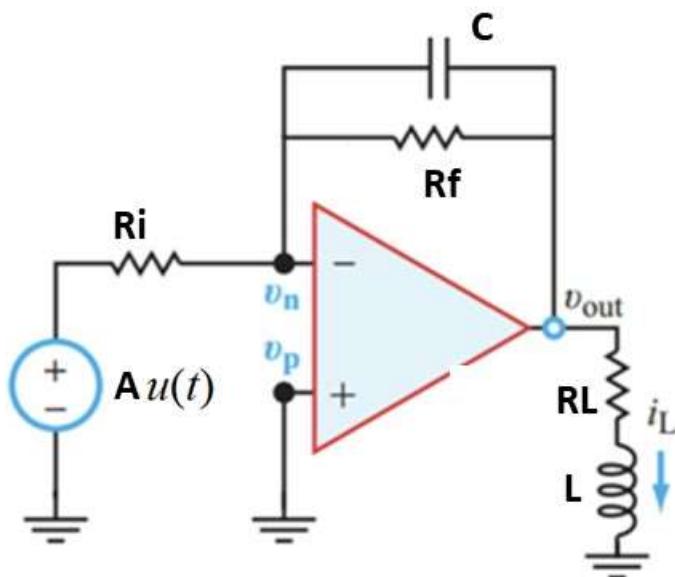

$$|A| \angle 0^\circ = A$$


$$V_{out}(\infty) = -\frac{R_f}{R_i} A$$

$$t = \infty$$

$$i_L(\infty) = \frac{V_{out}(\infty)}{R_L} = -\frac{R_f A}{R_i R_L}$$

214 Hemmer sections -- Test 3 -- Name _____

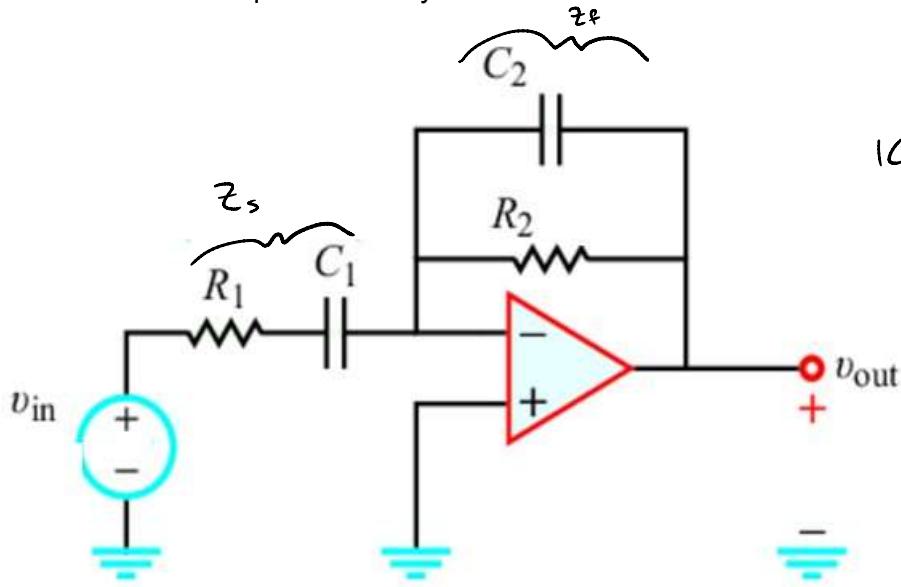- 11) For the circuit below, write down the differential and auxiliary equations that are needed to find the output voltage, V_{out} . Hint: Be sure to outline how to find a differential equation of only one variable.




$$\omega_s = 2\pi \times V_{in} \text{ (frequency)}$$

$$|G| = \frac{\omega R_2 C_1}{[(1 + \omega^2 R_1^2 C_1^2)(1 + \omega^2 R_2^2 C_2^2)]^{1/2}}$$

$$|V_{out}| = |G| |V_{in}|$$

- 12) For the circuit below, write down all the equations needed to find the output voltage V_{out} , when the source voltage is $|V_{in}| / 0^\circ$.

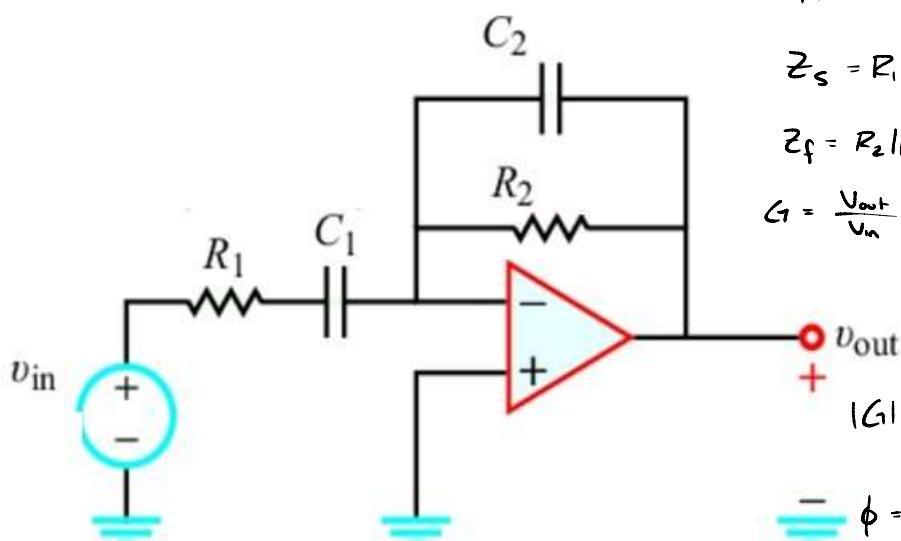

Inverting amp w/ complex source

$$Z_s = R_1 + \frac{1}{j\omega C_1} = \frac{j\omega R_1 C_1 + 1}{j\omega C_1}$$

$$Z_f = R_2 \parallel \frac{1}{j\omega C_2} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$G = \frac{V_{out}}{V_{in}} = -\frac{Z_f}{Z_s} = \frac{-j\omega R_2 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

$$G = G e^{j\phi}$$

$$|G| = \frac{\omega R_2 C_1}{[(1 + \omega^2 R_1^2 C_1^2)(1 + \omega^2 R_2^2 C_2^2)]^{1/2}}$$


$$\phi = 0^\circ - \tan^{-1}(\omega R_1 C_1) - \tan^{-1}(\omega R_2 C_2)$$

$$V_{out}(t) = |G| V_{in} \cos(\omega t + \phi)$$

214 Hemmer sections -- Test 3 -- Name _____

Extra credit section

EC1) For the circuit below, make a log-log plot of the gain magnitude $|V_{out}/V_{in}|$ vs ω (use can use angular frequency). Also make a semi-log plot of the phase shift vs $\log \omega$. Label x and y values at locations where there are noticeable changes in slope (for magnitude plots) or phase. Choose two cases: 1) $R_1 C_1 \gg R_2 C_2$ (at least 100 X) and 2) $R_1 C_1 \ll R_2 C_2$. Hint: there will be 4 plots total, 2 magnitude and 2 phase.

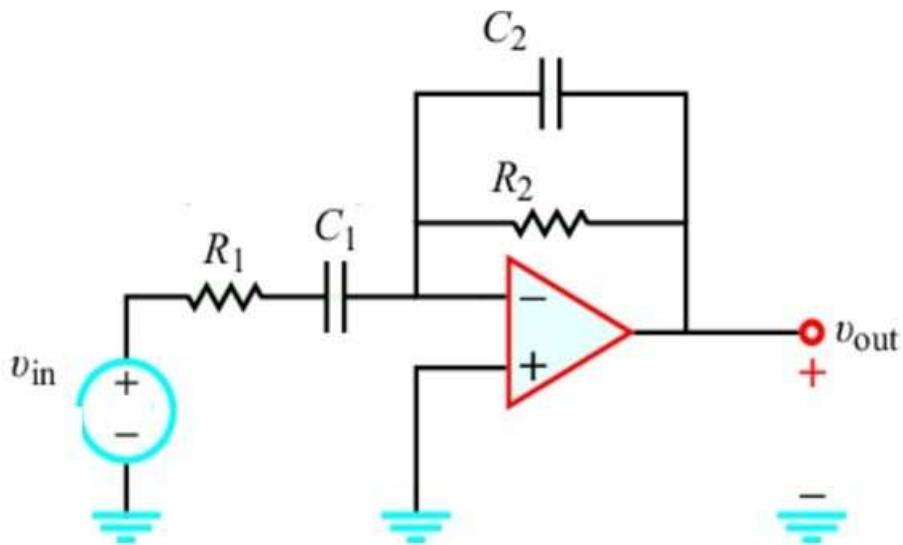

214 Hemmer sections -- Test 3 -- Name _____

EC2) For the two circuits below, make a log-log plot of the gain magnitude $|V_{out}/V_{in}|$ vs w (use can use angular frequency). Also make a semi-log plot of the phase shift vs log w . Label x and y values at locations where there are noticeable changes in slope (for magnitude plots) or phase. Choose two cases: 1) $R_2 \gg R_1$ and $C_2 \ll C_1$ (at least 100 X) but $R_1 C_1 = R_2 C_2$, and 2) $R_1 = R_2$ and $C_1 = C_2$. Hint: there will be 4 plots total, 2 magnitude and 2 phase for each of the two circuits.

