



ECEN 248

Introduction to Digital Systems Design

Lecture 2

Boolean Algebra and its Relation to Digital Circuits

- “Traditional” algebra
 - Variables represent real numbers (x, y)
 - Operators operate on variables, return real numbers ($2.5x + y - 3$)
- **Boolean Algebra**
 - Variables represent 0 or 1 only
 - Operators return 0 or 1 only
 - Basic operators
 - AND: $a \text{ AND } b$ returns 1 only when both $a=1$ and $b=1$
 - OR: $a \text{ OR } b$ returns 1 if either (or both) $a=1$ or $b=1$
 - NOT: $\text{NOT } a$ returns the opposite of a (1 if $a=0$, 0 if $a=1$)

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1


a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



George Boole

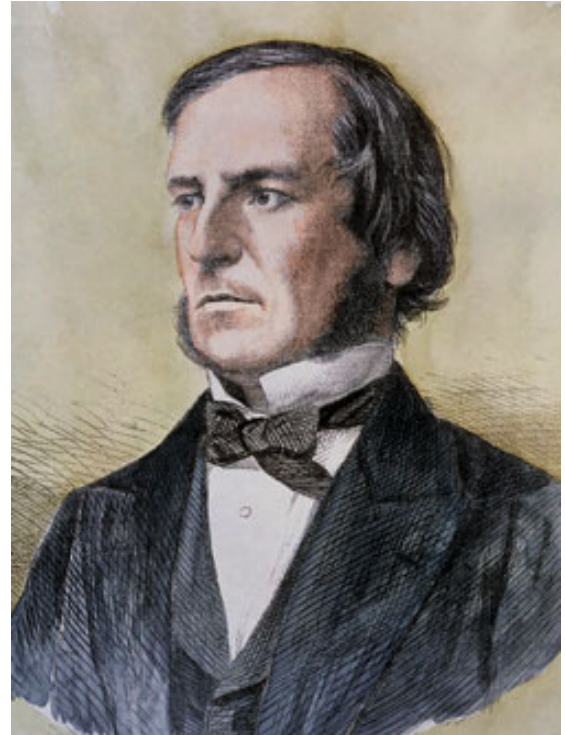- English mathematician, 1815-1864
- Author of *Laws of Thoughts* (1854)
- Creator of Boolean Algebra



Boolean Algebra and its Relation to Digital Circuits

(Scalable)

- Developed mid-1800's by George Boole to formalize human thought
 - Ex: "I'll go to lunch if Mary goes OR John goes, AND Sally does not go."
 - Let F represent my going to lunch (1 means I go, 0 I don't go)
 - Likewise, m for Mary going, j for John, and s for Sally
 - Then **$F = (m \text{ OR } j) \text{ AND NOT}(s)$**
 - Nice features
 - Formally evaluate**
 - $m=1, j=0, s=1 \rightarrow F = (1 \text{ OR } 0) \text{ AND NOT}(1) = 1 \text{ AND } 0 = \underline{0}$
 - Formally transform**
 - $F = (m \text{ and NOT}(s)) \text{ OR } (j \text{ and NOT}(s))$
 - Looks different, but same function
 - We'll show transformation techniques soon
 - Formally prove**
 - Prove that if Sally goes to lunch ($s=1$), then I don't go ($F=0$)
 - $F = (m \text{ OR } j) \text{ AND NOT}(1) = (m \text{ OR } j) \text{ AND } 0 = 0$

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Evaluating Boolean Equations

- Evaluate the Boolean equation $F = (a \text{ AND } b) \text{ OR } (c \text{ AND } d)$ for the given values of variables a , b , c , and d :
 - Q1: $a=1, b=1, c=1, d=0$.
 - Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 0) = 1 \text{ OR } 0 = 1$.
 - Q2: $a=0, b=1, c=0, d=1$.
 - Answer: $F = (0 \text{ AND } 1) \text{ OR } (0 \text{ AND } 1) = 0 \text{ OR } 0 = 0$.
 - Q3: $a=1, b=1, c=1, d=1$.
 - Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 1) = 1 \text{ OR } 1 = 1$.

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Converting to Boolean Equations

- **Convert the following English statements to a Boolean equation**
 - Q1. a is 1 and b is 1.
 - Answer: $F = a \text{ AND } b$
 - Q2. either of a or b is 1.
 - Answer: $F = a \text{ OR } b$
 - Q3. a is 1 and b is 0.
 - Answer: $F = a \text{ AND NOT}(b) = b \text{ is } 0$
 - Q4. a is not 0.
 - Answer:
 - (a) Option 1: $F = \text{NOT}(\text{NOT}(a))$
 - (b) Option 2: $F = a$




Converting to Boolean Equations


- Q1. A fire sprinkler system should spray water if high heat is sensed and the system is set to enabled.
 - Answer: Let Boolean variable h represent “high heat is sensed,” e represent “enabled,” and F represent “spraying water.” Then an equation is: $F = h \text{ AND } e$.
- Q2. A car alarm should sound if the alarm is enabled, and either the car is shaken or the door is opened.
 - Answer: Let a represent “alarm is enabled,” s represent “car is shaken,” d represent “door is opened,” and F represent “alarm sounds.” Then an equation is: $F = a \text{ AND } (s \text{ OR } d)$.
 - (a) Alternatively, assuming that our door sensor d represents “door is closed” instead of open (meaning $d=1$ when the door is closed, 0 when open), we obtain the following equation: $F = a \text{ AND } (s \text{ OR } \text{NOT}(d))$.




NOT gate

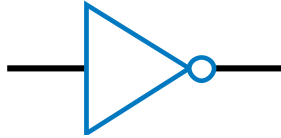


x	F
0	1
1	0

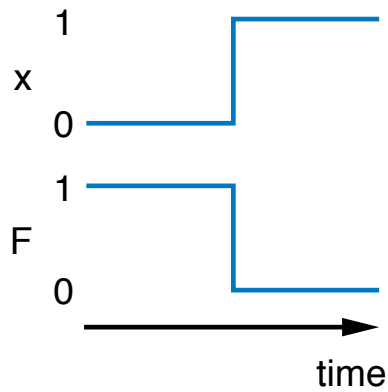


OR gate

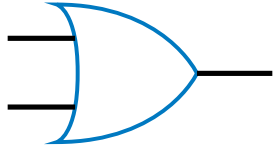


x	y	F
0	0	0
0	1	1
1	0	1
1	1	1

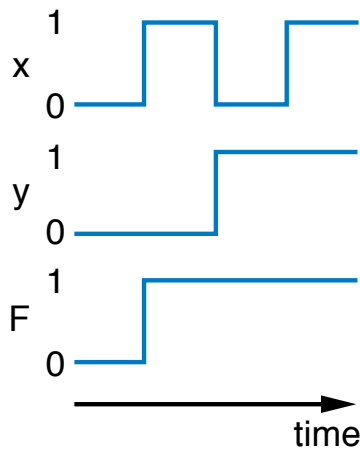

AND gate

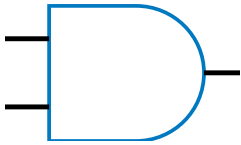


x	y	F
0	0	0
0	1	0
1	0	0
1	1	1

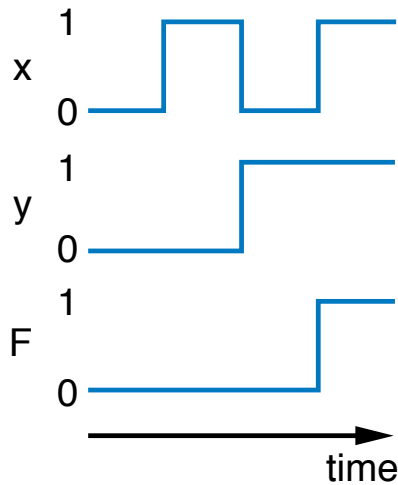


Claude Shannon

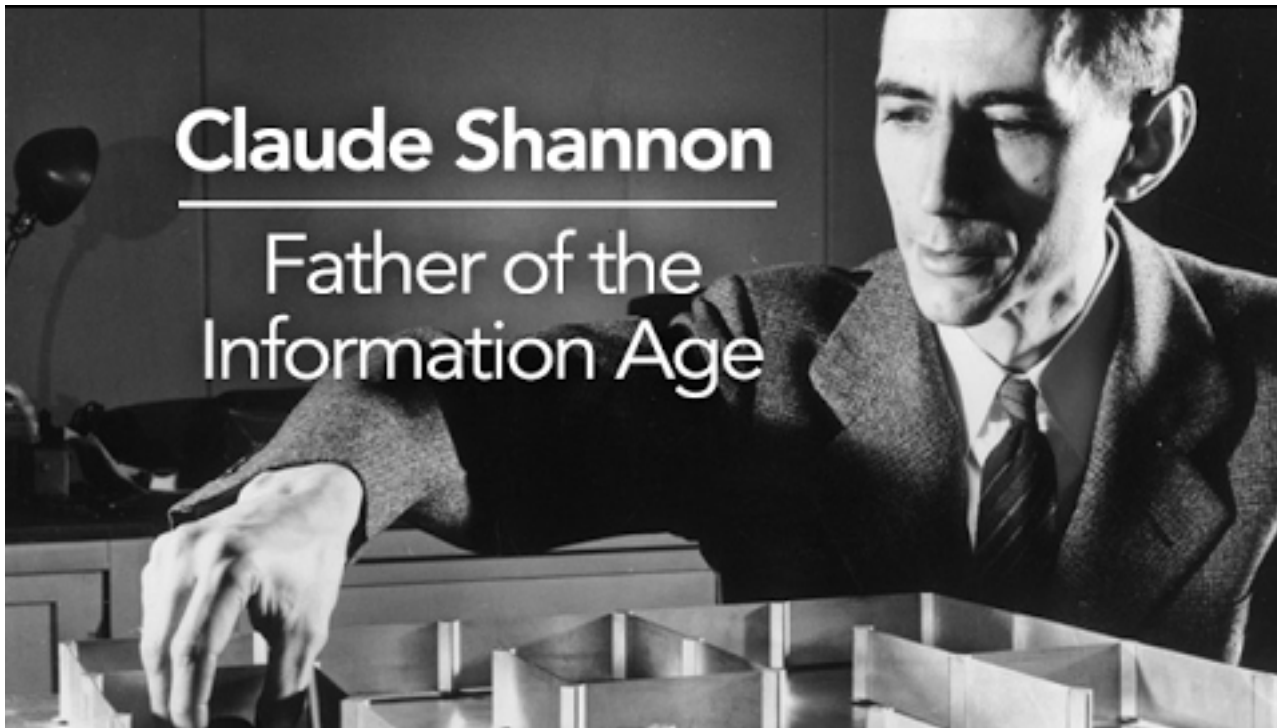- American mathematician & electrical engineer (1916-2001)
- *A symbolic analysis of switching and delay circuits*, Master's thesis, MIT , 1937.



Building Circuits Using Gates

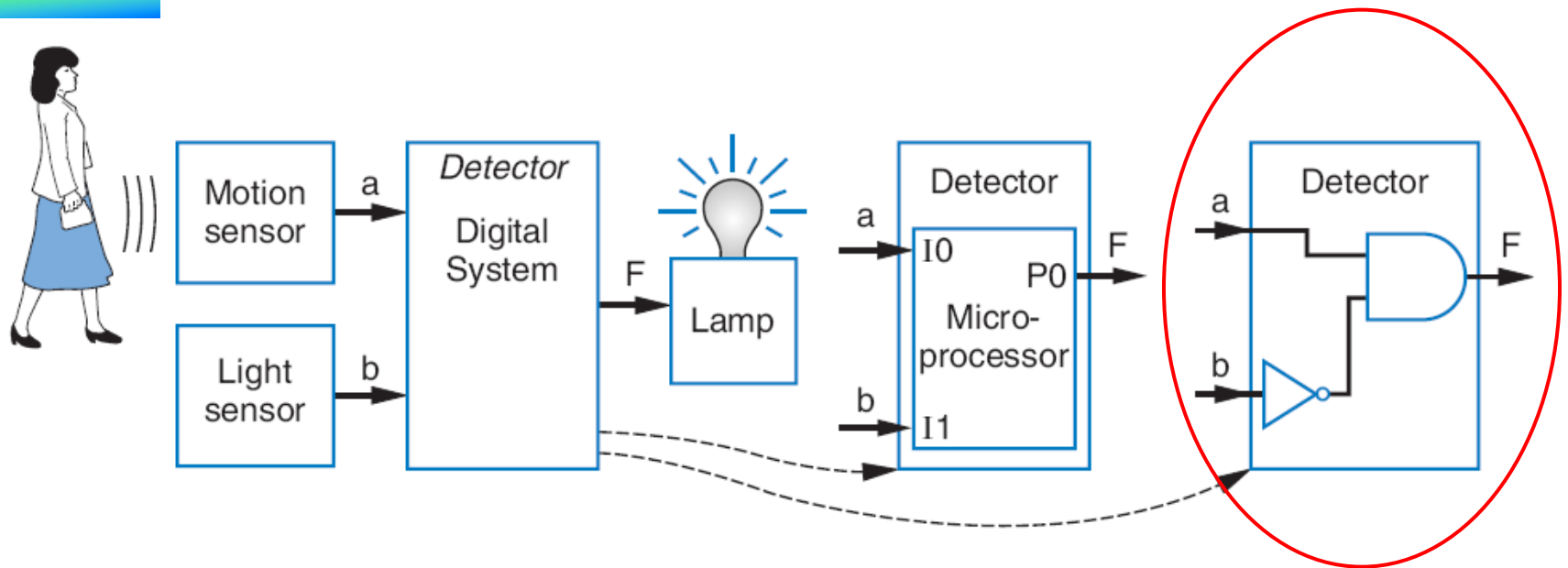


- Turn on lamp ($F=1$) when motion sensed ($a=1$) and no light ($b=0$)
- $F = a \text{ AND NOT}(b)$
- Build using logic gates, AND and NOT, as shown
- We just built our first digital circuit!




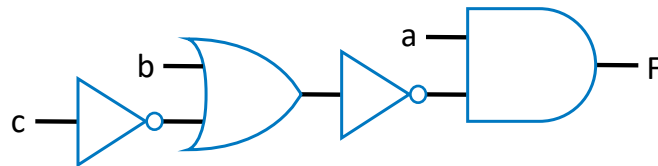
Example: Converting a Boolean Equation to a Circuit of Logic Gates

Start from the output, work back towards the inputs

- Q: Convert the following equation to logic gates:
$$F = a \text{ AND NOT}(b \text{ OR NOT}(c))$$




More examples

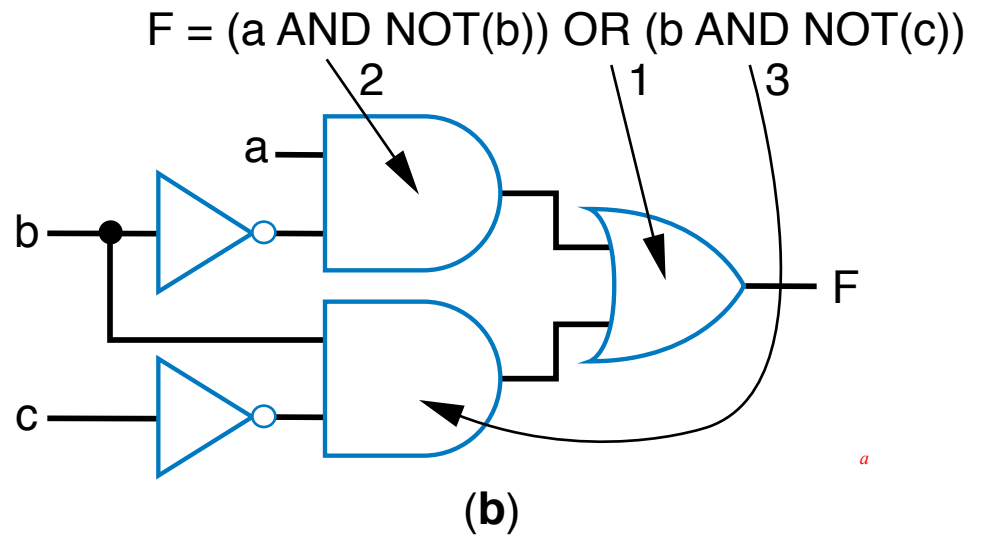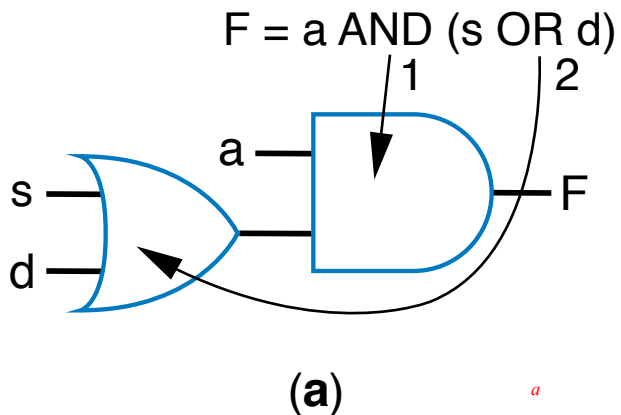

Start from the output, work back towards the inputs



Using gates with more than 2 inputs

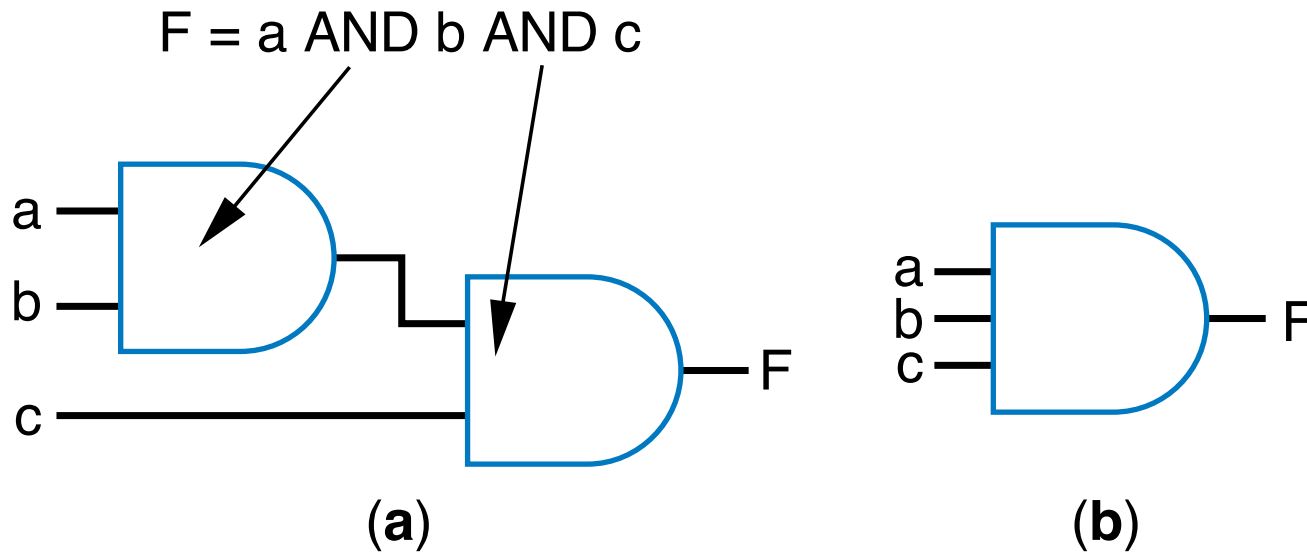


Can think of as $AND(a,b,c)$



Example: Seat Belt Warning Light System


- Design circuit for warning light
- Sensors
 - $s=1$: seat belt fastened
 - $k=1$: key inserted
- Capture Boolean equation
 - seat belt not fastened, and key inserted
- Convert equation to circuit

$$w = \text{NOT}(s) \text{ AND } k$$

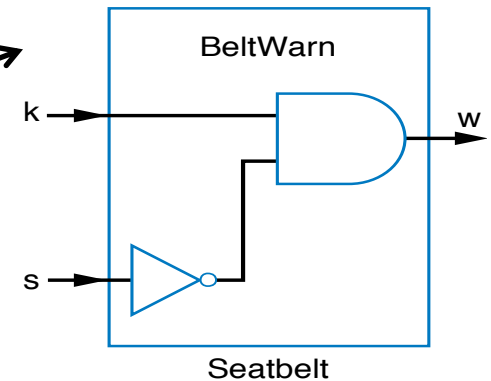


- *Timing diagram* illustrates circuit behavior

Inputs


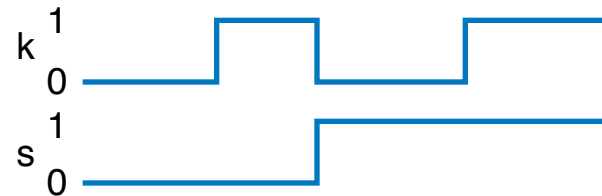


Outputs


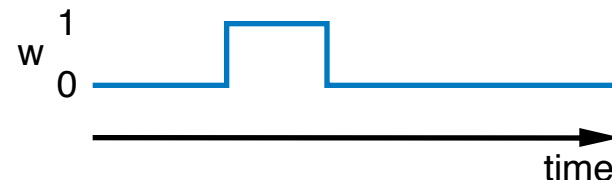


More examples: Seat belt warning light extensions

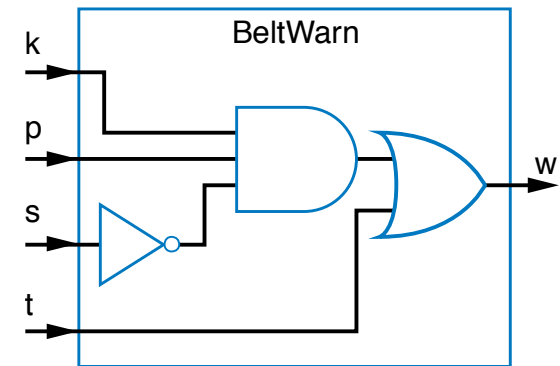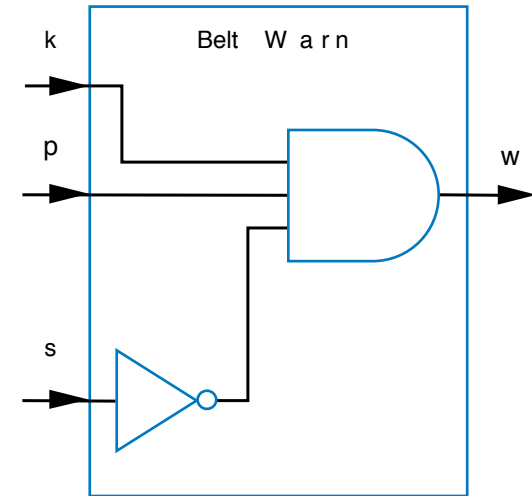
- Only illuminate warning light if person is in the seat ($p=1$), and seat belt not fastened and key inserted
- $w = p \text{ AND NOT}(s) \text{ AND } k$
- Given $t=1$ for 5 seconds after key inserted. Turn on warning light when $t=1$ (to check that warning lights are working)
- $w = (p \text{ AND NOT}(s) \text{ AND } k) \text{ OR } t$



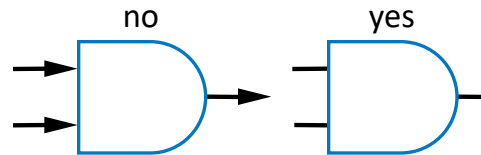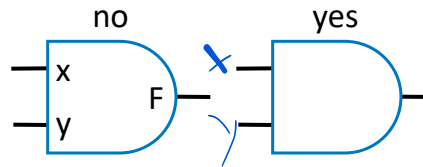Some Gate-Based Circuit Drawing Conventions



a

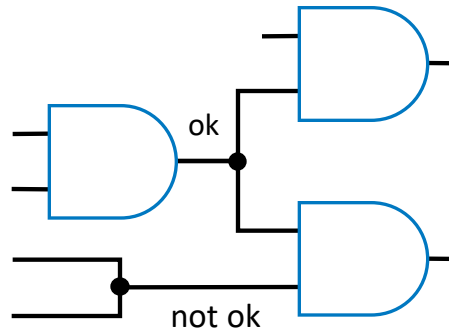

a



Boolean Algebra

- By defining logic gates based on Boolean algebra, we can *use algebraic methods to manipulate circuits*
- Notation: Writing a AND b, a OR b, NOT(a) is cumbersome
 - Use symbols: $a * b$ (or just ab), $a + b$, and a'
 - Original: $w = (p \text{ AND NOT}(s) \text{ AND } k) \text{ OR } t$
 - New: $w = ps'k + t$
 - Spoken as “w equals p and s prime and k, or t”
 - Or just “w equals p s prime k, or t”
 - s' known as “complement of s”
 - While symbols come from regular algebra, **don't** say “times” or “plus”
 - “product” and “sum” are OK and commonly used

Boolean algebra precedence, highest precedence first.

Symbol	Name	Description
()	Parentheses	Evaluate expressions nested in parentheses first
'	NOT	Evaluate from left to right
*	AND	Evaluate from left to right
+	OR	Evaluate from left to right



Boolean Algebra Operator Precedence

- Evaluate the following Boolean equations, assuming $a=1$, $b=1$, $c=0$, $d=1$.
 - Q1. $F = a * b + c$.
 - Answer: $*$ has precedence over $+$, so we evaluate the equation as $F = (1 * 1) + 0 = (1) + 0 = 1 + 0 = 1$.
 - Q2. $F = ab + c$.
 - Answer: the problem is identical to the previous problem, using the shorthand notation for $*$.
 - Q3. $F = ab'$.
 - Answer: we first evaluate b' because NOT has precedence over AND, resulting in $F = 1 * (1') = 1 * (0) = 1 * 0 = 0$.
 - Q4. $F = (ac)'$.
 - Answer: we first evaluate what is inside the parentheses, then we NOT the result, yielding $(1*0)' = (0)' = 0' = 1$.
 - Q5. $F = (a + b') * c + d'$.
 - Answer: Inside left parentheses: $(1 + (1')) = (1 + (0)) = (1 + 0) = 1$. Next, $*$ has precedence over $+$, yielding $(1 * 0) + 1' = (0) + 1'$. The NOT has precedence over the OR, giving $(0) + (1') = (0) + (0) = 0 + 0 = 0$. [Boolean algebra precedence, highest precedence first.](#)

Symbol	Name	Description
()	Parentheses	Evaluate expressions nested in parentheses first
'	NOT	Evaluate from left to right
*	AND	Evaluate from left to right
+	OR	Evaluate from left to right



Boolean Algebra Terminology

- Example equation: $F(a,b,c) = a'bc + abc' + ab + c$
- **Variable**
 - Represents a value (0 or 1)
 - Three variables: a, b, and c
- **Literal**
 - Appearance of a variable, in true or complemented form
 - Nine literals: a' , b, c, a, b' , c' , a, b, and c
- **Product term**
 - Product of literals
 - Four product terms: $a'bc$, abc' , ab, c
- **Sum-of-products**
 - Equation written as OR of product terms only
 - Above equation is in sum-of-products form. “ $F = (a+b)c + d$ ” is not.

$$x^2+2x+3$$

$$F=ac+bc+d$$



Boolean Algebra Properties

- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - Can write as: $a(b+c) = ab + ac$
 - $a + (b * c) = (a + b) * (a + c)$
 - (This second one is tricky!)
 - Can write as: $a+(bc) = (a+b)(a+c)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- To prove, just evaluate all possibilities


Example uses of the properties

- Show abc' equivalent to $c'ba$.
 - Use commutative property:
 - $a*b*c' = a*c'*b = c'*a*b = c'*b*a$
- Show $abc + abc' = ab$.
 - Use first distributive property
 - $abc + abc' = ab(c+c')$
 - Complement property
 - Replace $c+c'$ by 1: $ab(c+c') = ab(1)$.
 - Identity property
 - $ab(1) = ab*1 = ab$.
- Show $x + x'z$ equivalent to $x + z$.
 - Second distributive property
 - Replace $x+x'z$ by $(x+x')*(x+z)$.
 - Complement property
 - Replace $(x+x')$ by 1,
 - Identity property
 - replace $1*(x+z)$ by $x+z$.



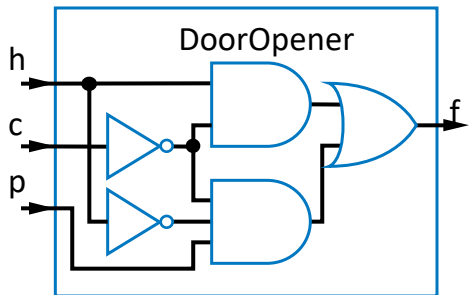Example that Applies Boolean Algebra Properties

- Want automatic door opener circuit (e.g., for grocery store)
 - Output: $f=1$ opens door
 - Inputs:
 - $p=1$: person detected
 - $h=1$: switch forcing hold open
 - $c=1$: key forcing closed
 - Want open door when
 - $h=1$ and $c=0$, or
 - $h=0$ and $p=1$ and $c=0$
 - Equation: $f = hc' + h'pc'$



- Can the circuit be simplified?

$$f = hc' + h'pc'$$


$$f = c'h + c'h'p \quad (\text{by the commutative property})$$

$$f = c'(h + h'p) \quad (\text{by the first distrib. property})$$

$$f = c'((h+h')*(h+p)) \quad (\text{2nd distrib. prop.; tricky one})$$

$$f = c'((1)*(h+p)) \quad (\text{by the complement property})$$
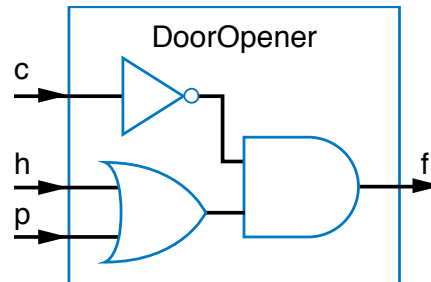
$$f = c'(h+p) \quad (\text{by the identity property})$$



Simplified
circuit


*Simplification of circuits is covered
in Sec. 2.11 / Sec 6.2.*



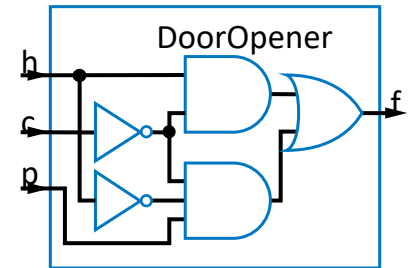Example that Applies Boolean Algebra Properties



- Found inexpensive chip that computes:
 - $f = c'hp + c'hp' + c'h'p$
 - Can we use it for the door opener?
 - Is it the same as $f = hc' + h'pc'$?
- Apply Boolean algebra:
- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$



$$f = c'hp + c'hp' + c'h'p$$

$$f = c'h(p + p') + c'h'p \text{ (by the distributive property)}$$

$$f = c'h(1) + c'h'p \text{ (by the complement property)}$$

$$f = c'h + c'h'p \text{ (by the identity property)}$$

$$f = hc' + h'pc' \text{ (by the commutative property)}$$

Same! Yes, we can use it.



Boolean Algebra: Additional Properties

- Null elements
 - $a + 1 = 1$
 - $a * 0 = 0$
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a' b'$
 - $(ab)' = a' + b'$
 - *Very useful!*
- To prove, just evaluate all possibilities





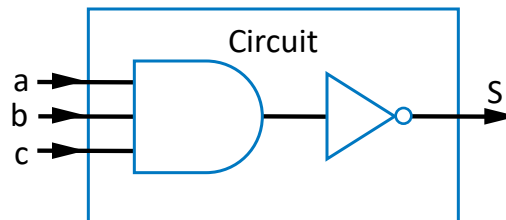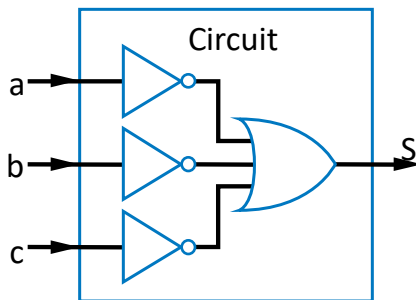Example Applying DeMorgan's Law

Aircraft lavatory sign example



- Behavior
 - Three lavatories, each with sensor (a, b, c), equals 1 if door locked
 - Light "Available" sign (S) if any lavatory available
- Equation and circuit
 - $S = a' + b' + c'$
- Transform
 - $(abc)' = a' + b' + c'$ (by DeMorgan's Law)
 - $S = (abc)'$
- New circuit



$$(a + b)' = a' b'$$

$$(ab)' = a' + b'$$

- Alternative: Instead of lighting "Available," light "Occupied"
- Opposite of "Available" function
 - $S = a' + b' + c'$
- So $S' = (a' + b' + c')'$
 - $S' = (a')' * (b')' * (c')'$ (by DeMorgan's Law)
 - $S' = a * b * c$ (by Involution Law)
- Makes intuitive sense
 - Occupied if all doors are locked



Example Applying Properties

- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- Null elements
 - $a + 1 = 1$
 - $a * 0 = 0$
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a' b'$
 - $(ab)' = a' + b'$
- For door opener $f = c'(h+p)$, *prove* door stays closed ($f=0$) when $c=1$
 - $f = c'(h+p)$
 - *Let $c = 1$* (door forced closed)
 - $f = 1'(h+p)$
 - $f = 0(h+p)$
 - $f = 0h + 0p$ (by the distributive property)
 - $f = 0 + 0$ (by the null elements property)
 - $f = 0$




Complement of a Function

- Commonly want to find complement (inverse) of function F
 - 0 when F is 1; 1 when F is 0
- Use DeMorgan's Law repeatedly
 - Note: DeMorgan's Law defined for more than two variables, e.g.:
 - $(a + b + c)' = (abc)'$
 - $(abc)' = (a' + b' + c')$
- Complement of $f = w'xy + wx'y'z'$
 - $f' = (w'xy + wx'y'z')'$
 - $f' = (w'xy)'(wx'y'z')'$ (by DeMorgan's Law)
 - $f' = (w+x+y')(w'+x+y+z)$ (by DeMorgan's Law)
- Can then expand into sum-of-products form



Representations of Boolean Functions

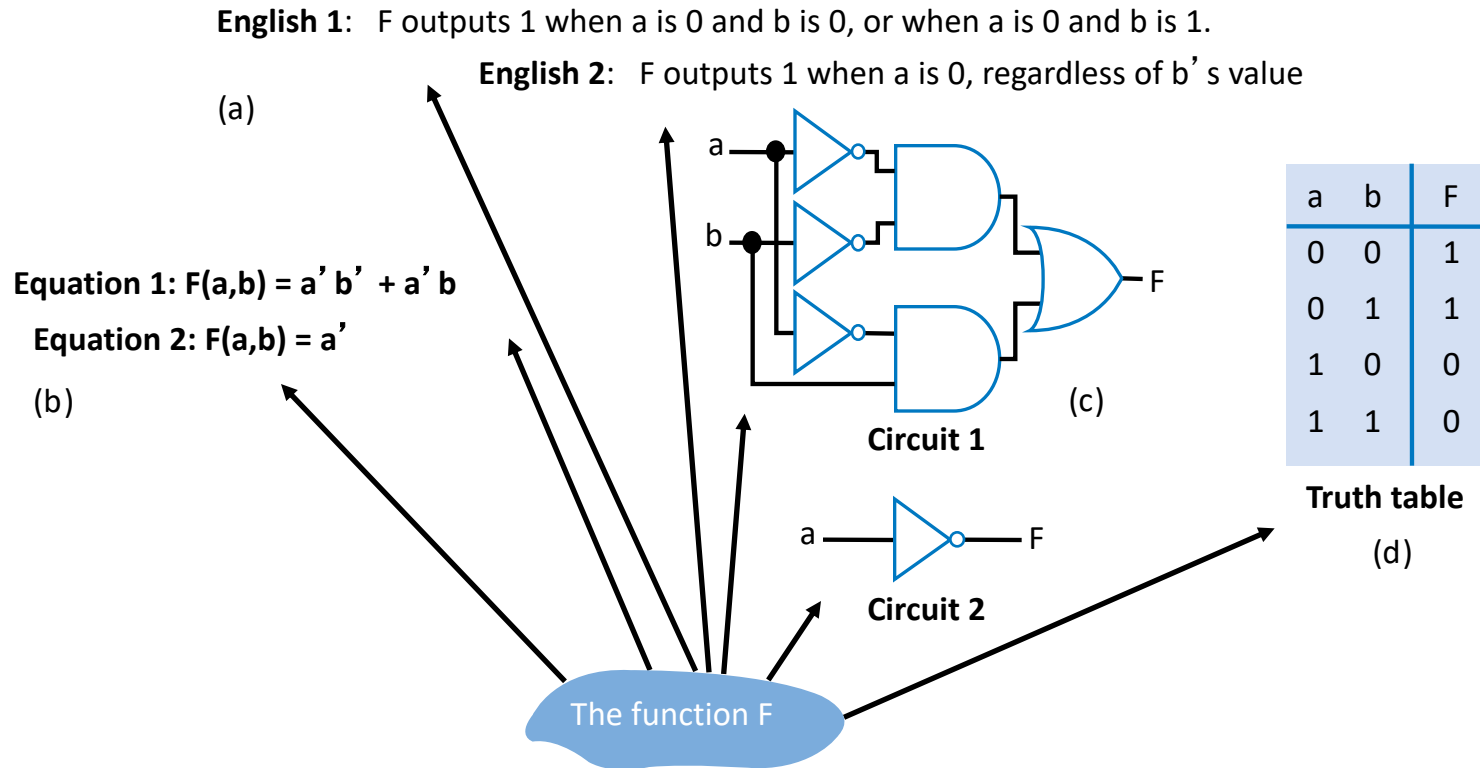

- A function can be represented in different ways
 - Above shows seven representations of the same functions $F(a,b)$, using four different methods: English, Equation, Circuit, and Truth Table



Truth Table Representation of Boolean Functions

- Define value of F for each possible combination of input values
 - 2-input function: 4 rows
 - 3-input function: 8 rows
 - 4-input function: 16 rows
- Q: Use truth table to define function $F(a,b,c)$ that is 1 when abc is 5 or greater in binary

a	b	F
0	0	
0	1	
1	0	
1	1	

(a)

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

a



a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

(c)




Converting among Representations

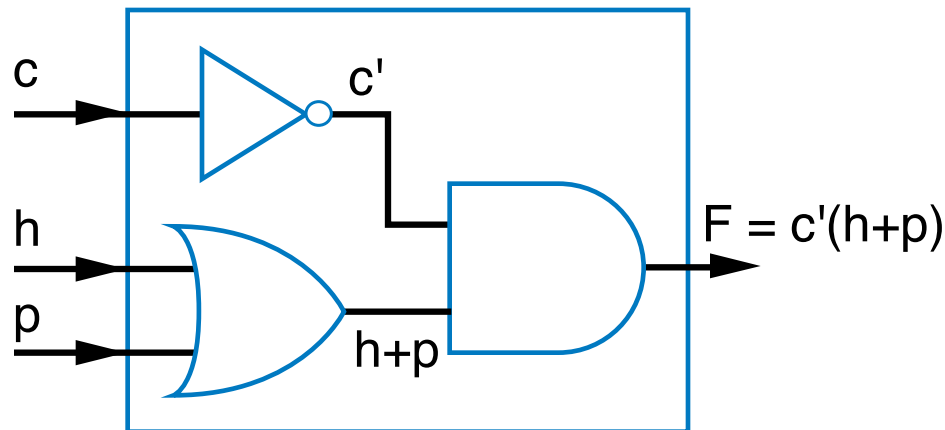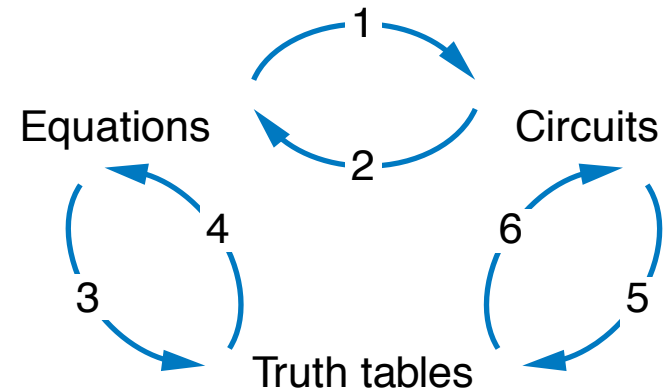- Can convert from any representation to another
- Common conversions
 - Equation to circuit (we did this earlier)
 - Circuit to equation
 - Start at inputs, write expression of each gate output



Converting among Representations

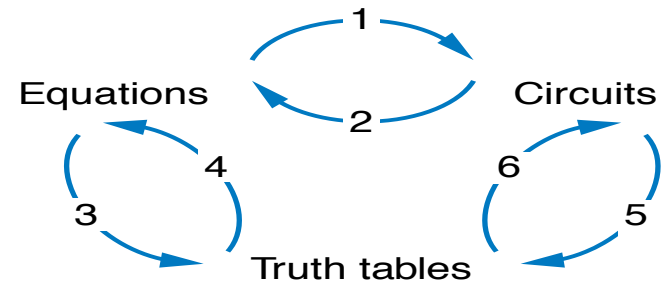

- Additional common conversions
 - Truth table to equation (which we can then convert to circuit)
 - Easy—just OR each input term that should output 1
 - Equation to truth table
 - Easy—just evaluate equation for each input combination (row)
 - Creating intermediate columns helps

Inputs		Outputs	Term
a	b	F	F = sum of
0	0	1	$a' b'$
0	1	1	$a' b$
1	0	0	
1	1	0	

$$F = a' b' + a' b$$

Q: Convert to equation

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$ab'c$
 abc'
 abc

$$F = ab'c + abc' + abc$$

Q: Convert to truth table: $F = a' b' + a' b$

Inputs				Output
a	b	$a' b'$	$a' b$	F
0	0	1	0	1
0	1	0	1	1
1	0	0	0	0
1	1	0	0	0



Example: Converting from Truth Table to Equation

- Parity bit
 - Extra bit added to data, intended to enable detection of error (a bit changed unintentionally)
 - e.g., errors can occur on wires due to electrical interference
- Even parity
 - Set parity bit so total number of 1s (data + parity) is even
 - e.g., if data is 001, parity bit is 1 → 0011 has even number of 1s
- Want equation, but easiest to start from truth table for this example

a	b	c	P	
0	0	0	0	(0 1s: even)
0	0	1	1	(2 1s: even)
0	1	0	1	
0	1	1	0	
1	0	0	1	
1	0	1	0	
1	1	0	0	
1	1	1	1	


Convert to equation

$$P = a'b'c + a'bc' + ab'c' + abc$$



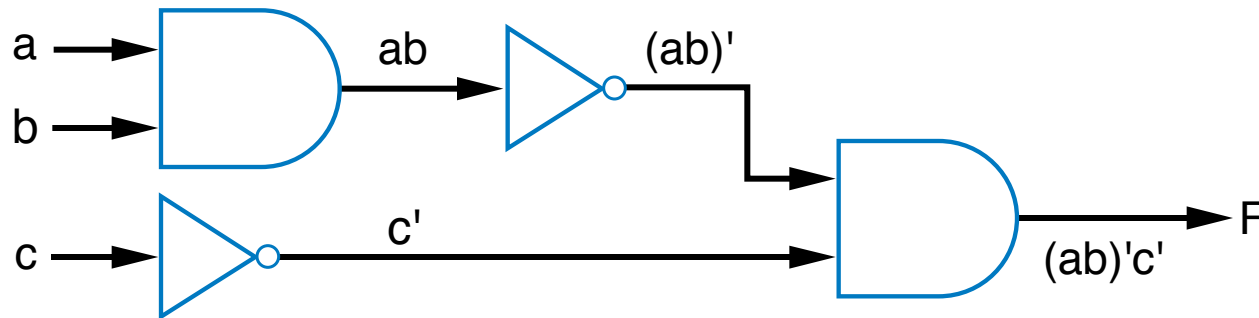Example: Converting from Circuit to Truth Table

- First convert to circuit to equation, then equation to table



Inputs						Outputs
a	b	c	ab	$(ab)'$	c'	F
0	0	0	0	1	1	1
0	0	1	0	1	0	0
0	1	0	0	1	1	1
0	1	1	0	1	0	0
1	0	0	0	1	1	1
1	0	1	0	1	0	0
1	1	0	1	0	1	0
1	1	1	1	0	0	0



Standard Representation: Truth Table

- How can we determine if two functions are the same?
 - Recall automatic door example
 - Same as $f = hc' + h'pc'$? $= ?$
 - Used algebraic methods
 - But if we failed, does that prove *not* equal? No.
- Solution: Convert to truth tables
 - Only ONE truth table representation of a given function
 - Standard** representation—for given function, only one version in standard form exists

$$f = c'hp + c'hp' + c'h'$$

$$f = c'h(p + p') + c'h'p$$

$$f = c'h(1) + c'h'p$$

$$f = c'h + c'h'p \text{ (what if we stopped here?)}$$

$$f = hc' + h'pc'$$

Q: Determine if $F = ab + a'$ is same function as $F = a'b' + a'b + ab$, by converting each to truth table first

F = ab + a'			F = a'b' + a'b + ab		
a	b	F	a	b	F
0	0	1	0	0	1
0	1	1	0	1	1
1	0	0	1	0	0
1	1	1	1	1	1

Same



Truth Table Canonical Form

- Q: Determine via truth tables whether $ab + a'$ and $(a+b)'$ are equivalent

$F = ab + a'$			$F = (a+b)'$		
a	b	F	a	b	F
0	0	1	0	0	1
0	1	1	0	1	0
1	0	0	1	0	0
1	1	1	1	1	0

Not equivalent



Canonical Form – Sum of Minterms

- Truth tables too big for numerous inputs
- Use standard form of equation instead
 - Known as **canonical form**
 - Regular algebra: group terms of polynomial by power
 - $ax^2 + bx + c$ ($3x^2 + 4x + 2x^2 + 3 + 1 \rightarrow 5x^2 + 4x + 4$)
 - Boolean algebra: create sum of minterms
 - **Minterm**: product term with every function literal appearing exactly once, in true or complemented form
 - Just multiply-out equation until sum of product terms
 - Then expand each term until all terms are minterms

Q: Determine if $F(a,b)=ab+a'$ is equivalent to $F(a,b)=a' b' +a' b+ab$, by converting first equation to canonical form (second already is)

$F = ab+a'$ (already sum of products)

a $F = ab + a' (b+b')$ (expanding term)

$F = ab + a' b + a' b'$ (Equivalent – same three terms as other equation)



Canonical Form – Sum of Minterms

- Q: Determine whether the functions $G(a,b,c,d,e) = abcd + a'bcde$ and $H(a,b,c,d,e) = abcde + abcde' + a'bcde + a'bcde(a' + c)$ are equivalent.

$$G = abcd + a'bcde$$

$$G = abcd(e+e') + a'bcde$$

$$G = abcde + abcde' + a'bcde$$

$$G = a'bcde + abcde' + abcde \quad (\text{sum of minterms form})$$

Equivalent

$$H = abcde + abcde' + a'bcde + a'bcde(a' + c)$$

$$H = abcde + abcde' + a'bcde + a'bcdea' + a'bcdec$$

$$H = abcde + abcde' + a'bcde + a'bcde + a'bcde$$

$$H = abcde + abcde' + a'bcde \quad (\text{last two terms were redundant})$$

$$H = a'bcde + abcde' + abcde$$




Compact Sum of Minterms Representation

- List each minterm as a number
- Number determined from the binary representation of its variables' values
 - $a'bcd$ corresponds to 01111, or 15
 - $abcde'$ corresponds to 11110, or 30
 - $abcde$ corresponds to 11111, or 31
- Thus, $H = a'bcd + abcde' + abcde$ can be written as:
 - $H = \sum m(15, 30, 31)$
 - "H is the sum of minterms 15, 30, and 31"




Multiple-Output Circuits

- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Ex: $F = \underline{ab} + c'$, $G = \underline{ab} + bc$

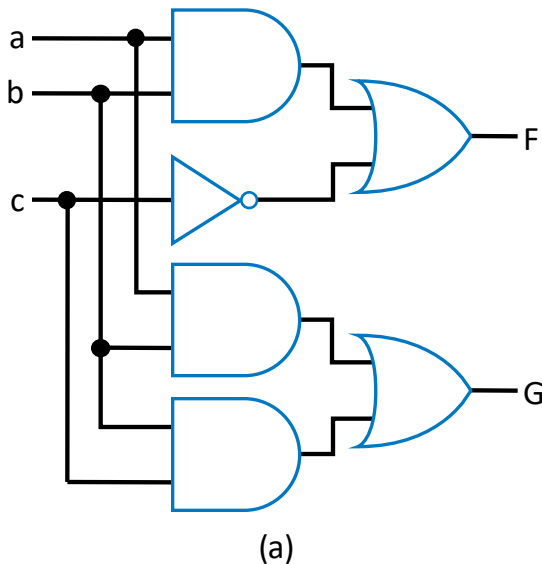



Option 1: Separate circuits

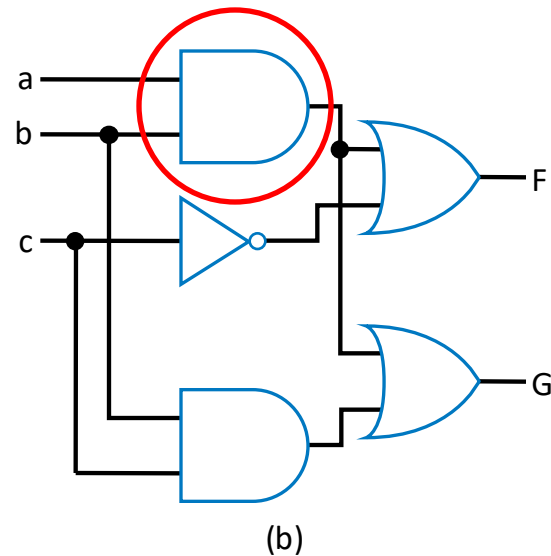

Option 2: Shared gates



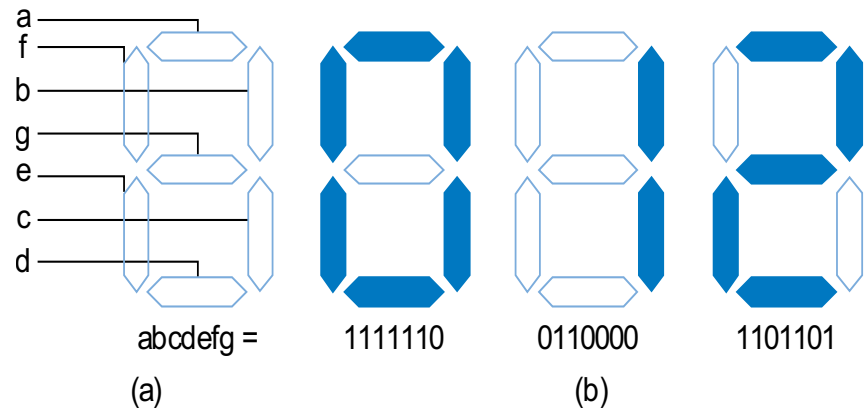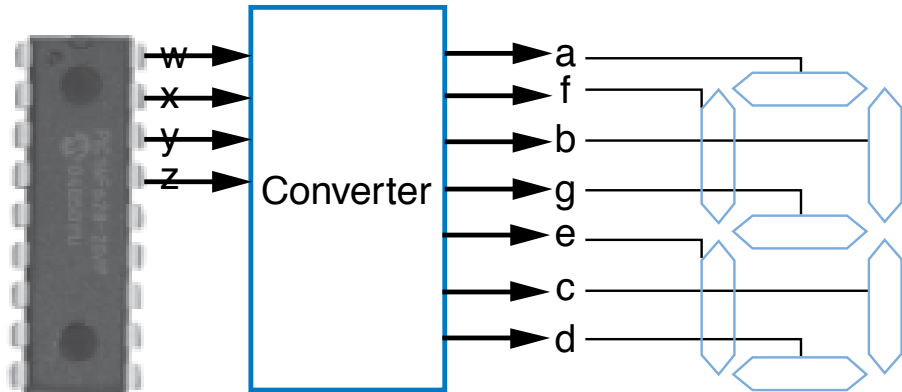
Multiple-Output Example: BCD to 7-Segment Converter



Multiple-Output Example: BCD to 7-Segment Converter

TABLE 2-4 4-bit binary number to seven-segment display truth table

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

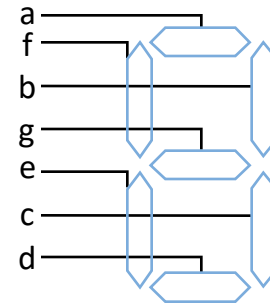


$$a = w'x'y'z' + w'x'yz' + w'x'yz + w'xy'z + w'xyz' + w'xyz + wx'y'z' + wx'y'z$$

$$b = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz + w'xy'z' + w'xyz + wx'y'z' + wx'y'z$$


...




More Gates

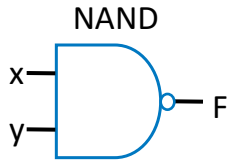


x	y	F
0	0	1
0	1	1
1	0	1
1	1	0

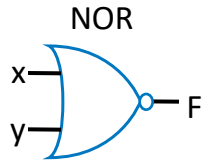

x	y	F
0	0	1
0	1	0
1	0	0
1	1	0

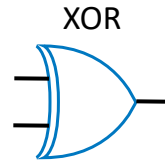

x	y	F
0	0	0
0	1	1
1	0	1
1	1	0

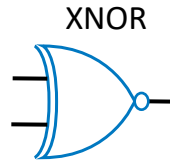

x	y	F
0	0	1
0	1	0
1	0	0
1	1	1


- NAND: Opposite of AND (“NOT AND”)
- NOR: Opposite of OR (“NOT OR”)
- XOR: Exactly 1 input is 1, for 2-input XOR. (For more inputs -- odd number of 1s)
- XNOR: Opposite of XOR (“NOT XOR”)



More Gates: Example Uses


- Aircraft lavatory sign example

- $S = (abc)'$

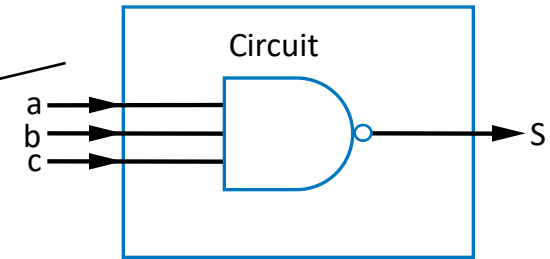


- Detecting all 0s

- Use NOR

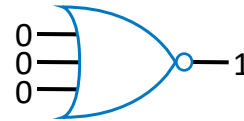

- Detecting equality

- Use XNOR

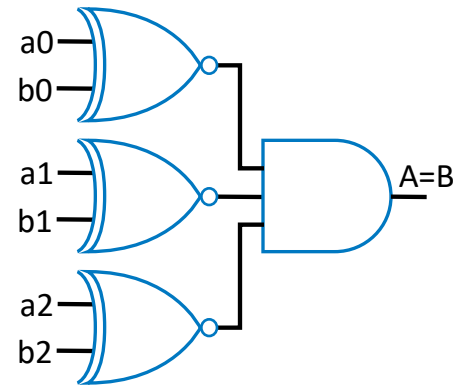

- Detecting odd # of 1s


- Use XOR

- Useful for generating “parity” bit common for detecting errors



Completeness of NAND

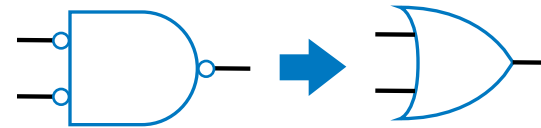- Any Boolean function can be implemented *using just NAND gates*. Why?
 - Need AND, OR, and NOT
 - NOT: 1-input NAND (or 2-input NAND with inputs tied together)
 - AND: NAND followed by NOT
 - OR: NAND preceded by NOTs
 - Thus, NAND is a universal gate
 - Can implement any circuit using just NAND gates
- Likewise for NOR



Number of Possible Boolean Functions

- How many possible functions of 2 variables?
 - 2^2 rows in truth table, 2 choices for each
 - $2^{(2^2)} = 2^4 = 16$ possible functions
- N variables
 - 2^N rows
 - $2^{(2^N)}$ possible functions



a	b	F
0	0	0 or 1 2 choices
0	1	0 or 1 2 choices
1	0	0 or 1 2 choices
1	1	0 or 1 2 choices

$2^4 = 16$
possible functions



a	b	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		0	a AND b		a	b		a XOR b	a OR b	a NOR b	a XNOR b	b'	a'		a NAND b		1







Venn Diagram: $A+B$

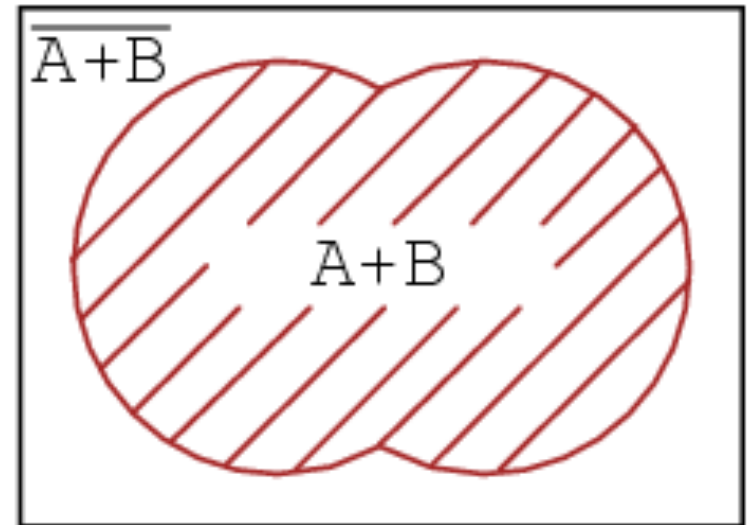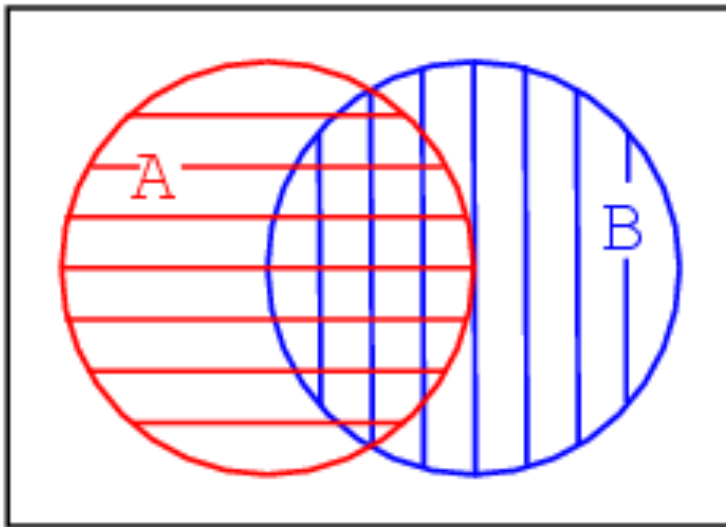




Venn Diagram: $A \cdot B$

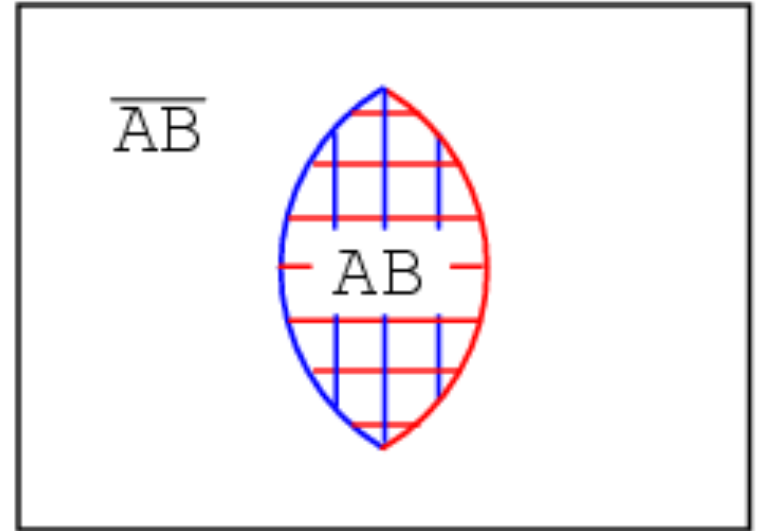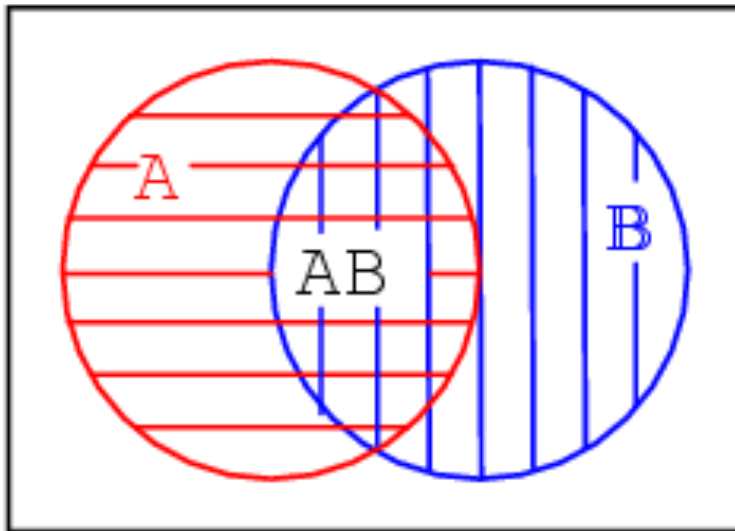


Venn Diagram: $A' B$

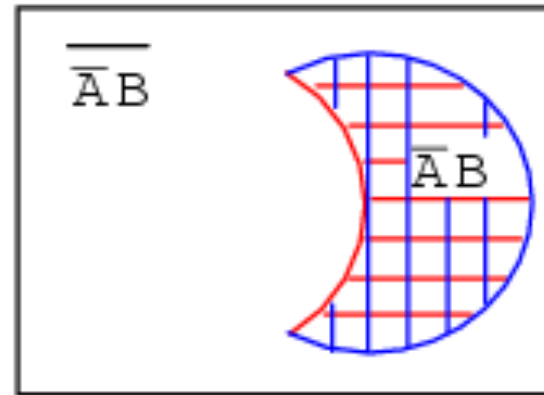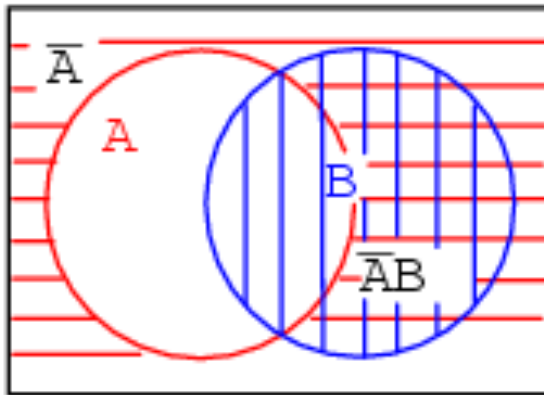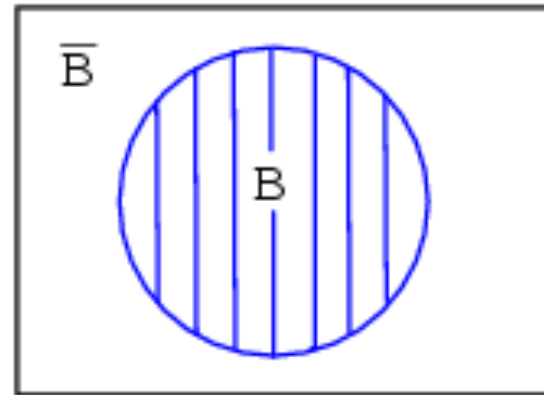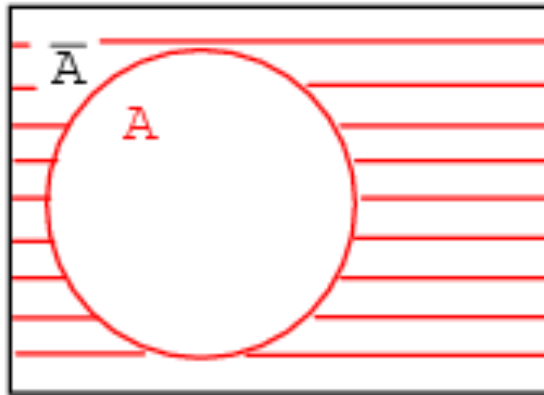




Venn Diagram: $A+B'$

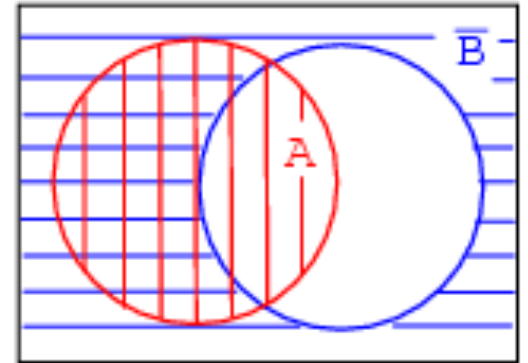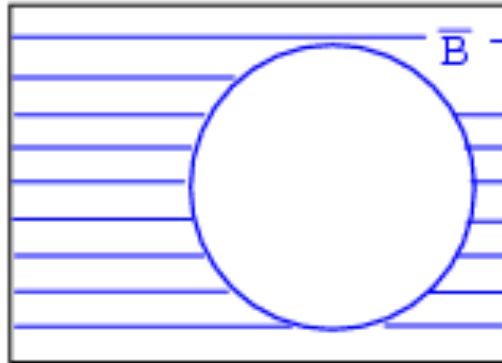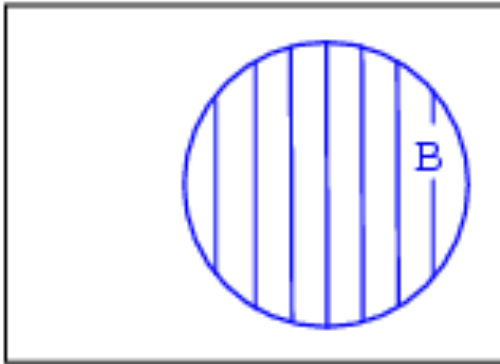




Venn Diagram: $(A+B')' = A' \cdot B$

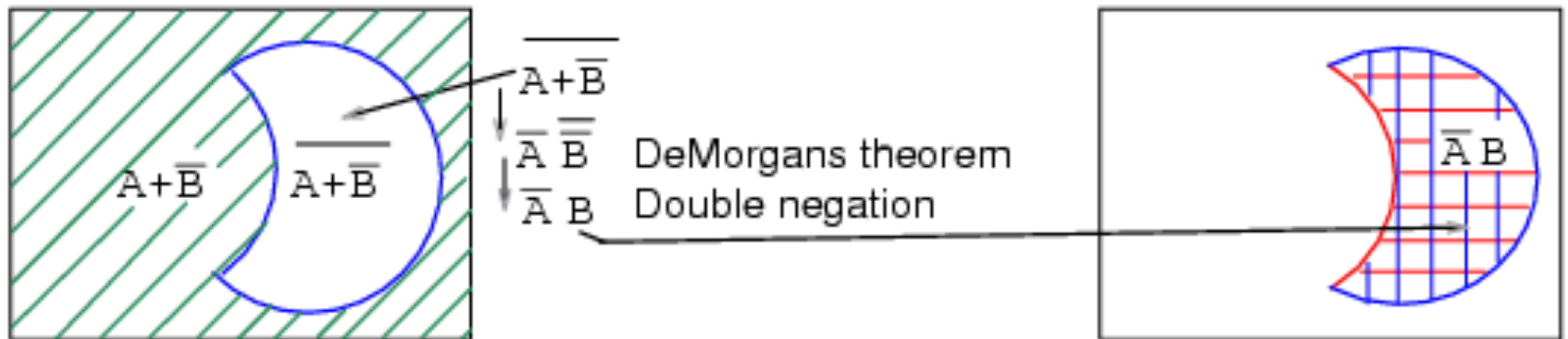

Venn Diagram: $A' + B' = ?$

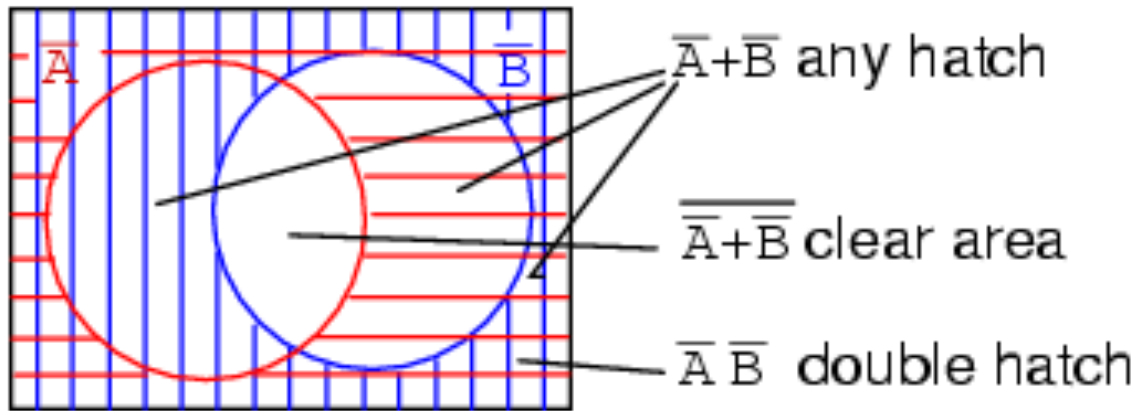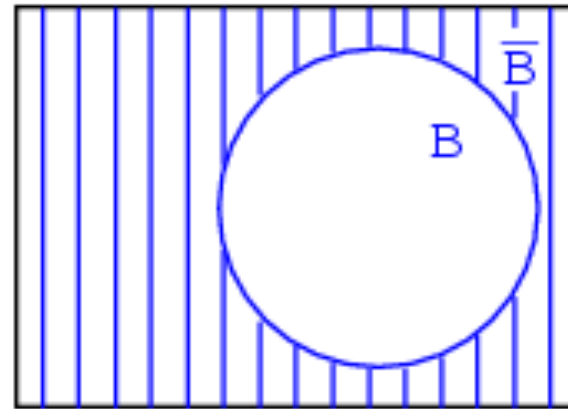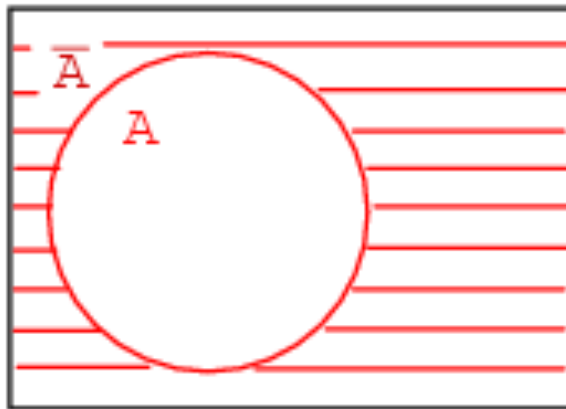

Venn Diagram: $A' + B' = (AB)'$

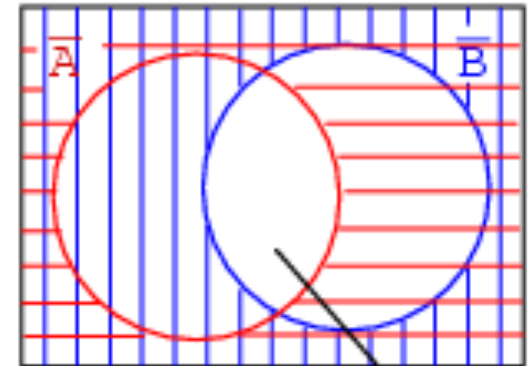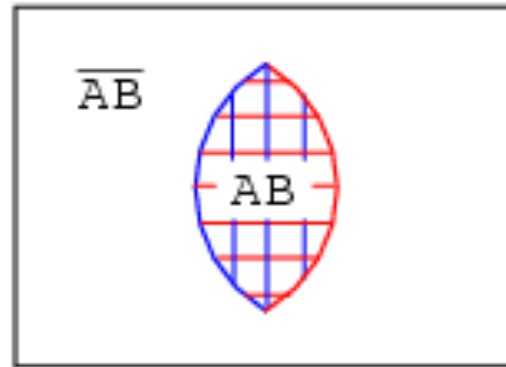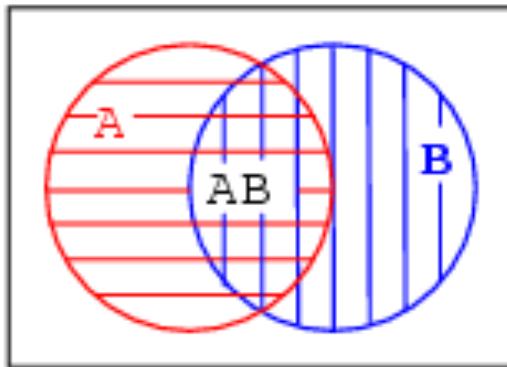

$$\overline{\overline{A+B}} \text{ no hatch}$$

$$\overline{\overline{A+B}} = \overline{\overline{A}} \overline{\overline{B}} = A B$$