

1.

$$\text{Find } L_m$$

$$L_m = \frac{N^2}{\left(\frac{1_m}{M_0 A} + \frac{1_s}{M_0 A}\right)} = \frac{40^2}{\frac{0.7 \times 10^{-3}}{(4\pi \times 10^{-7})(0.0001)}}$$

$$\underline{L_m = 37.98 \text{ m}}$$

2.

$$C = \frac{D}{R \cdot f \cdot \left(\frac{\Delta V_o}{V_o}\right)}$$

$$100 \times 10^{-6} = \frac{0.51}{8 \cdot (40 \times 10^3) (x)}$$

$$\frac{\Delta V_o}{V_o} = 0.0159$$

$$\underline{1.6010}$$

$$\text{Find } D.$$

$$D = \frac{V_o}{V_o + V_{in} (N^2 / N_1)}$$

$$= \frac{5}{5 + 24(\frac{1}{5})} = 0.51$$

$$D = 0.51$$

3. Find DF

$$DF = \frac{I_1}{I_{Rms}}$$

$$I_1 = \frac{10.1}{\sqrt{2}} = 7.14$$

$$I_{Rms} = \sqrt{\left(\frac{10.1}{\sqrt{2}}\right)^2 + (7.9/\sqrt{2})^2 + (6.9/\sqrt{2})^2 + (4/\sqrt{2})^2}$$

$$I_{Rms} = 10.6778$$

$$DF = \frac{7.14}{10.6778} = \underline{0.6686}$$

4.

$$V_d = V_{in} \frac{N^2}{N_1} + V_o$$

$$\rightarrow = 30 \left(\frac{1}{2}\right) + 12 = \underline{30} \quad \underline{N_d = 30}$$

$$\frac{V_o}{V_{in}} = \frac{D}{1-D} \cdot \frac{N^2}{N_1} \rightarrow V_o = \frac{D}{1-D} \cdot \frac{N^2}{N_1} \cdot V_{in}$$

$$12 = \frac{0.4}{1-0.4} \cdot \left(\frac{1}{2}\right) \cdot 30$$

$$V_{sw} = 30 + 12(2) = \underline{60} \quad \underline{V_{sw} = 60}$$

5. Find DF.

JOAQUIN SALAS 731000141

6.

$$PF = \frac{I_1}{I_{RMS}} \cos(\phi)$$
$$= \frac{11/\sqrt{2}}{I_{RMS}} \cos(34) = 0.575$$
$$I_{RMS} \quad PF = 0.5754$$

7.

$$L_m = \frac{N^2}{\left(\frac{\lambda_m}{M_0 A}\right) + \left(\frac{\lambda_g}{M_0 A}\right)} = \frac{N^2}{\frac{1 \times 10^{-3}}{(4\pi \times 10^{-7})(0.000007)}} = 71 \times 10^{-4}$$
$$\underline{N = 90}$$

8.

$$B = \frac{\Phi}{A}, \quad \Phi = \frac{N i}{\frac{\lambda_m}{M_0 A} + \frac{\lambda_g}{M_0 A}} = \frac{(234)(2)}{\frac{0.8 \times 10^{-3}}{(4\pi \times 10^{-7})(0.0001)}}$$
$$B = \frac{7.35 \times 10^{-5}}{0.0001} = 0.735 \quad \Phi = 7.35 \times 10^{-5}$$

9.

JOAQUIN SALAS 731000141

12. Find  $L_m$  for 77% output load

~~$L_m = P_o / f$~~

$$P_i = \frac{1}{2} \frac{V_i^2 D^2}{f L_m} = 7.7 = \frac{1}{2} \frac{(10^2)(0.25)^2}{(51000)(x)} = 3.125$$

$$7.7 = \frac{3.125}{(51000)(x)} \cdot 51000$$

$$392700 = \frac{3.125}{x}$$

$$2.5416 \times 10^{-6} = \frac{x}{3.125}$$

$$x = 7.96 \times 10^{-6}$$

13.

14.  $P = NI_1 \cos(\theta_1)$

$$= \left(\frac{170}{\sqrt{2}}\right) \left(\frac{14.6}{\sqrt{2}}\right) \cos(47) = 846.4$$

$$\underline{15.} \quad L_m = \frac{\frac{N_1^2}{1m}}{\frac{M_0 M_r A}{}} = \frac{\frac{214^2}{0.01}}{M_0 (9743) (0.0002)}$$

17.

$$\underline{18.} \quad C_d = \frac{P_{in}}{N_d^2 \cdot 2\pi \cdot \left(\frac{\Delta V_d}{V_d}\right)} = \frac{37.113}{(120^2) \cdot 2\pi (100) (x)} = 674 \times 10^{-6}$$

$$P_{in} = \frac{V^2}{R} = \frac{120^2}{388} = 37.113 \quad \frac{\Delta V_d}{V_d} = 0.01014$$


$$1.014$$

19. FIND  $N_d$

$$V_d = V_{in} \frac{N_d^2}{N_1} + V_o = 20 \left(\frac{1}{5}\right) + 9 = \underline{14.2V}$$

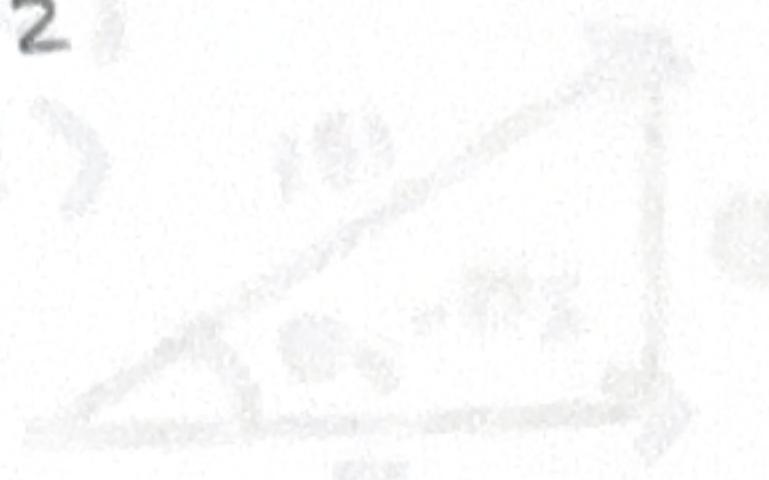20. FIND THD.

$$THD = \frac{\sqrt{I_3^2 + I_5^2}}{I_1}$$



5.  $P = \left(\frac{3.21}{\sqrt{2}}\right)(1.5)(0.76) = 258$

$$\cos(x) = 40$$

$$PF = DF \cdot DPF$$

$$0.76 = x (0.000)$$

20.  $\cos(x) = 45.57$

$$PF = \frac{I}{I_{RMS}} \quad \cos(45.57)$$

$$DF = \frac{I_1}{I_{RMS}}$$

17.

$$i_s = \sqrt{2} I_s \sin \omega t$$

13.

## Complex Power

$$V(t) = V_p \cos(\omega t + \theta_V)$$

$$i(t) = I_p \cos(\omega t + \theta_I)$$

$$\bar{V} = V_{RMS} \angle \theta_V$$


$$\bar{I} = I_{RMS} \angle \theta_I$$

S: Complex power (VA, kVA, MVA)

|SI|: Apparent Power (VA, kVA, MVA) =  $V_{RMS} \cdot I_{RMS}$

P: Real Power (W, kW, MW)

Q: Reactive Power (Var, kVar, MVar)

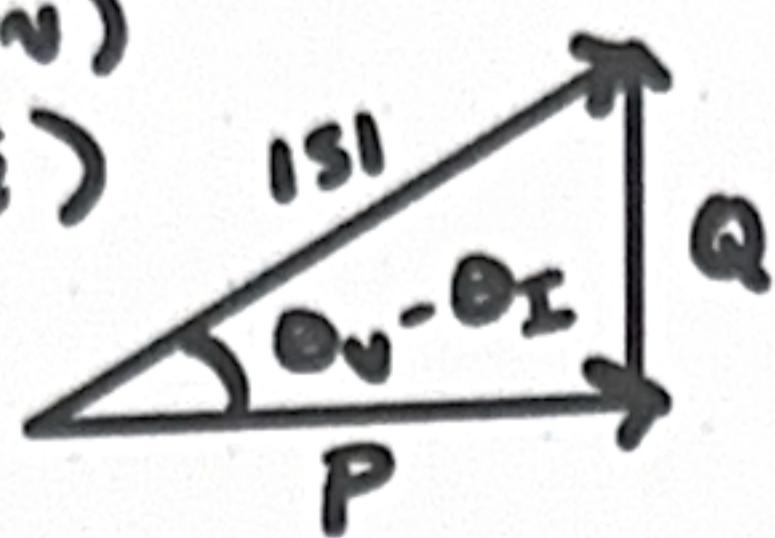

## POWER FACTOR / RMS

$$I = V/I_Z \quad PF = \cos(\phi)$$

$$PF = \frac{\text{REAL POWER}}{\text{APPARENT POWER}} = \frac{P}{V_{RMS} \cdot I_{RMS}} = \frac{P}{|SI|}$$

$$THD = \frac{\sqrt{I_3^2 + I_5^2}}{I_1} = \frac{\sqrt{I_{RMS}^2 \cdot I_1^2}}{I_1} = \sqrt{\frac{1}{DF^2} - 1}$$

$$DF = I_1/I_{RMS}, DPF = \cos(\theta_1)$$

## SINGLE PHASE PF CORRECTION

$$i_s = \frac{E \cdot I_s}{N_d} \cos 2\omega t$$

$$L = \frac{N_d}{4 \cdot f \cdot RF_L \cdot I_s}$$

w/ TRANSISTOR

$$V_d = \sqrt{2} \cdot E \sin \omega t$$

$$P_m = EI_s(1 - \cos 2\omega t)$$

$$i_s = \sqrt{2} I_s \sin \omega t \quad P_{out} = N_d \cdot I_d$$

## MAGNETIC CIRCUIT CONCEPTS

FLUX DENSITY -  $B = \Phi/A$  MAGNETIC FIELD STRENGTH -  $H = N \cdot i / l$

$$\phi = N \cdot i / (l/\mu \cdot A) \quad B = \mu H \quad \mu = \mu_0 \mu_r, \mu_r = 1 \text{ FOR AIR}$$

$$\text{WITH AN AIR GAP} \quad [\mu_0 = 4\pi \cdot 10^{-7}] \quad 1 \text{ cm}^2 = 0.0001 \text{ m}^2$$

$$\Phi = \frac{N_i}{\frac{l_m}{\mu_0 \mu_r A} + \frac{l_g}{\mu_0 A}} \quad \begin{array}{l} \text{lm-core} \\ \text{lg-gap} \end{array} \quad L_m = \lambda_m / i = N^2 / \left( \frac{l_m}{\mu_0 \mu_r A} + \frac{l_g}{\mu_0 A} \right)$$

$$i = \frac{H_m l_m}{N}$$

flux linkage -  $\lambda_m = N \cdot \Phi_m = L_m \cdot i$

$$L_m = \lambda_m / i = N^2 / \left( \frac{l_m}{\mu_0 \mu_r A} + \frac{l_g}{\mu_0 A} \right)$$

ENERGY STORED IN CORE -  $W_{core} = \frac{1}{2} \cdot B^2 / \mu_0 \mu_r$

$$W_{airgap} = \frac{1}{2} \cdot B^2 / \mu_0$$

## FLYBACK DC-DC CONVERTER

$$V_d = V_{in} \frac{N_2}{N_1} + V_o \quad V_{sw} = V_{in} + V_o \frac{N_1}{N_2}$$

$$\frac{V_o}{V_{in}} = \frac{D}{1-D} \cdot \frac{N_2}{N_1}$$

$$I_{offset} = \frac{I_o (N_2/N_1)}{1-D} \cdot I_{lm, peak} = I_{offset} + \frac{\alpha I_L}{2}$$

$$P = \frac{V_p I_p \cos(\phi)}{2} \quad V_{RMS} = V_p / \sqrt{2}$$

$$I_{RMS} = I_p / \sqrt{2}$$

$$Q = \frac{V_p I_p \sin(\phi)}{2} \quad \phi = \theta_V - \theta_I$$

## POWER TRIANGLE

$$S = \bar{V} \bar{I}^* = V_{RMS} I_{RMS} \angle (\theta_V - \theta_I)$$

$$S = \bar{V} \bar{I}^* = P + jQ$$

$$P = V_{RMS} I_{RMS} \cos(\phi) \quad [By LOAD]$$

$$Q = V_{RMS} I_{RMS} \sin(\phi)$$

$$\text{Given } V(t) = \sqrt{2} V \cdot \cos(\omega t) \quad V$$

$$i(t) = \sqrt{2} I_1 \cos(\omega t - \theta_1) + \sqrt{2} I_3 \cos(\omega t + \theta_3)$$

$$V_{RMS} = \sqrt{\left(\frac{V_1}{\sqrt{2}}\right)^2 + \left(\frac{V_3}{\sqrt{2}}\right)^2} \quad I_{RMS} = \sqrt{I_1^2 + I_2^2 + I_3^2}$$

$$P = V I \cos(\theta_1), |SI| = V \cdot I_{RMS}$$

$$PF = \frac{I_1}{I_{RMS}} \cdot \cos(\theta_1)$$

$$C_d = \frac{P_{in}}{V_d^2 \cdot 2\omega \cdot \left(\frac{m}{M}\right)} \quad E_d = \frac{P_{in}}{4\omega \cdot \left(\frac{m}{M}\right) \cdot V_d^2}$$

$$RF_L = \Delta I_{L, \max} / I_s$$

$$E_d = (1/2) C_d V_d^2$$

$$\text{Two-Winding Transformer} \quad I_m = \frac{V_1}{\omega L_m} \quad L_m = \frac{\mu V_1^2 A_m}{I_m}$$

$$I_{peak} = \sqrt{i_1^2 + I_m^2}$$

$$1 \text{ cm}^2 = 0.0001 \text{ m}^2$$

$$1 \text{ cm}^2 = 0.0001 \text{ m}^2$$