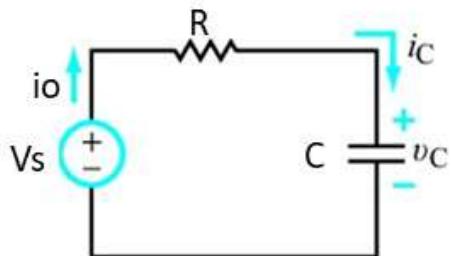


214Final Exam

- 1) In zyBooks exercises 5.6.8 --10 a circuit is given along with different input voltages for each problem, and you are asked to solve for the current. Repeat this for the circuit and input voltage shown below. Be sure to write down and label all the equations needed to arrive at the solution. Hint: In class I showed you a simpler way to get the answer without using an integrating factor.

• Use Mesh to get the Differential Equation

KCL MESH




$$RC \frac{dvc}{dt} + vc = Vs$$

$$\frac{dvc}{dt} + \frac{1}{RC} vc = \frac{Vs}{RC} \quad \text{and} \quad \tau = RC$$

$$Vs = -\alpha t, \quad \alpha = \alpha R$$

$$\frac{dvc}{dt} + \frac{v}{\tau} = -\frac{\alpha}{\tau} t \quad \left. \begin{array}{l} b + b \frac{t}{\tau} - b \frac{t_0}{\tau} = \frac{\alpha}{\tau} t \\ b = \frac{\alpha}{\tau} t_0, \quad t_0 = \tau \end{array} \right\} \quad v_c = \frac{\alpha}{\tau} t^2 \left(\frac{t}{\tau} - 1 \right)$$

Driver Part $i_d = b(t - t_0)$

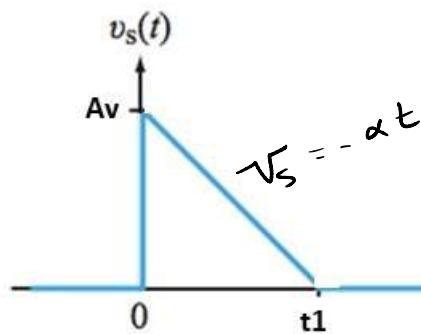

$$\text{Initial } i_L = 0 = i_d(0) + i_{\text{trans}}$$

$$i_L = -\frac{\alpha}{\tau} t^2 \quad i_L(0) = \frac{dv}{dt} = C \cdot \left(-\frac{Av}{\tau} \right)$$

$$i_d = -\frac{Av}{t} C t^2 \left(\frac{t}{\tau} - 1 \right)$$

$$v_c = e^{-t/\tau} \int \frac{e^{t/\tau}}{RC} vs dt$$

$$v(t) = v(0) e^{-t/\tau} + v(\infty) (1 - e^{-t/\tau})$$

$$v_c = Vs (1 - e^{-t/\tau})$$


$$\frac{dvc}{dt} + \frac{vc}{RC} = 0, \quad v_c(0) = Vs$$

$$v_c(t) = Vs e^{-t/\tau}$$

$$C \frac{dv}{dt} \downarrow \quad i = C \frac{dv}{dt}$$

214 Hemmer sections – Final exam -- Name _____

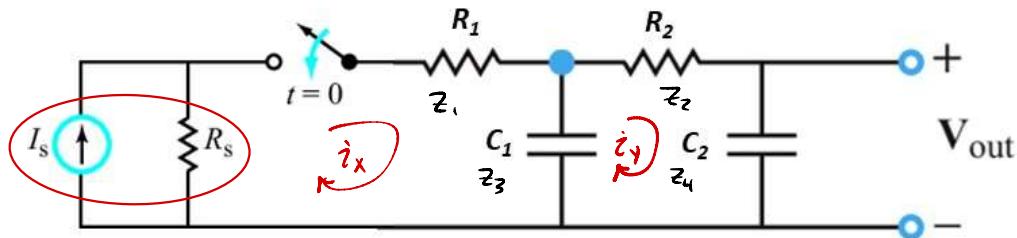- 2) In zyBooks exercises 6.10.5 – 11 a circuit is given, and you are asked to develop the differential equation for one of the currents or voltages in the circuit. Do the same for the output voltage in the circuit below. Be sure to write down and label all the equations needed to arrive at the solution.



$$\text{KCL} \quad \frac{V_1 - V_s}{R_s + R_1} + \frac{V_1 - V_2}{R_2} + V_1' C_1 = 0 \quad (1)$$

$$\left\{ \begin{array}{l} V_2 = V_i (-L_1 R_1 - L_1 R_3) + V_2' (-C_2 R_1 - C_2 R_2 - C_2 R_3) + V_s \\ V_2' = V_i'' (-L_1 R_1 - L_1 R_3) + V_2'' (-C_2 R_1 - C_2 R_2 - C_2 R_3) \end{array} \right.$$

$$V_s = I_s R_s \quad \text{Ohm's law}$$

$$\frac{V_2 - V_1}{R_2} + V_2' C_2 = 0 \quad (2)$$

$$R_2 \cdot \frac{V_2 - V_1}{R_2} = -V_2' C_2 \cdot R_2$$

$$V_2 - V_1 = -V_2' C_2 R_2$$

$$V_1 = V_2' C_2 R_2 + V_2 \quad -2$$

Plug V_2 & V_2' into N1

$$V_A = C_2 R_2 \left(\frac{C_1 V_2'' R_2 R_3 + C_1 V_2' R_2 R_3 + R_1 V_1 - R_2 V_s + R_2 V_1}{R_1 + R_2} \right) + \left(\frac{C_1 V_1 R_2 R_3 + C_1 V_1' R_2 R_3 + R_1 V_1 - R_2 V_s + R_2 V_1}{R_1 + R_2} \right)$$


Solve for V_{out} which is V_{out} w/ V_2 in this Circuit

$$= V_i'' = C_2 V_2'' R_2 + V_2' \rightarrow V_1' = -\frac{C_2 V_2' R_1 - C_2 V_2' R_2 - C_2 V_2' R_3 - V_2 + V_s}{C_1 R_1 + C_2 R_2} = C_2 V_2'' R_2 + V_2'$$

$$V_{out} = C_2 R_2 V_2'' + V_2'$$

214 Hemmer sections – Final exam -- Name _____

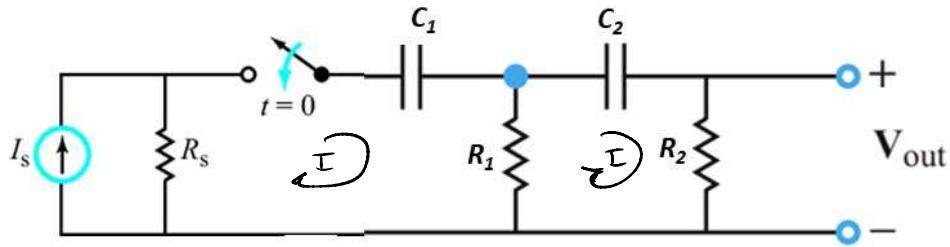- 3) In zyBooks exercises 6.10.4 – 7 a circuit is given, and you are asked to find the initial values of voltage and current on one or more of the elements. Do the same for both capacitors in the circuit below. Be sure to write down and label all the equations needed to arrive at the solution.



$$V_{C_1}(0^-) = 0$$

$$V_{C_1}(0^-) = V_{C_1}(0^+) = 0$$

$$V_{C_2}(0^-) = V_{C_2}(0^+) = 0$$

$$\text{First, } I_c = I_{R_1} + I_{C_2}$$


$$R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$\dot{I}_{C_1}(0) = \frac{V_s}{R_s + R_1 \parallel R_2}$$

$$\dot{I}_{C_2}(0) = \dot{I}_{C_1}(0) \cdot \frac{R_1}{R_1 + R_2}$$


214 Hemmer sections – Final exam -- Name _____

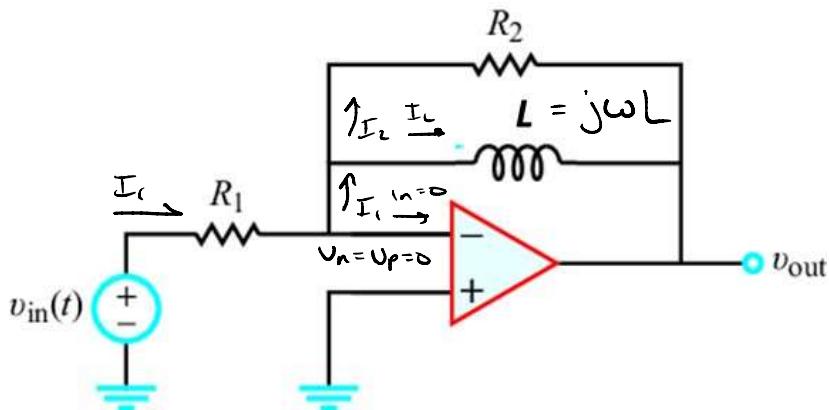- 4) In zyBooks exercises 7.12.2 – 5 you are asked to find the output voltage of a circuit as a function of the input voltage. Do the same for the circuit below. Be sure to write down and label all the equations needed to arrive at the solution.



$$\begin{aligned}
 V_{in} &= V_{in}(t), \quad I_1 = \frac{V_{in}}{R_1}, \quad I_1 = I_2 + I_L \quad L = j\omega L \\
 \frac{V_n - V_{out}}{R_2} + \frac{V_n - V_{out}}{j\omega L} &= -V_{out} \left(\frac{1}{R_2} + j\omega L \right) \\
 \text{So, } V_{out} &= - \left(\frac{R_2}{R_1} \right) \left(\frac{1}{1 + j\omega R_2 L} \right) V_{in} \\
 &= - \left(\frac{R_2}{R_1} \right) \frac{1 - j\omega R_2 L}{1 + \omega^2 R_2^2 L^2} V_{in}
 \end{aligned}$$

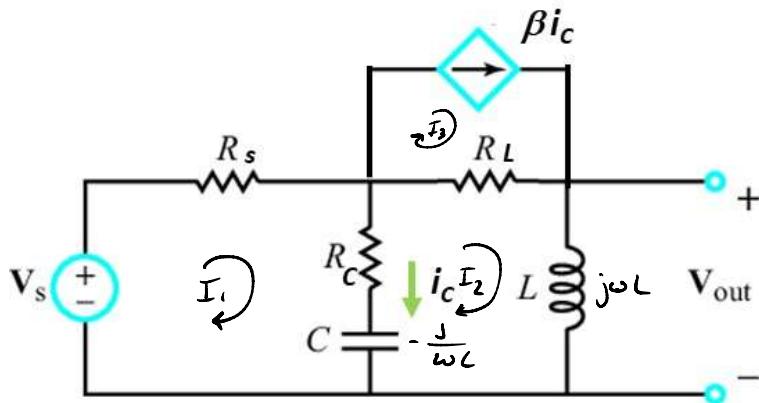- 5) In zyBooks exercises 7.10.5 -- 11 you are asked to find one of the currents or voltages in a circuit. Do the same for V_{out} in the circuit below. Be sure to write down and label all the equations needed to arrive at the solution.



Using Mesh Analysis to get an expression for phasor V_{out} in terms of V_s and R , we know that

$$R = \omega L = 1/\omega C$$

$$\text{First, } -V_s + RI_1 + \left(R - \frac{j}{\omega C}\right)(I_1 - I_2) = 0$$

$$\left(R - \frac{j}{\omega C}\right)(I_2 - I_1) + j\omega LI_2 = 0$$

$$R_L \beta I_c = 0$$

$$\text{use } R = \omega L = \frac{1}{\omega C}$$

$$-V_s + RI_1 + (R - jR)(I_1 - I_2) = 0$$

$$(R - jR)(I_2 - I_1) + jRI_2 = 0$$

$$\text{Simplify, } I_1(2 - j1) - I_2(1 - j1) = \frac{V_s}{R} \quad \textcircled{1}$$

$$-I_1(1 - j1) + I_2 = 0 \quad \textcircled{2}$$


$$I_2 + R_L \beta I_c = 0 \quad \textcircled{3}$$

$$V_{out} = j\omega L I_2 = jR I_2.$$

214 Hemmer sections – Final exam -- Name _____

Extra credit) The dual op amp circuit below has two outputs v_{o1} and v_{o2} . Note that the first op amp has positive feedback and so is saturated to $+V_{cc}$ or $-V_{cc}$. Because of this the two input voltages, v_{n1} and v_{p1} , are not necessarily equal. Begin with $V_{s1}=0$.

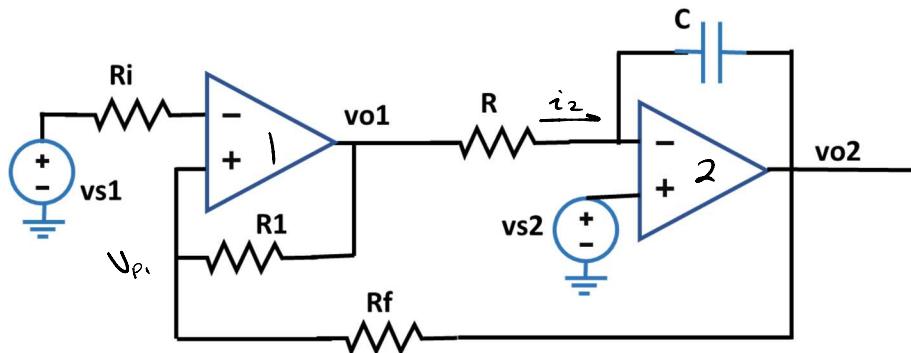- How does v_{o2} depend on V_{s2} for each value of v_{o1} ?
- If V_{s1} is not zero, how does the maximum value of v_{o2} depend on V_{s1} ? Note there will be two answers, one for negative and one for positive output voltages.



Op amp 2 - Integrator

$$v_{o2} = v(0) - \int_0^t i_2 dt \frac{1}{C}$$

$$= v(0) - \frac{v_{o1}}{RC} t$$

$$(a) +V = v_{p2} > v_{n2}, -V = v_{p2} < v_{n2}$$

$$(b) \frac{R_f}{R} (v_{o1} - v_{s1}) \text{ AND } \frac{R_f}{R} (v_{o1} + v_{s1})$$

$$\text{Node } v_{p1} \quad \frac{v_{p1} - v_{o1}}{R_i} + \frac{v_{p1} - v_{o2}}{R_f} = 0$$

$$\frac{R_f}{R} (v_{o1} + v_{s1})$$

Starting at $t=0, v_{o1} = V_{cc}, v_{o2} = 0$

$$v_{o2} = -V_{cc} \frac{t}{\tau} \text{ AND } \tau = RC = v_{p1} = (R_i || R_f) \left(\frac{V_{cc}}{R_i} - \frac{V_{cc}}{R_f} \frac{t}{\tau} \right)$$

$$\frac{t}{\tau} = \frac{R_f}{R_i} \rightarrow v_{o1} \rightarrow -V_{cc} \rightarrow v_{o2} = -\frac{V_{cc}}{\tau} \left(t \frac{R_f}{R_i} \right) + \frac{V_{cc}}{\tau} t$$

$$v_{o2} = v(0) - \frac{v_{o1}}{RC} t = -\frac{V_{cc}}{\tau} t$$

$$v_{p1} @ t_1 = \tau \left(\frac{R_f}{R_i} \right), v_{o2}(t_1) = -\frac{V_{cc}}{\tau} \tau \left(\frac{R_f}{R_i} \right), v_{o1}(t-t_1) = -V_{cc}$$

$$v_{o2}(t > t_1) = -V_{cc} \left(\frac{R_f}{R_i} \right) + V_{cc} \frac{t}{\tau}$$