

I-1 (10 pts) 2 points each part.

True (T) or False (F). One point each. Circle your selected response.

Respond to the statements as written. Do not edit them before responding.

- 1) Amplifier power gain G_P is defined in decibels as $10 \log_{10} (G_P)$. 1) ☒ T or F
- 2) A passive high-pass RC filter has a voltage gain of +3 dB at its break frequency. 2) T or ☒ F
- 3) For the 741 IC op amp, unity gain bandwidth f_t is the product of its DC gain A_o and its 3-dB break frequency f_B . 3) ☒ T or F

Multiple choice. Circle your response.

- 4) The conductivity of silicon can be increased by introducing into it an appropriate impurity element in a process called:
- a) drift ☒ b) doping c) diffusion d) biasing
- 5) Silicon and germanium are elemental semiconductors. By contrast, GaAs is a _____ semiconductor.
- a) bipolar b) doped ☒ c) compound d) type IV


I-2 (10 pts)

- a) A single time constant RC low pass filter is to have a break frequency of 10 [kHz]. Calculate the required value of capacitance C if a 10 [k Ω] resistor is to be used.
- b) Draw a schematic for this filter. Label V_{in} , V_{out} and both components with values.

a) $C = 1.59 \text{ nF}$


b) schematic

Please do not mark in this box ==>>>

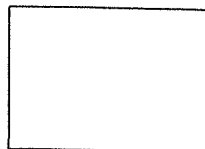

I-3 (10 pts)

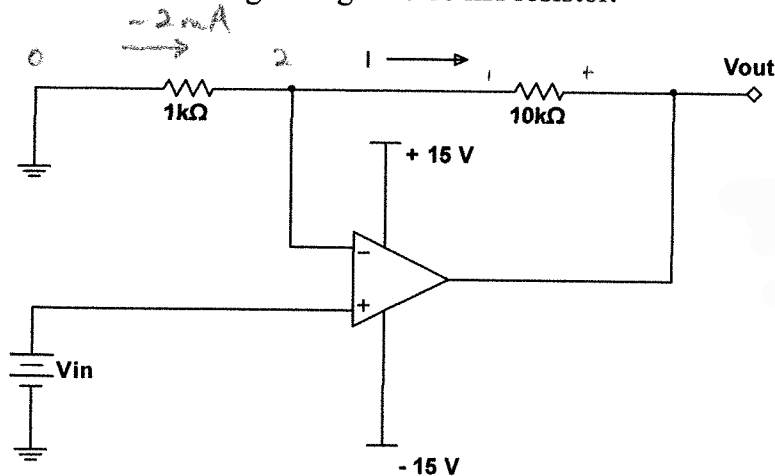For the circuit shown, $V_{in} = 2$ [V]. Assuming an ideal op amp, calculate the values of V_{out} and the current I flowing through the $10\text{ k}\Omega$ resistor.




$$V_{out} = 15 \text{ [V]}$$

$$I = -1.3 \text{ [mA]}$$

I-4 (10 pts)

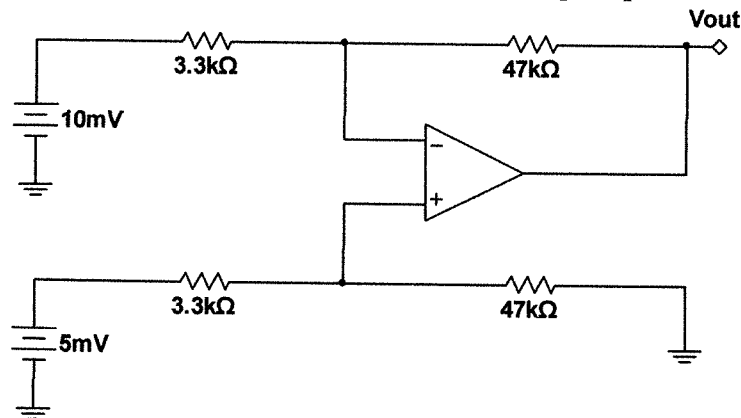Calculate the value of V_{out} in the circuit below. Assume an ideal op amp.




$$V_{out} = \left(\frac{47}{3.3} \right) (5 - 10) \text{ [mV]}$$

$$= 14.24 (-5)$$

$$V_{out} = -71.2 \text{ [mV]}$$

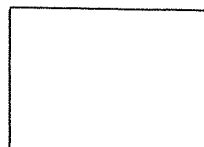Please do not mark in this box $\Rightarrow \Rightarrow$



II-1 (30 pts)

Consider a circuit consisting of these three parts connected in cascade: 1) a power supply with a Thevenin equivalent model of 1.0 [mVDC] and $100\ \Omega$; 2) a voltage amplifier with input resistance of $5\ \text{M}\Omega$, open loop voltage gain A_v of 55 dB, and output resistance of $75\ \Omega$; 3) a load resistor of $3\ \text{k}\Omega$.

- Draw a clearly labeled schematic of this complete circuit. Use a voltage-controlled voltage source in the amplifier stage. Label every component with its value.
- Calculate the closed loop voltage gain G_v in [dB].
- Calculate the current gain G_i in [dB].
- Calculate the power delivered by the supply.
- Calculate the power delivered to the load resistor.
- Calculate the power gain G_P in [dB].

Note: All gains assume a comparison of load value to respective power supply value.

a) schematic

b) $G_v = 54.8\ \text{dB}$

c) $G_i = 119\ \text{dB}$

*d) $P_S = 200\ \text{fW}$

e) $P_L = 100\ \mu\text{W}$

f) $G_P = 87.0\ \text{dB}$

$\times 2 (10^{-13})$
 $.2\ \text{pW}$


Please do not mark in this box =====>>



II-2 (30 pts)

In the circuit below both op amps are ideal.

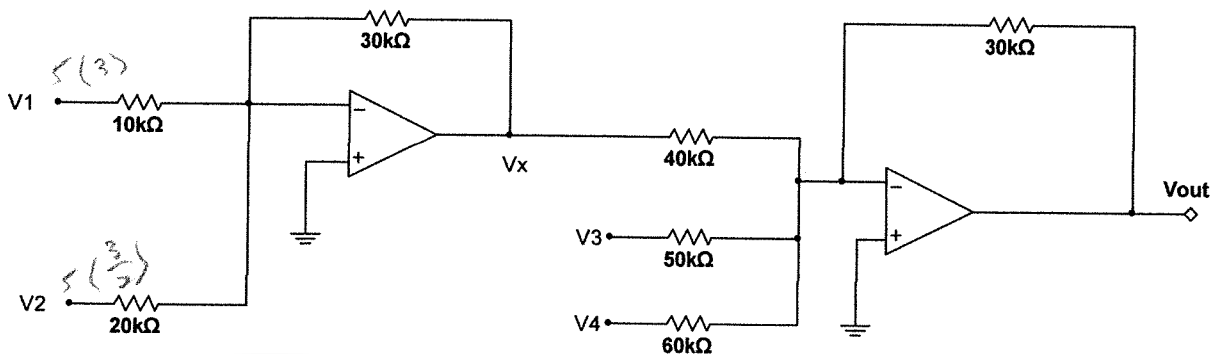- Find V_x in terms of V_1 and V_2 . Box your answer.
- Find V_{out} in terms of V_x , V_3 , and V_4 . Box your answer.
- Let $V_1 = V_2 = 5$ [mV], and $V_3 = V_4 = 4$ [mV]. Find the value of V_{out} .



a) Box answer

b) Box answer

c) $V_{out} = 12.5$ mV

Please do not mark in this box $\Rightarrow \Rightarrow$

