


Lecture # 11

# ECEN 438/738 Power Electronics


Spring 2025 Semester



**Dr. Prasad Enjeti,**  
Electrical & Computer Engineering  
Texas A&M University  
<http://enjeti.tamu.edu>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

## ECEN 438/738 Power Electronics

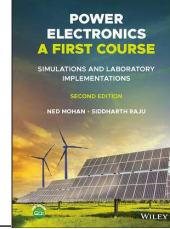

### Power Electronics A First Course: 2<sup>nd</sup> Edition

Free Textbook Online Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

## Chapter 5 RECTIFICATION OF UTILITY INPUT USING DIODE RECTIFIERS

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu


## ECEN 438/738 Power Electronics

Free Textbook Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

**O'REILLY** Explore Skills Start Learning Featured

Power Electronics, A First Course, 2nd Edition

WILEY

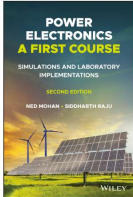

TIME TO COMPLETE: 9h, 47m  
LEVEL: Beginner  
COURSE: Electrical Engineering  
PUBLISHED BY: WILEY  
PUBLICATION DATE: January 2023  
PAGE LENGTH: 352 pages  
Add to playlist

Power Electronics, A First Course, 2nd Edition

WILEY

94% of book complete

Cover: 100% complete

Title Page: 100% complete

Copyright: 100% complete

Dedication: 100% complete

LIST OF SIMULATION AND HARDWARE IMPLEMENTATION EXAMPLES AND FIGURES: 100% complete

PREFACE: 100% complete

ACKNOWLEDGMENT: 100% complete

ABOUT THE COMPANION WEBSITE: 100% complete

CHAPTER 1 POWER ELECTRONICS: AN EMERGING TECHNOLOGY: 100% complete

**Click Here to Access Book Chapters online and Download**


Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

## Total Harmonics - THD - PF - DF

$v(t) = \sqrt{2}V \sin(\omega t)$  Volts

$i(t) = \sqrt{2}I_1 \sin(\omega t - \phi_1) + \sqrt{2}I_3 \sin(3\omega t + \phi_3) + \sqrt{2}I_5 \sin(5\omega t + \phi_5)$  Amps

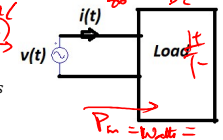*Handwritten notes:* (170V, 60Hz), (240V, 180Hz), Harm



$P_{in} = W_{del} =$

$THD = \frac{\text{rms of the harmonic components}}{\text{rms of the fundamental component}}$

*Handwritten:*  $DF = \frac{I_1}{I_{rms}}$

Note:  $I_{rms} = \sqrt{I_1^2 + I_3^2 + I_5^2}$  Therefore rms of the harmonic components =  $\sqrt{I_3^2 + I_5^2}$

Not:  $\sqrt{I_3^2 + I_5^2} = \sqrt{I_{rms}^2 - I_1^2}$

Therefore  $THD = \frac{\sqrt{I_3^2 + I_5^2}}{I_1} = \frac{\sqrt{I_{rms}^2 - I_1^2}}{I_1} = \frac{\sqrt{I_{rms}^2}}{I_1} - 1 = \frac{1}{DF} - 1$

**$THD = \sqrt{\frac{1}{DF^2} - 1}$**

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

## Single Phase Diode Rectifier

Note: as C increases  $\alpha$  decreases and  $\Delta V_o$  decreases

The RC discharge equation is  $v_o(t) = V_m * e^{-\frac{t}{RC}}$

Also note that input current flows ONLY when diodes conduct i.e. power is supplied during the conduction  $\alpha$  only


Now  $v_x(t) = V_m * e^{\frac{t}{RC}}$  As C is large  $t_1 \rightarrow \frac{\pi}{\omega}$

Therefore  $V_x = V_m * e^{-\frac{\pi}{\omega RC}}$

$$\Delta V_o = V_m - V_x = V_m - V_m * e^{-\frac{\pi}{\omega RC}} = V_m (1 - e^{-\frac{\pi}{\omega RC}})$$


From Math,  $e^{-\frac{\pi}{\omega RC}} \approx 1 - \frac{\pi}{\omega RC}$

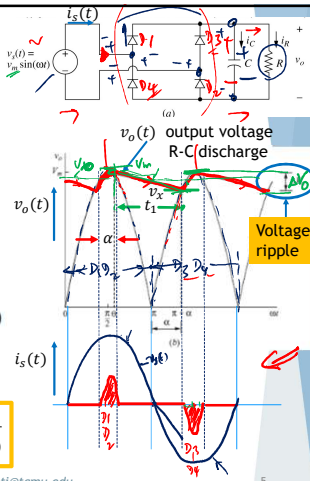Therefore  $\Delta V_o \approx \frac{V_m \pi}{\omega RC} = \frac{V_m}{2fRC}$  and  $C = \frac{1}{2 * f * R * (\frac{\Delta V_o}{V_m})}$


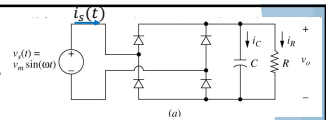
## Single Phase Diode Rectifier

For a single phase diode rectifier shown in figure,  $v_s = 120 \text{ V (rms)}$   
 $R = 500 \text{ ohms}$ ,  $C = 100 \text{ uF}$ , a) Calculate the voltage ripple b) Find the capacitance C to limit the voltage ripple to 1%



Note  $C = \frac{1}{2 * f * R * (\frac{\Delta V_o}{V_m})}$

a) Voltage ripple  $\frac{\Delta V_o}{V_m} = 0.167$  or 16.7%

b) For a voltage ripple  $\frac{\Delta V_o}{V_m} = 0.01$ , we have  $C = 1670 \text{ uF}$


## Attendance



## Current Sensor

## Single Phase Diode Rectifier

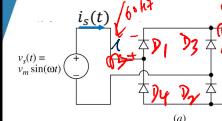
Example:  $V_s = 120 \text{ rms}$ ,  
 $R = 500 \text{ ohms}$ ,  $C = 100 \text{ uF}$   
 $RF = 0.167$  or 16.7%







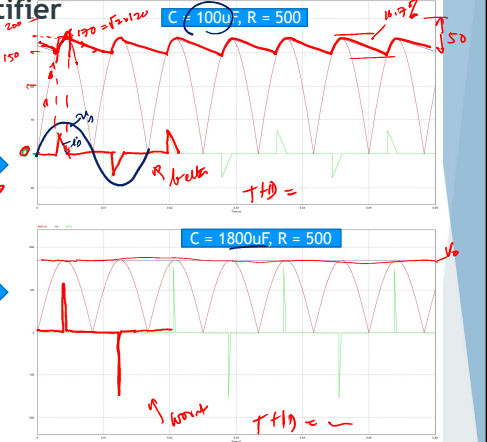
Example:  $V_s = 120 \text{ rms}$ ,  
 $R = 500 \text{ ohms}$ ,  $C = 1800 \text{ uF}$   
 $RF = 0.01$  or 1%

Note: As C is increased RF decreases.  
 However input current peak increases & quality deteriorates


Solution: Add an Inductor to limit the current peak




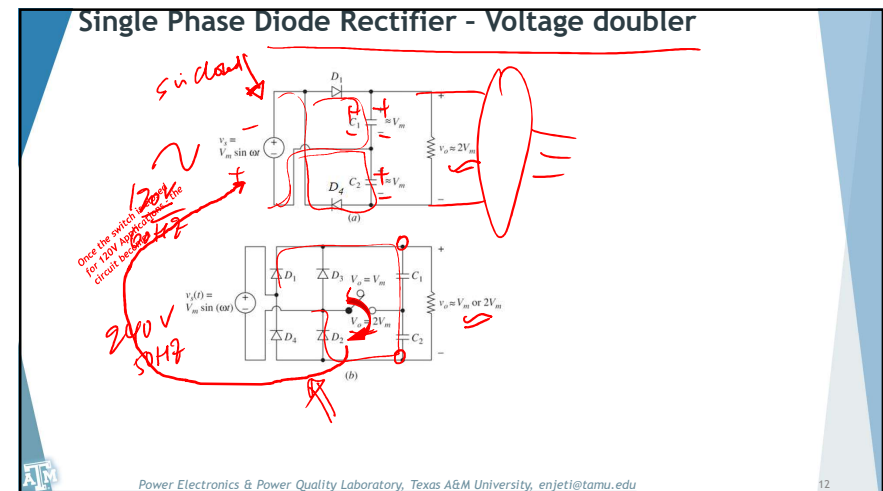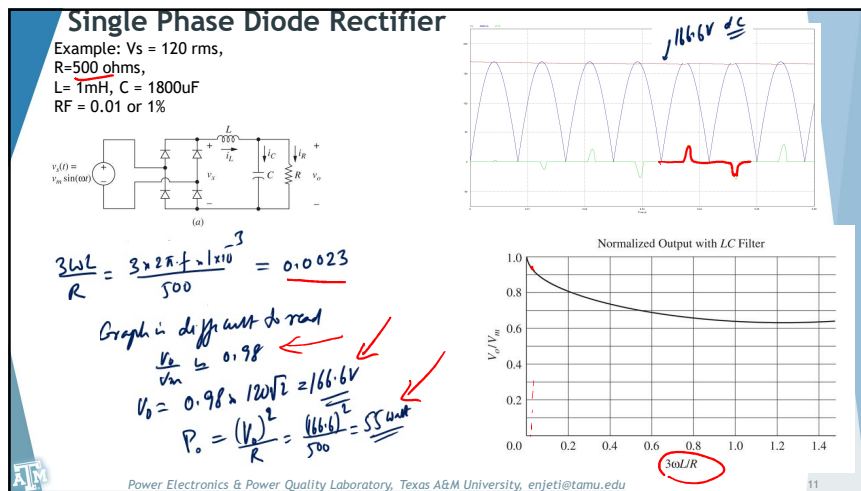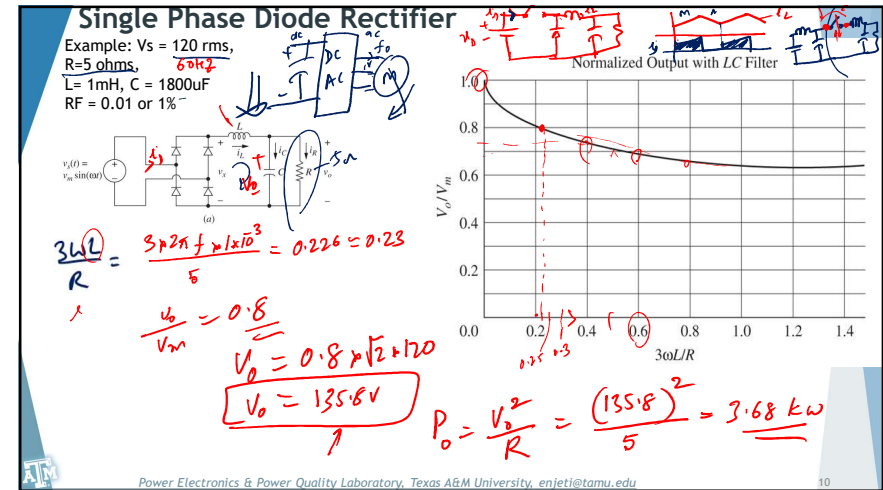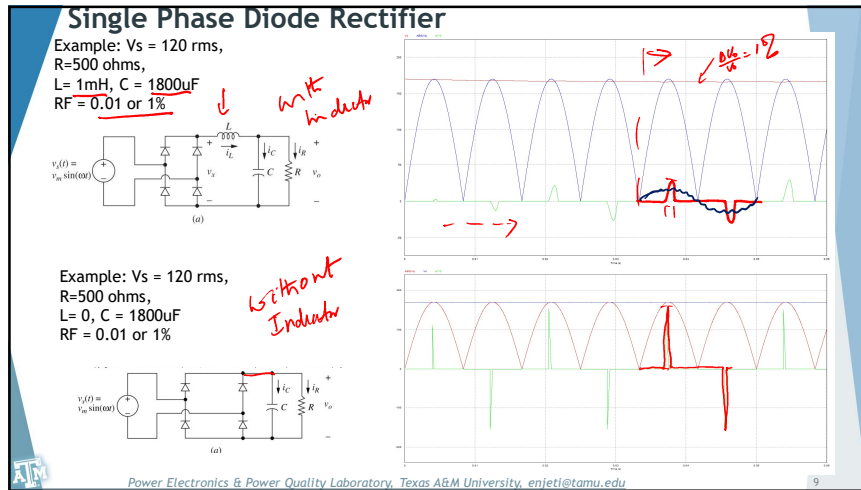



dual voltage  
(120V/220V)


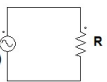
$V_s$   
120 V (rms)
 

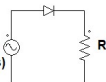$V_s$   
240 V (rms)
 

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

### Single Phase Diode Rectifier --- and - Neutral Current



- AC mains: 230V and 50Hz
- Line impedance: 0.4Ω and 800μH
- For 300W and 10% voltage ripple: C = 200μF

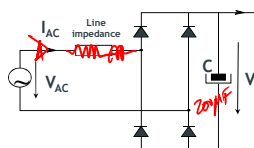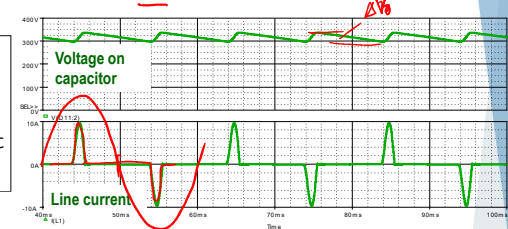➤ Current only flows during the center portion of the input sine wave

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu



### Single Phase Diode Rectifier --- and - Neutral Current

$I_{N,rms} = \sqrt{I_a^2 + I_b^2 + I_c^2}$ 
 $I_{N,rms} = \sqrt{3} * I_{ph,rms}$

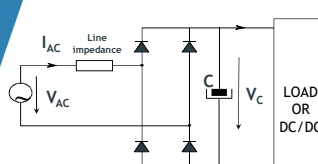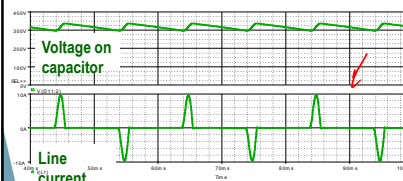Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu


### Single Phase Diode Rectifier --- and - Neutral Current

$I_N = I_a + I_b + I_c$

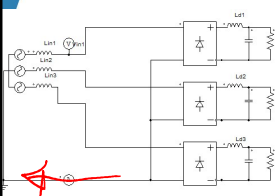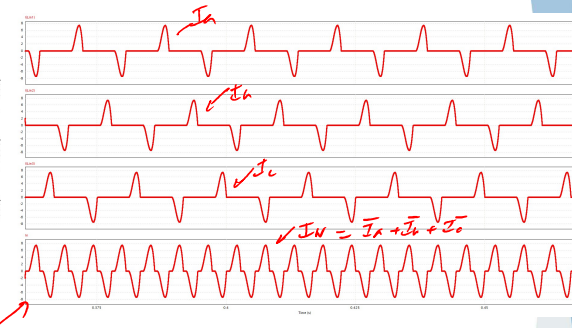Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu
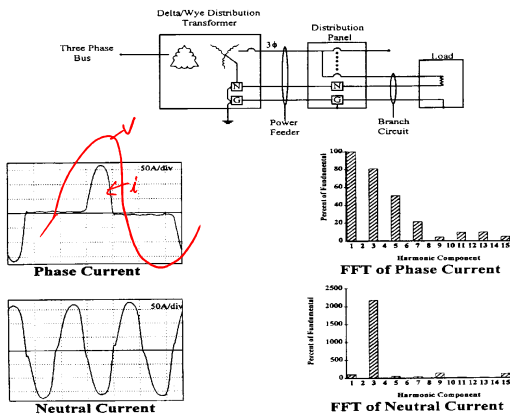
## Single Phase Diode Rectifier --- and - Neutral Current




**WITH THIRD HARMONIC**  
 APPARENT POWER = 48kVA  
 POWER FACTOR = .73  
 CREST FACTOR = 2.36  
 K RATING = 5.8

**WITHOUT THIRD HARMONIC**  
 APPARENT POWER = 40kVA  
 POWER FACTOR = .89  
 K RATING = 5.34

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

17
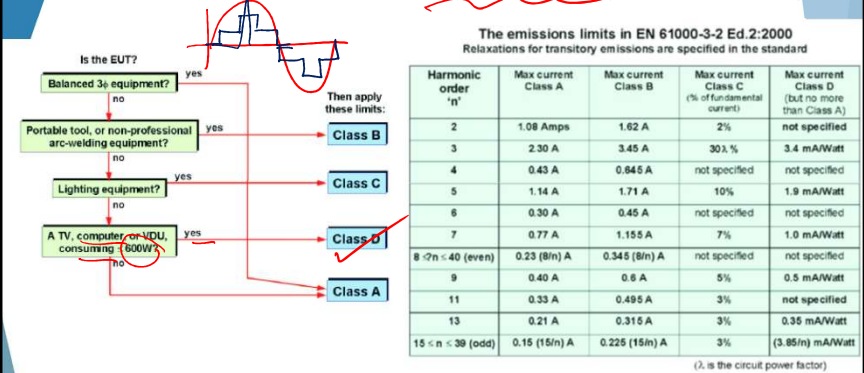
## Harmonic Current Limits - IEC 1000-3-2 (EN6 1000-3-2)



[https://www.emcstandards.co.uk/files/61000-3-2\\_mains\\_harmonics.pdf](https://www.emcstandards.co.uk/files/61000-3-2_mains_harmonics.pdf)

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

18