



Valero

For: EXAM 1 ECEN 438

Date: 02/18/2025

Subject: JOAQUIN SALAS | 731000141

By:

$$\textcircled{1} \quad V_o = 8V \text{ to } 15V \text{ in CCM}$$

$$V_{in} = 12V$$

$$f_s = 5\text{kHz}$$

$$R_L = 8\Omega$$

Find min L (uH)

\textcircled{1} Find D.

$$\frac{N_o}{N_{in}} = \frac{D}{1-D} \cdot \frac{1}{\phi}$$

$$\frac{N_o}{N_{in}} = \frac{1}{1-D} \rightarrow D \cdot \frac{N_{in}}{N_o} = 1 - D$$

$$\text{min } N_o = 8V$$

$$L_{min} = \frac{(R(1-D))^2}{2 \cdot f} \cdot \frac{1}{\phi^2}$$

$$= \frac{8(1-0.4)^2}{2 \cdot 5} \cdot \frac{1}{\phi^2}$$

$$H \cdot \phi = P_o / 2 \cdot (5k) \text{ in CCM}$$

$$\boxed{L = 288 \mu H}$$

D = 0.4 Buck Converter

CASE 2 $V_o = 15$

D = 0.556 Boost

$$L_{min} = \frac{D(1-D)^2 R}{2 \cdot f} = 87.6 \times 10^{-6}$$

$$\textcircled{2} \quad V_{in} = 43$$

$$V_{out} = 3.3$$

$$P_o = 41W$$

$$f_s = 259\text{kHz}$$

$$R_{DS(on)} = 42m\Omega$$

$$t_r = 9.1\text{ns}$$

$$t_f = 10.4\text{ns}$$

(a) Total loss = Conduction loss + Switching loss

$$P_{sw-on-loss} = \frac{1}{2} N_{in} \cdot I_o \cdot (t_{con}) \cdot f$$

\uparrow
 $t_r + t_f$

$$I = \frac{P_o}{V_o} = \frac{41}{3.3} = 12.42 = \frac{1}{2} (43)(12.42)(2 \cdot (9.1+10.4)\text{ns}) \cdot (259k)$$

$$P_{sw-on-loss} = 2.697$$

$$P_{cond} = d(R_{DS(on)}) I_o^2 = (12.42)^2 \cdot (42 \times 10^{-3})$$

$= 6.478$

$$\boxed{\text{Total Loss} = 9.175W}$$

JOAQUIN SALAS

Q3

$$V_{in} = 194V$$

$$V_o = 298V \quad \text{IN CCM}$$

$$R = 32 \Omega$$

$$\text{Ripple} < 10\% \quad \left(\frac{\Delta V_o}{V_o} \right)$$

$$t_r = 103 \text{ ns}, t_f = 51 \text{ ns}$$

Find max f, Do not exceed 5% of P_o .

① Find D, Duty Cycle

$$N_o = \frac{V_{in}}{1-D} = 0.349 = D \quad I_o = N_o / R = \frac{298}{32}$$

$$② L_{min} = \frac{D(1-D)^2 R}{2 \cdot f} \quad P_o = \frac{N_o^2}{R} = \frac{298^2}{32} =$$

$$P_o = 2775.125 \text{ W}$$

③ Switching Loss, $2775.125 (0.05)$

$$P_{sw-loss} = \frac{1}{2} V_{in} \cdot I_o \cdot (t_{L, on}) \cdot f \quad P_{loss} \neq 138 \text{ W}$$

$$138 = \frac{1}{2} (194) \cdot (9.3125) \cdot (103 + 51) \text{ ns} \quad (\times)$$

$$x = 992019.8 \quad f = 992 \text{ kHz}$$

$$\text{or } f = 496 \text{ kHz?}$$

$$L_{min} = \frac{0.349 (1-0.349)^2 (32)}{2 \cdot (992 \text{ k})}$$

Answer

$$f = 992 \text{ kHz}$$

Q4 Boost converter

$$V_{in} = 11V$$

$$V_o = 28V$$

$$P_o = 93W$$

$$f_s = 100kHz$$

$$L = 2\mu H$$

Find $I_{L,\max}$

① Find D

$$\frac{N_o}{N_{in}} = \frac{1}{1-D} \rightarrow \frac{N_o}{N_{in}} = \frac{1}{1-D} \rightarrow \frac{N_{in}}{N_o} = 1-D$$

$$D = 0.607$$

② DCM or CCM?

$$R_{crit} = \frac{2 \cdot f \cdot L}{D(1-D)^2} = 4.266, R = \frac{N_o^2}{P_o} = \frac{28^2}{93} = 8.43$$

$R > R_{crit}$ so, DCM

③ Find New D.

$$N_o = \frac{N_{in}}{2} [1 + \sqrt{1+4m}] \Rightarrow m = 3.9338$$

$$m = \left(\frac{R}{2L f_s}\right) D^2 \rightarrow 3.9338 = \left(\frac{8.43}{2L f_s}\right) D^2$$

$$\rightarrow D = 0.432 \text{ IN DCM.}$$

④ Find $I_{L,\max}$

$$\Delta I_L = \frac{N_{in} - D}{L f_s} = \frac{11(0.432)}{(2\mu H)(100k)} = 23.76A$$

$$I_L = \frac{N_o \cdot I_o}{N_{in}}$$

$$I_L = \frac{28 \cdot (3.32)}{11}$$

$$I_o = \frac{93}{28} = 3.32$$

$$I_L = 8.45$$



$$I_{L,\max} = I_L + \frac{\Delta I_L}{2} = 8.45 + 11.88 \quad \frac{\Delta I_L}{2} = 11.88$$

$$I_{L,\max} = 20.33A$$

Q5 Buck Converter

$$V_{in} = 30V$$

Find D.

$$V_o = 15V$$

$$L = 9\mu H$$

$$P_o = 10W$$

$$f_s = 300kHz$$

(1) Find duty cycle

$$N_o = D N_{in} \rightarrow D = 0.5$$

(2) Check Dcm and ccm

$$R_{crit,buck} = \frac{2L_f}{(1-D)} = 10.8\Omega$$

$$R = \frac{N_o^2}{P_o} = \frac{15^2}{10} = 22.5$$

 $R > R_{crit}$ So, Dcm(3) Find new ~~D~~ in Dcm

$$N_o = \frac{N_{in}}{2} \cdot (\sqrt{m \cdot (m+1)} - m)$$

$$\rightarrow m = 0.500$$

$$m = \left(\frac{R}{2 \cdot L \cdot f} \right) \cdot D^2 \rightarrow D = 0.346$$

ANSWER

$$D = 0.346$$

BUCK CONVERTER

$$1 - N_o = D N_{in}$$

$$2 - \Delta I_L = \frac{N_o(1-D)}{L \cdot f}, I_{c, rms} = \frac{\Delta I_L}{2\sqrt{3}}$$

$$3 - L_{min} = \frac{(1-D)R}{2f}, I_{L,RMS} = \sqrt{I_L^2 + \left(\frac{\Delta I_L}{\sqrt{3}}\right)^2}$$

$$4 - I_L = I_o = N_o / R$$

$$T = 1/f$$

$$5 - [\text{INPUT POWER}] N_{in} I_{in} = N_o I_o [\text{OUTPUT POWER}]$$

$$I_{in} = \frac{N_o}{N_{in}} \cdot I_o = D \cdot I_o = D \cdot I_L$$

$$6 - C = \frac{(1-D)}{\left(\frac{\Delta N_o}{N_o}\right) \cdot 8 \cdot L \cdot f^2}$$

$$r_L: N_o = \frac{N_{in} \cdot D}{1 + r_L / R}, \eta = \frac{1}{1 + r_L / R}$$

DCM: if $R > R_{crit,buck}$

$$R_{crit,buck} = \frac{2Ls}{(1-D)}, R = \frac{N_o^2}{P_o}$$

DCM Duty Cycle (D):

$$N_o = \frac{N_{in}}{2} \left(\sqrt{m \cdot (m+4)} - m \right)$$

$$\text{where } m = \left(\frac{R}{2Ls} \right) \cdot D^2$$

Buck | Boost Converter

$$\frac{N_o}{N_{in}} = \frac{D}{1-D} \quad 0 < D < 0.5 \rightarrow \text{Buck}$$

$$0.5 < D < 1 \rightarrow \text{Boost}$$

$$\Delta I_L, L \text{ SAME AS BOOST AND "C"} \quad L_{min} = \frac{R(1-D)^2}{2f}$$

$$\begin{cases} N_{in} \cdot I_{in} = N_o \cdot I_o \\ I_{in} = \frac{N_o}{N_{in}} I_o = \frac{D}{1-D} I_o \\ I_L = I_{in} + I_o \\ I_L = I_{in} + I_o = \frac{1}{1-D} I_o = \frac{1}{1-D} \cdot \frac{N_o}{N_{in}} I_o \end{cases}$$

$$\begin{cases} \text{DCM:} \\ V_o = D N_{in} \sqrt{\frac{R}{2Ls}} \end{cases}$$

EFFICIENCY - η

SWITCHING LOSS

$$P_{in} = P_{out} + P_{loss}$$

$$P_{in} = I_o \cdot D \frac{P_o}{P_o + P_{loss}}$$

$$\eta = \frac{P_o}{P_{in}} = \frac{P_o}{P_o + P_{loss}}, P_{loss} = P_o \left(\frac{1}{n} - 1 \right)$$

$$P_{sw-on-loss} = \frac{1}{2} N_{in} \cdot I_o \cdot (t_{c, on}) \cdot f$$

Ohm's LAW

$$P = V^2 / R, P = R \times I^2, P = V \cdot I$$

$$I = \sqrt{P/R}, I = P/V, I = V/R$$

$$N = R \cdot I, N = P/I, N = \sqrt{P/R}$$

$$R = N/I, R = N^2/P, R = P/I^2$$

$$P_{cond} = d(R_{DS(on)}) I_o^2$$

$$\text{Conduction Loss} = I_L^2 \cdot R_{DS(on)}$$

$$N = P/I, N = P/R, N = \sqrt{P/R}$$

$$R = N/I, R = N^2/P, R = P/I^2$$

BOOST CONVERTER

$$N_o = \frac{N_{in}}{1-D}$$

$$\Delta I_L = \frac{N_{in} \cdot DT}{L}; L = \frac{N_{in} \cdot DT}{\Delta I_L} = \frac{N_{in} \cdot D}{f \cdot \Delta I_L}$$

$$L_{min} = \frac{D(1-D)^2 R}{2 \cdot f}$$

$$N_{in} \cdot I_L = N_o \cdot I_o$$

$$I_{diode} = I_o = N_o / R$$

$$I_{switch} = I_L \cdot D$$

$$C = \frac{I_o \cdot DT}{\Delta N_o} = \frac{D}{R \cdot \left(\frac{\Delta N_o}{N_o}\right) f}$$

$$r_L: \frac{N_o}{N_{in}} = \frac{1}{(1-D)} \cdot \left(\frac{1}{1 + \frac{r_L}{R(1-D)^2}} \right)$$

$$\eta = \frac{1}{1 + \frac{r_L}{R(1-D)^2}}, \text{ DCM Begins at: } P_o = N_o^2 / R_{crit}$$

DCM: If $R > R_{crit, boost}$

$$R_{crit, boost} = \frac{2 \cdot f \cdot L}{D \cdot (1-D)^2}$$

DCM DUTY CYCLE

$$N_o = \frac{N_{in}}{2} [1 + \sqrt{1 + 4m}] \text{ in DCM}$$

$$m = \left(\frac{R}{2Ls} \right) \cdot D^2$$

$$\begin{aligned} P_{in} &= P_{out} + P_{loss} \\ P_{in} &= I_o \cdot D \frac{P_o}{P_o + P_{loss}} \\ \eta &= \frac{P_o}{P_{in}} = \frac{P_o}{P_o + P_{loss}}, P_{loss} = P_o \left(\frac{1}{n} - 1 \right) \\ P_{sw-on-loss} &= \frac{1}{2} N_{in} \cdot I_o \cdot (t_{c, on}) \cdot f \\ t_{c, on/off} &= t_r + t_f, i_{diode} = I_o - i_o \\ I_{DS(on)} &= \sqrt{D \cdot I_{L,rms}} \\ \text{LARGER } D & \rightarrow I_D = \sqrt{1-D} \cdot I_{L,rms} \\ \text{SMALL } D & \end{aligned}$$

$$\text{FAULTURE: } Q = \frac{2\pi f L}{r_L}$$