

214 homework 4


1. According to zybooks, a diode can be modelled with a quadratic dependence of current vs input voltage. Therefore the base-to-emitter diode in a transistor can be modelled the same way $i_b = a v_{be}^2$ (for $V_{be} > 0$), as shown in the circuit diagrams below. For the op amp model its output is $v_{o1} = A(v_p - v_n)$ where v_n and v_p are the voltages at the negative and positive terminal respectively. When plots are required choose $a=0.001$, $R_s=100 \text{ Ohm}$, $R_L=10 \text{ Ohm}$, $\beta=100$, $V_{cc}=5 \text{ V}$.

A) For the circuit diagram on the left write all the equations needed to find the output voltage v_o as a function of the source voltage v_s .

B) Plot v_o for v_s in the range 0 to 2 V.

C) For the circuit diagram on the right write all the equations needed to find the output voltage v_o as a function of the source voltage v_s .

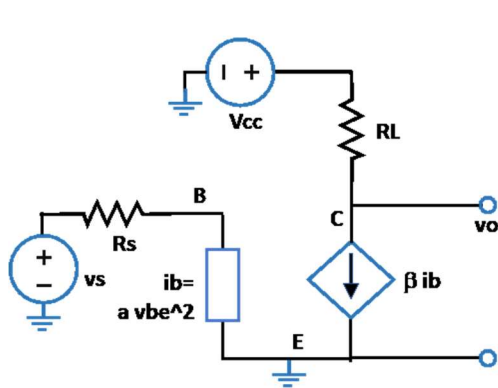D) What does the expression for the output voltage as a function of the source voltage become in the limit of large op amp gain?



$$A.) \quad I_1 = \frac{V_s - V_n}{R_s}$$

B.

$$I_2 = I_o$$

$$I_c = \beta I_b$$

$$V_o = V_{cc} - I_c \cdot R_L$$

$$C.) \quad V_1 = V_n$$

$$V_n = a \cdot v_{out}^2$$

$$V_2 = V_s$$



$$V_o = A \cdot (V_2 - V_1)$$

$$D.) \quad V_o = A \cdot (V_s - a \cdot v_{out}^2)$$

$$V_1 = V_n = a \cdot v_{out}^2$$

$$V_o = A \cdot (V_p - V_n) = A(V_2 - V_1)$$

$$= A(V_s - a v_{out}^2)$$

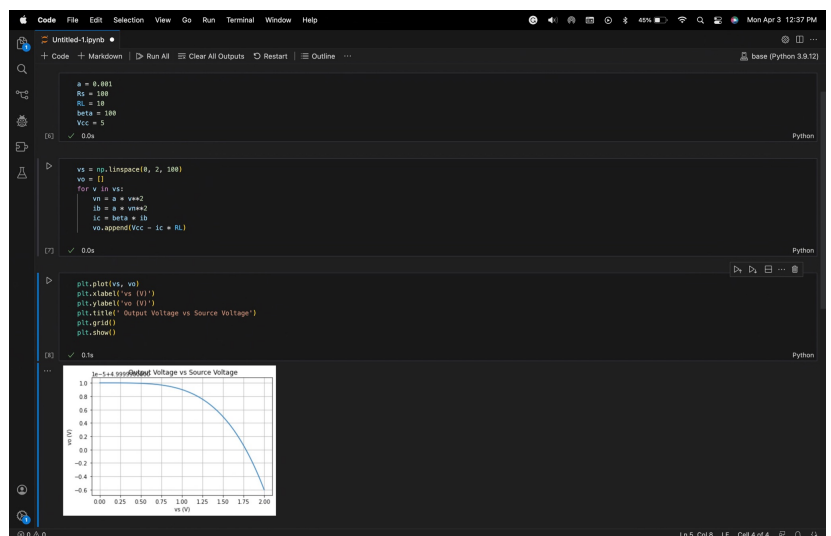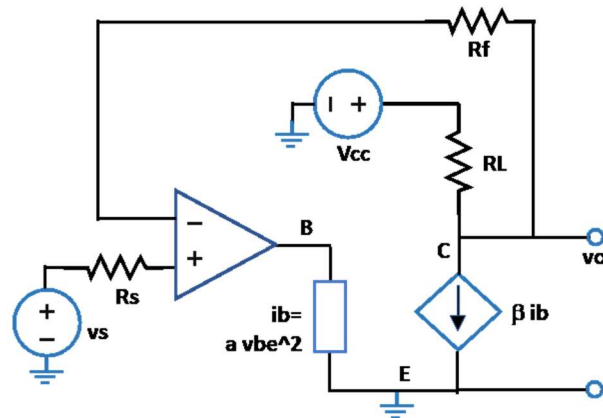


2. Consider a dual stage op amp amplifier, shown below that drives a transmitter antenna. The first amplifier is high gain and operates inside a protective enclosure. The second op amp is lower gain but can produce a higher output power and is placed outside the enclosure. As shown, feedback is applied by sampling the second op amp output and applying it to the input of the first op amp. Consider the case when a jamming signal is applied to the outside amplifier. For simplicity model this as a voltage v_j applied through a resistor R_j , as shown below. When plots are required choose $R_{i1}=100\ \Omega$, $R_{i2}=100\ \Omega$, $R_j=100\ \Omega$, $R_{f2}=1\ \text{k}\Omega$, $R_f=10\ \text{k}\Omega$, $v_s=1\ \text{V}$, $v_j=100\ \text{V}$, $V_{cc}=10\ \text{V}$.

A) Write all the equations needed to find the output voltage v_o as a function of the source voltage v_s and the jammer voltage v_j .

B) What is the equation for v_o as a function of v_s and v_j in the limit of a large gain of the first stage op amp?

C) What is the output voltage if the first stage has a gain of 1?

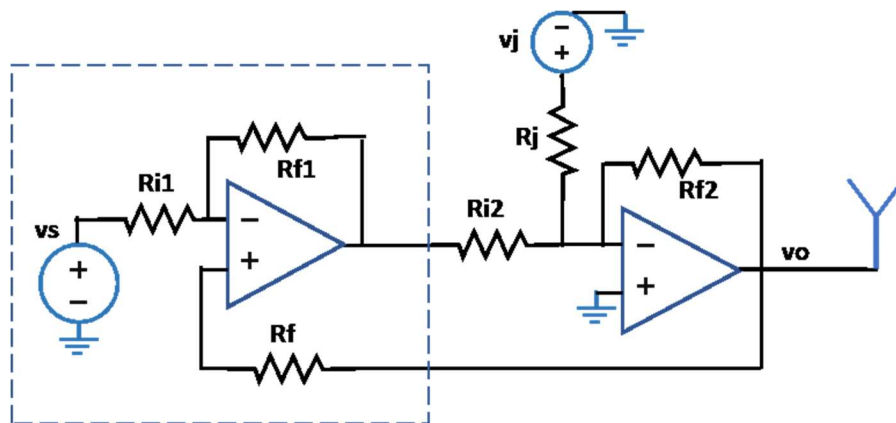D) Plot the output voltage as a function of gain of the first op amp from gain of 1 to 1000.



$$A) \quad v_o = -v_{o1} \left(\frac{R_{f2}}{R_{i2}} \right) - v_j \left(\frac{R_{f2}}{R_j} \right)$$

B) Equation -

$$v_o = \frac{A}{A^2 - 2.1A + 1.1} \left[A \cdot 10v_s - (1.1 - 0.1A)10v_j \right]$$

C) $A=1$

$$v_o = \frac{10A - (1.1 - 0.1A)10^3}{A^2 - 2.1A + 1.1}$$


3. The dual op amp circuit below has two outputs v_{o1} and v_{o2} . Note that the first op amp has positive feedback and so is saturated to $+V_{cc}$ or $-V_{cc}$. Because of this the two input voltages, v_{n1} and v_{p1} , are not necessarily equal. Begin with $V_{s1}=0=V_{s2}$.

A) Find the equations for both outputs as a function of time. Assume initial values of $v_{o1}(0)=+V_{cc}$, $v_{o2}(0)=0$ V.

B) Plot the output of both op amps for two cycles. For this choose $v_{s1}=0$ V, $v_{s2}=0$ V, $R_i=100$ Ohm, $R_1=200$ Ohm, $R=100$ Ohm, $R_f=100$ Ohm, $C=0.01$ mF, $V_{cc}=10$ V

C) What happens to the waveform as V_{s2} is increased?

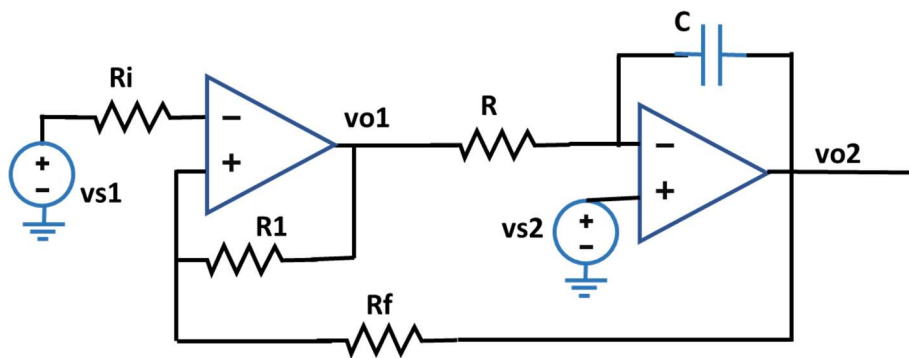D) What happens when V_{s1} is increased?



a) Made up of INTEGRATOR CIRCUIT
AND NON-INVERTING AMP.

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_s$$

$$V_{out2}(t) = \frac{1}{R_{in} C} \int_0^t V_{in} dt \quad \text{AND} \quad V_{out1}(0) = +V_{cc}$$