


Lecture # 17

ECEN 438/738 Power Electronics


Spring 2025 Semester



Dr. Prasad Enjeti,
Electrical & Computer Engineering
Texas A&M University
<http://enjeti.tamu.edu>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

ECEN 438/738 Power Electronics

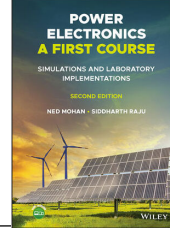

Power Electronics A First Course: 2nd Edition

Free Textbook Online Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/?ar>

Chapter 7

Magnetic Circuit Concepts

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu



Exam # 2 on 3/25/2025

- Topics covered: Lecture # 8, 9, 10, 11, 12, 13, 14 and 15 ONLY
- One sided formula sheet
- Exam # 2 will have a multiple choice questions with many parts
- Bring a calculator, Formula sheet and be prepared to scan and upload your work sheets on the Assignment Section of CANVAS
- Don't leave the exam without handing over the following: formula sheet + copy of your work

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu


Flyback DC-DC Converter – with Leakage Inductance

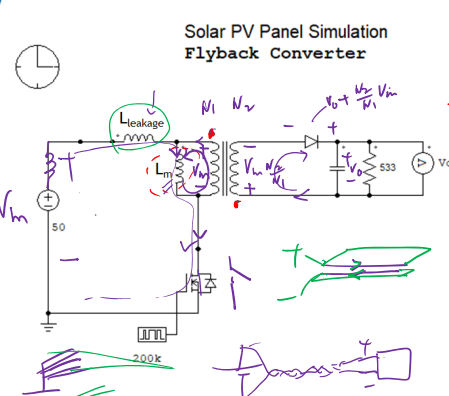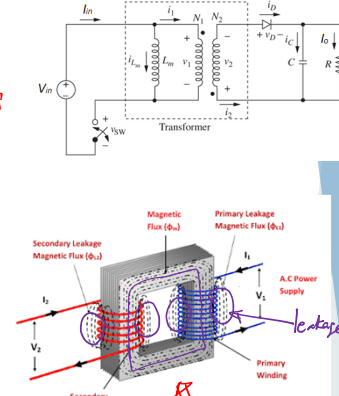Solar PV Panel Simulation
Flyback Converter





Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu


Flyback DC-DC Converter – Simulation

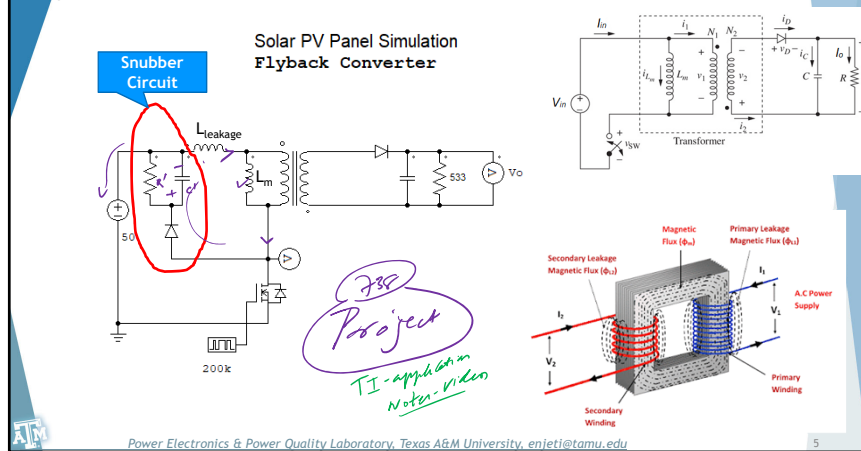


Forward DC-DC Converter - Analysis

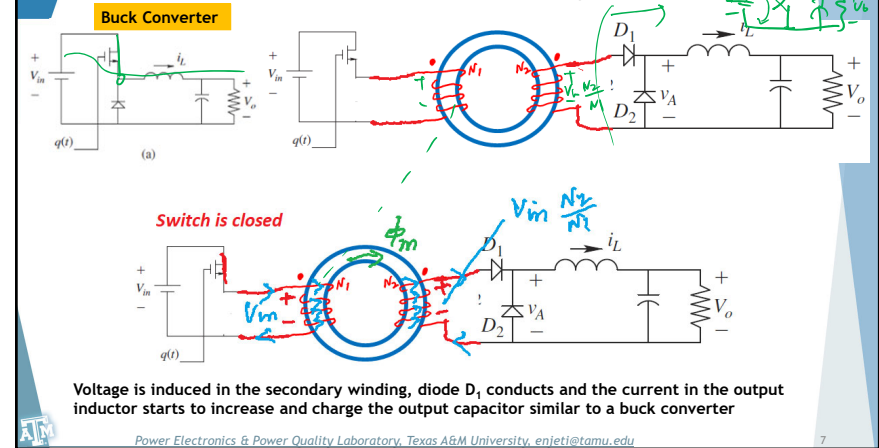


Forward DC-DC Converter - Analysis

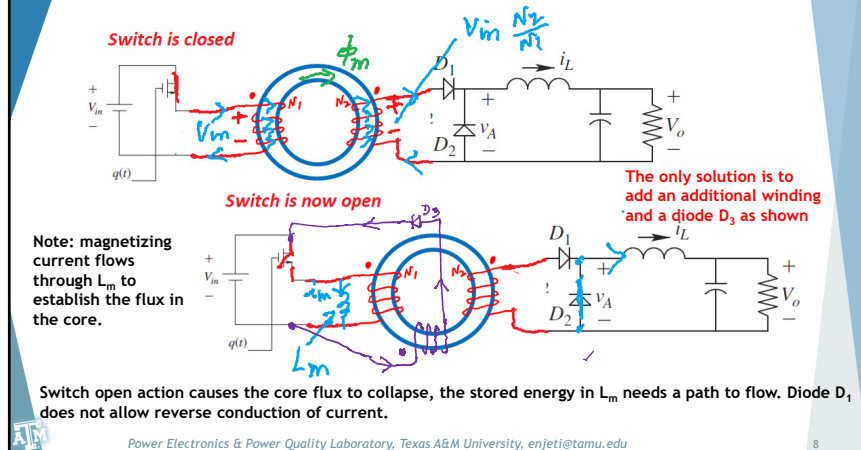

Forward DC-DC Converter - Analysis

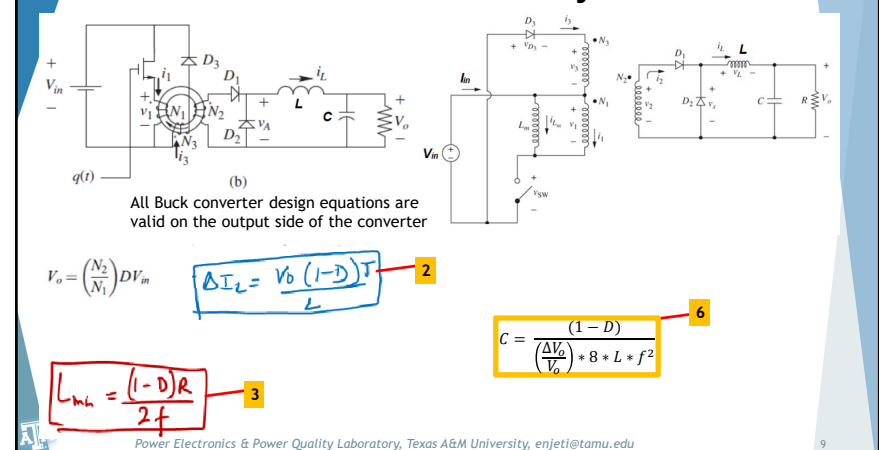

Forward DC-DC Converter - Analysis

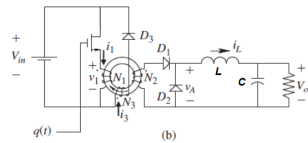

All Buck converter design equations are valid on the output side of the converter

$$V_o = \left(\frac{N_2}{N_1}\right) D V_{in}$$


$$V_L = 200V, V_o = 5V$$

$$5 = \left(\frac{N_2}{N_1}\right) D \cdot 200$$

$$\Delta I_L = \frac{V_o (1-D) T}{L}$$

$$L_{min} = \frac{(1-D) R}{2f}$$

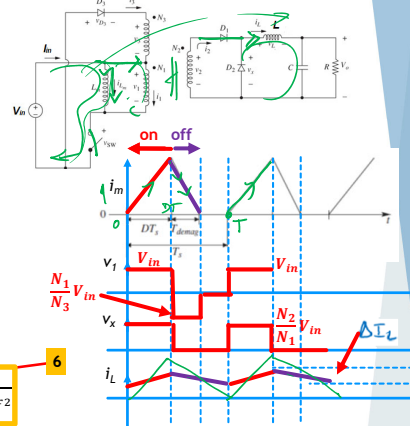
$$C = \frac{(1-D)}{\left(\frac{\Delta V_o}{V_o}\right) * 8 * L * f^2}$$



Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

10

Forward DC-DC Converter - Analysis

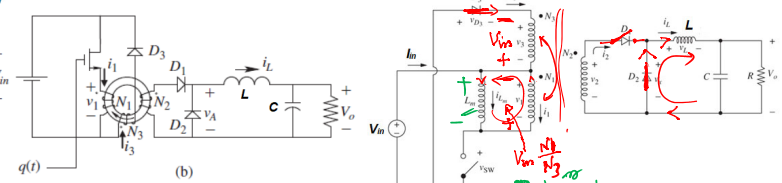

Note: when the switch is closed, core flux is established - this can be imagined as magnetizing current to flow through inductor L_m .


When the switch is open the magnetizing current in L_m finds a path via diode D_3 and winding N_3 and the stored energy in L_m is returned to input battery (source).

$$\text{Switch is on, we have } L_m \frac{\Delta i_{Lm}}{DT} = V_{in}$$

$$\text{Switch is off, we have } L_m \frac{\Delta i_{Lm}}{T_{dema}} = V_{in} \frac{N_1}{N_3}$$

Equating Δi_{Lm}
We have
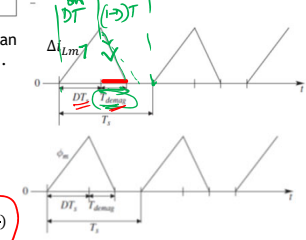
$$T_{dema} = DT \left(\frac{N_3}{N_1}\right)$$



Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

11

Forward DC-DC Converter - Analysis

$$\text{Note: } T_{dema} = DT \left(\frac{N_3}{N_1}\right)$$


$$\text{Also: } DT + T_{dema} < T$$

$$\text{i.e. } DT + DT \left(\frac{N_3}{N_1}\right) < T$$

$$\text{or } D(1 + \frac{N_3}{N_1}) < 1$$

$$\text{if } \frac{N_3}{N_1} = 1; \text{ we have } D < 0.5$$

if $D > 0.5$ - core will saturate

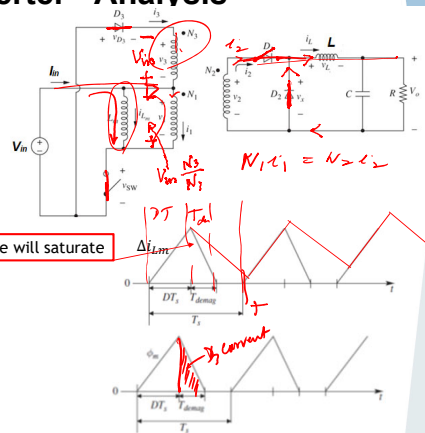

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

12

Forward DC-DC Converter - Analysis

Design a Forward converter for the following specifications:

$$V_{in} = 170V$$

$$V_o = 5V; \text{ Output power } P_o = 25W$$

$$f = 300kHz$$

The output voltage ripple must not exceed 2%, choose transformer turns ratios, duty ratio D

$$V_o = \left(\frac{N_2}{N_1}\right) D V_{in}$$

Substituting V_{in} , V_o and choosing $D < 0.5$
i.e. say $D = 0.35$, we have

$$\frac{N_1}{N_2} = 11.9; \text{ say } = 12$$

Now recalculate $D = 0.353$


$$\Delta I_L = \frac{V_o (1-D) T}{L}$$

Assume $\Delta I_L = 40\%$ of $I_o = 0.4 * 5 = 2A$

From (2) we have $L = 5.39 \mu H$

$$C = \frac{(1-D)}{\left(\frac{\Delta V_o}{V_o}\right) * 8 * L * f^2}$$

$$C = 8.3 \mu F$$

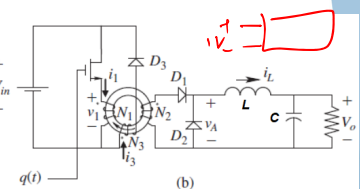

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

13

Forward DC-DC Converter - Analysis

Design a Forward converter for the following specifications:

$$V_{in} = 170V$$

$$V_o = 5V; \text{ Output power } P_o = 25W$$

$$f = 300kHz$$

The output voltage ripple must not exceed 2%, choose transformer turns ratios, duty ratio D

Find the switch and diode ratings

$$\text{Since } V_{in} * I_{in} = V_o * I_o = P_o; I_{in} = 0.147 A$$

$$\text{Also, } V_o * I_o = 25 W; I_o = 5 A$$


$$\text{For diode } D_1; I_{D1} = D * I_o = 0.353 * 5 = 1.765 A$$

$$\text{Voltage rating of diode } D_1 \text{ is } = \frac{N_2}{N_3} V_{in}; \text{ since } N_3 = N_1; \text{ we have the rating as } 14.17 V$$

$$\text{For diode } D_2; I_{D2} = (1 - D) * I_o = (1 - 0.353) * 5 = 3.235 A \quad \text{Current rating of diode } D_3 \text{ is } = \frac{1}{2} * \frac{T_{demag} * \Delta i_{Lm}}{T}$$

$$\text{Voltage rating of diode } D_3 \text{ is } = 2 * V_{in} \text{ since } N_3 = N_1$$

$$= \frac{1}{2} * D * \Delta i_{Lm}$$

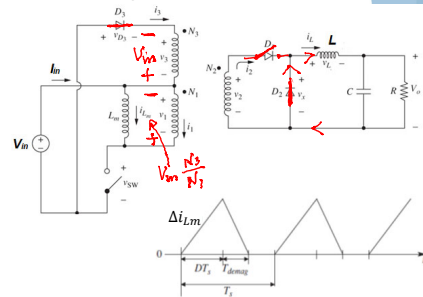

Forward DC-DC Converter - Analysis

Example 8.2

In a Forward converter shown in Figure 8.4b, $V_{in} = 48 V$, $V_o = 5 V$, $N_1/N_2 = 3.5$, $N_1/N_3 = 1$, and the magnetizing inductance $(L_m) = 150 \mu H$. This converter is operating in equivalent CCM with a switching frequency $f_s = 200 kHz$ and supplying an output load $P_o = 60 W$. Assume the filter inductor current i_L to be ripple-free. Assuming this converter to be lossless, calculate the waveforms associated with it.

$$V_o = \left(\frac{N_2}{N_1} \right) D V_{in} \quad \text{Therefore } D = 0.364$$


$$\text{Note: the output current } I_o = I_L = \frac{60}{5} = 12 A$$

$$\text{When switch is closed, input current on the primary winding } i_1 \text{ is: } i_1 = \frac{N_2}{N_1} * I_o = \frac{12}{3.5} = 3.43 A$$

$$\text{Switch is on, we have } L_m \frac{\Delta i_{Lm}}{DT} = V_{in}; \text{ and } \Delta i_{Lm} = \frac{V_{in} * DT}{L_m} = \frac{48 * 0.364}{200 kHz * 150 \mu H} = 0.5 A$$


$$\text{Switch is off, we have } L_m \frac{\Delta i_{Lm}}{T_{demag}} = V_{in} \frac{N_1}{N_3}$$
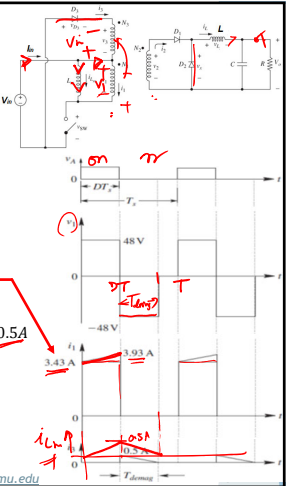
$$T_{demag} = DT \left(\frac{N_3}{N_1} \right) = 1.825 \text{ micro - sec}$$



Two Switch Forward DC-DC Converter

Conventional Forward Converter

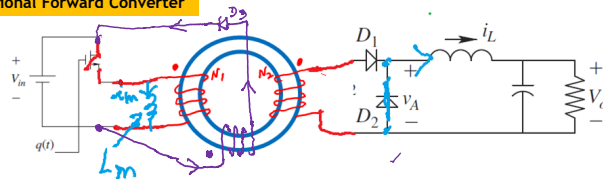

Two Switch Forward Converter

