


Lecture # 16

# ECEN 438/738 Power Electronics

Spring 2025 Semester




**Dr. Prasad Enjeti,**  
Electrical & Computer Engineering  
Texas A&M University  
<http://enjeti.tamu.edu>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

1

## ECEN 438/738 Power Electronics

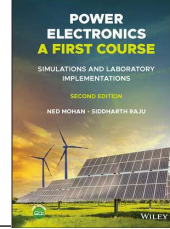

### Power Electronics A First Course: 2<sup>nd</sup> Edition

Free Textbook Online Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/7ar>

## Chapter 7


### Magnetic Circuit Concepts

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

2

### Forward DC-DC Converter - Analysis

**Buck Converter**

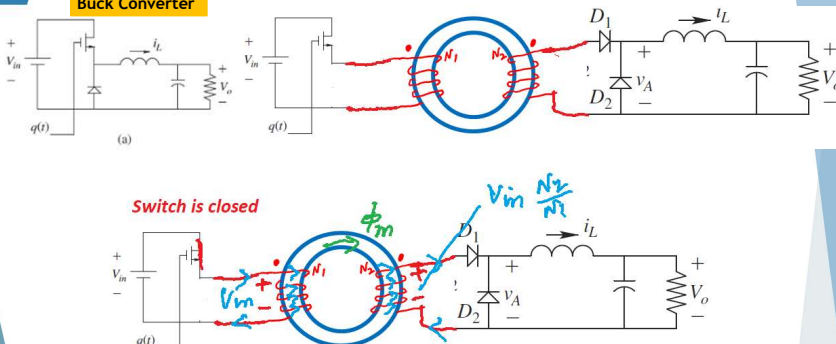


Switch is closed

Voltage is induced in the secondary winding, diode  $D_1$  conducts and the current in the output inductor starts to increase and charge the output capacitor similar to a buck converter

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

3

### Forward DC-DC Converter - Analysis

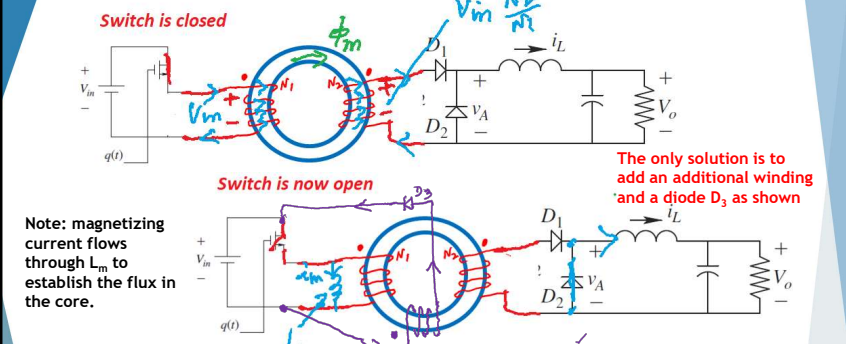

Switch is closed

Switch is now open

The only solution is to add an additional winding and a diode  $D_3$  as shown

Note: magnetizing current flows through  $L_m$  to establish the flux in the core.

Switch open action causes the core flux to collapse, the stored energy in  $L_m$  needs a path to flow. Diode  $D_1$  does not allow reverse conduction of current.

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

4

### Forward DC-DC Converter

Note: Transformer has NO airgap

### Flyback DC-DC Converter

Note: Inductor has an airgap

In Flyback, the magnetizing current is also the load current.

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

5

### Forward DC-DC Converter - Analysis

All Buck converter design equations are valid on the output side of the converter

$$V_o = \left(\frac{N_2}{N_1}\right) D V_{in}$$

$$\Delta I_L = \frac{V_o (1-D) T}{L}$$

$$L_{mh} = \frac{(1-D) R}{2f}$$

$$C = \frac{(1-D)}{\left(\frac{\Delta V_o}{V_o}\right) * 8 * L * f^2}$$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

6

### Attendance

### Spring Break

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

7

### Forward DC-DC Converter - Analysis

All Buck converter design equations are valid on the output side of the converter

$$V_o = \left(\frac{N_2}{N_1}\right) D V_{in}$$

$$\Delta I_L = \frac{V_o (1-D) T}{L}$$

$$L_{mh} = \frac{(1-D) R}{2f}$$

$$C = \frac{(1-D)}{\left(\frac{\Delta V_o}{V_o}\right) * 8 * L * f^2}$$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

8



**Thank you!!**

