

**ECEN 325 - 512**

**Operational Amplifiers - Part 1**

**Date: 9/24/2023**

**Contributors:**

**Dominic Treadwell | UIN: 720004254**

**Joaquin Salas | UIN: 731000141**


## Measurements

### Input Offset Current Measurement


Resistor #1:



Resistor #2:

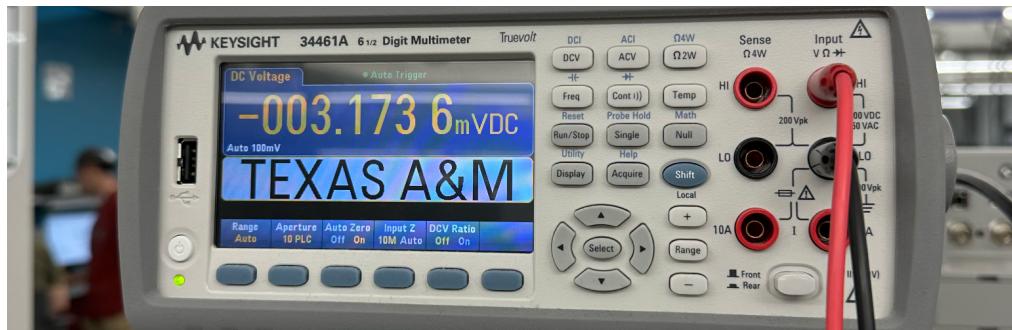

#### INPUT OFFSET CURRENT MEASUREMENT

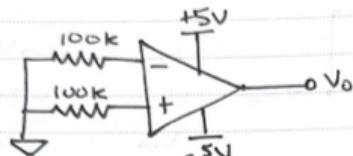

VOLTAGE THRU

$$R_1 = -3.166 \text{ mV}$$

$$R_2 = -3.2307 \text{ mV}$$


$$i_1 = \frac{-3.166 \text{ mV}}{100k\Omega} = -0.03166 \mu\text{A}$$

$$i_2 = \frac{-3.2307 \text{ mV}}{100k\Omega} = -0.032307 \mu\text{A}$$

$$I_{os} = I_B^+ - I_B^- \Rightarrow \underline{\underline{0.08 \text{ nA}}}$$

## DC Offset Current Measurement

### DC OFFSET VOLTAGE MEASUREMENT

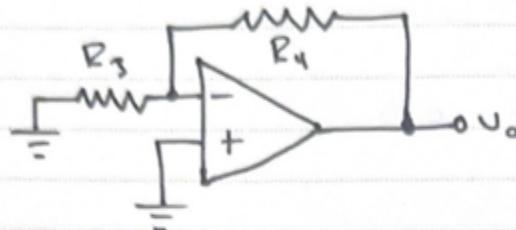

$$V_o = 5.11 \text{ mV}$$

$$\frac{V_{out}}{V_{in}} = -\frac{47 \text{ k}\Omega}{10 \text{ k}\Omega}$$

$$\rightarrow -4.7 \text{ dB}$$

①  $A_{dB} = 20 \log_{10} (A)$

$$\rightarrow A = 10^{\left(\frac{-4.7}{20}\right)} \rightarrow A = 0.316$$

$$V_{os} = \frac{5.11 \text{ mV}}{0.316} \approx \underline{16.17 \text{ mV}}$$




### ADDING POTENTIOMETER

$$V_{out} = 0.061 \text{ mV}$$

IN POTENTIOMETER:


$$R_1 = 90 \text{ k}\Omega + 91.5 \text{ k}\Omega$$

$$R_2 = 5.9 \text{ k}\Omega$$

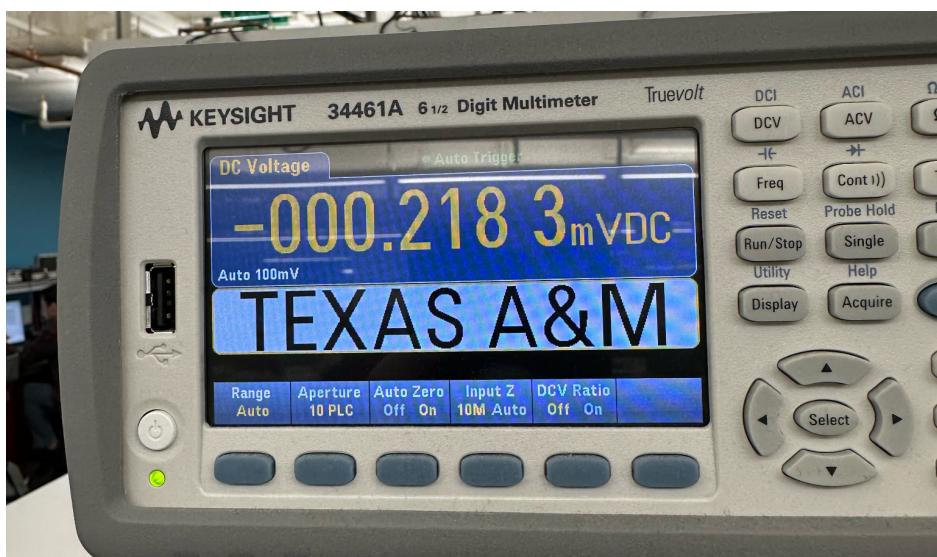


## Inverting Configuration

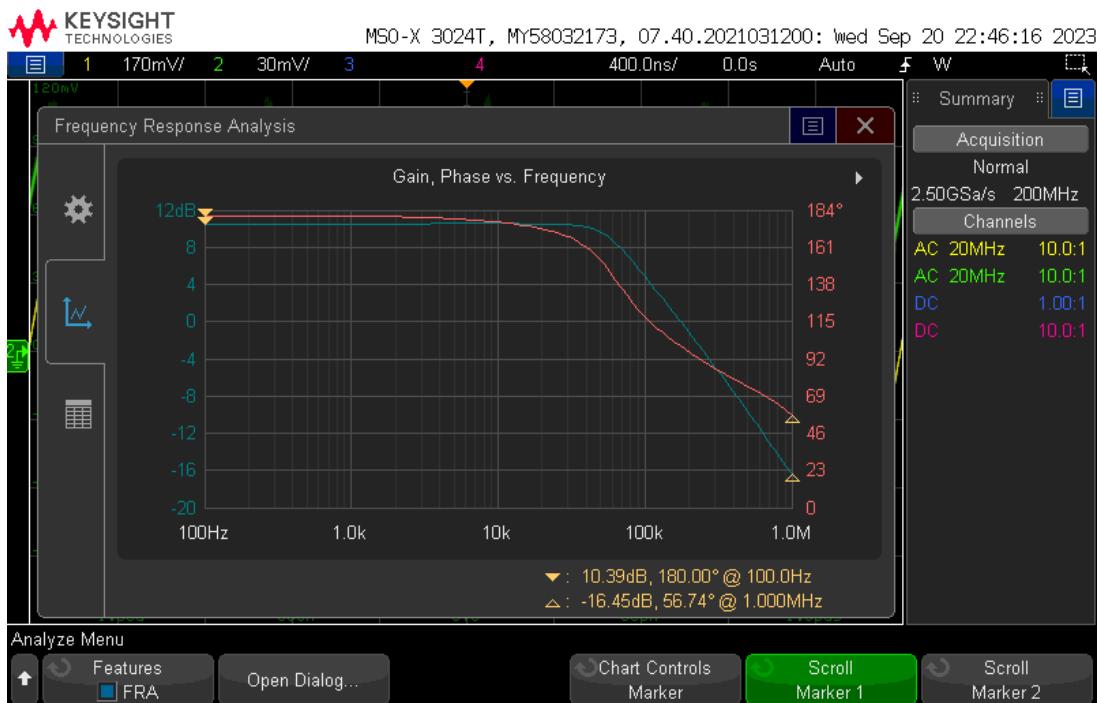
- 1) Bode plot with gain measured at 1kHz.




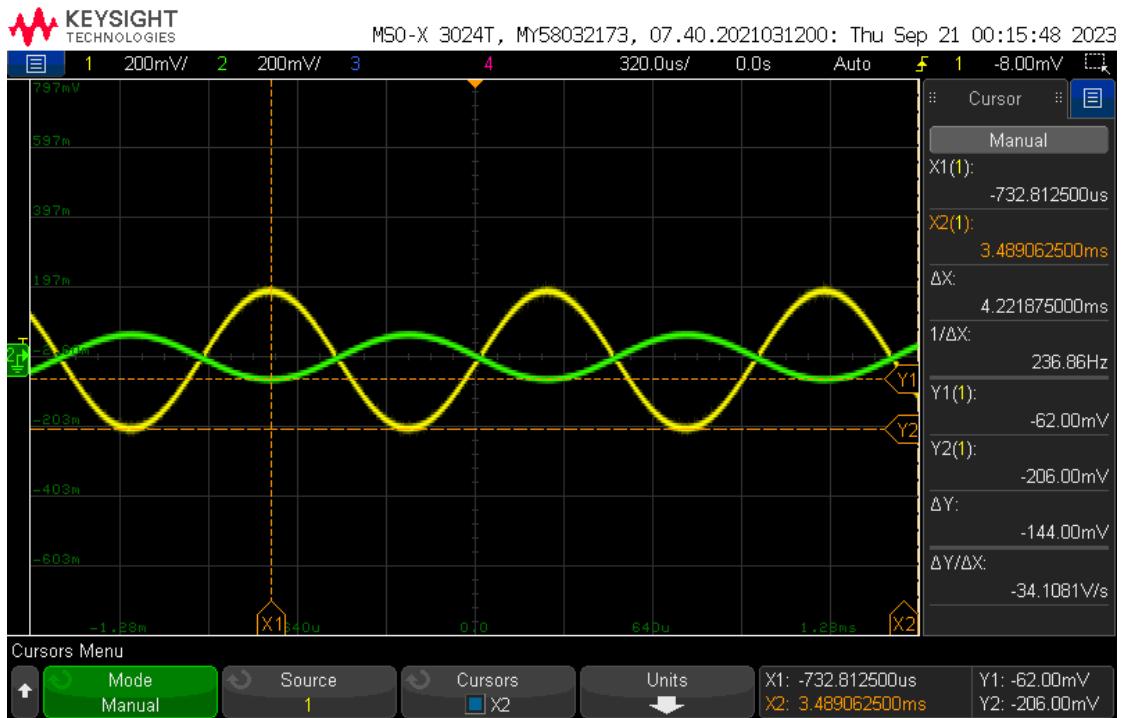- 2) Input  $V_i(t) = 0.2\sin(2\pi 1000t)$  time domain waveform




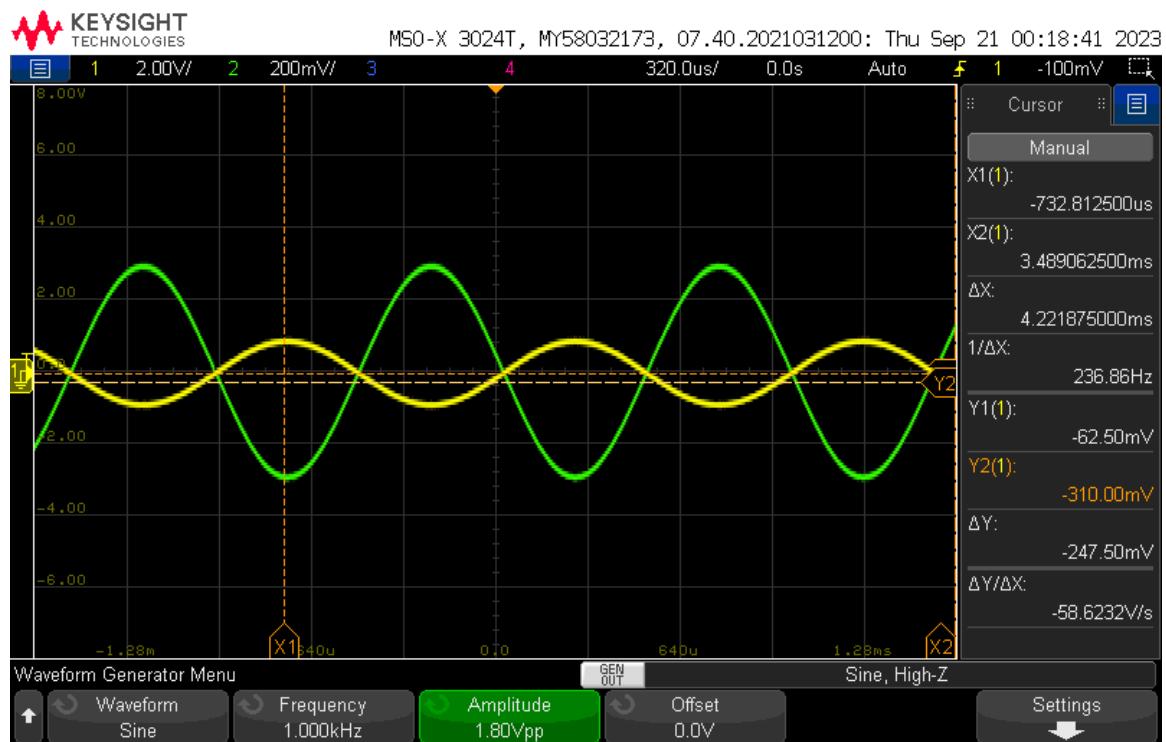3)  $V_{i,max}$  before and after clipping occurs



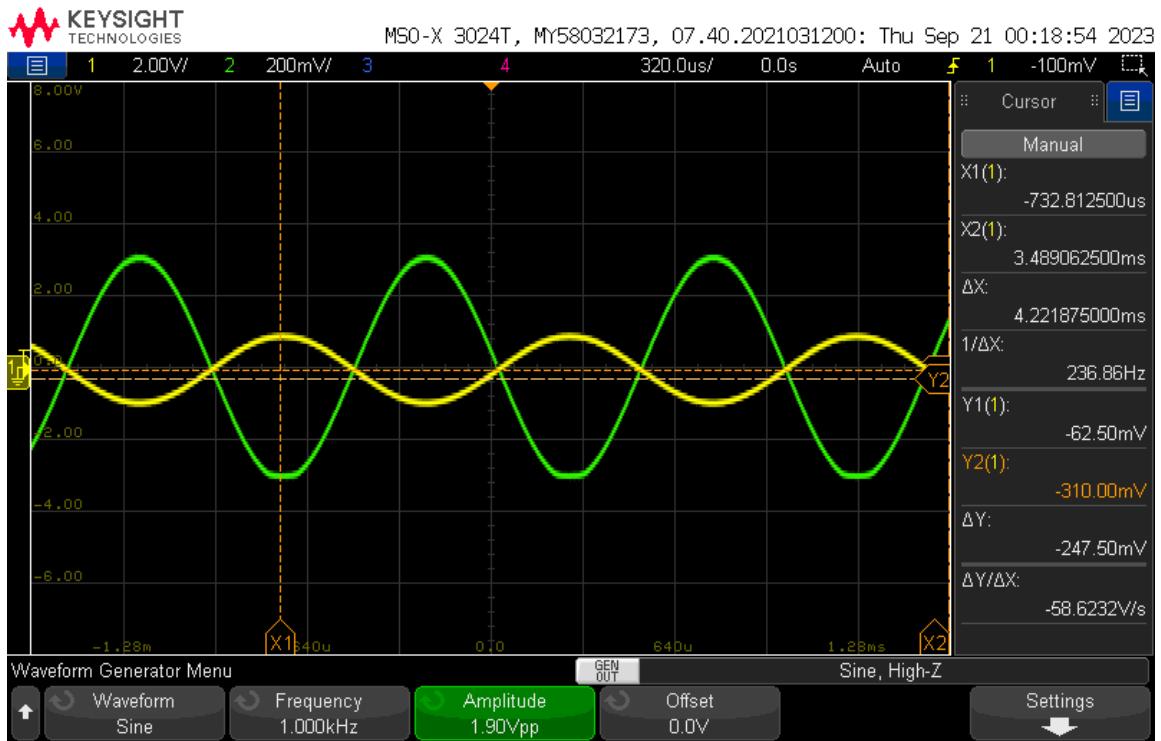


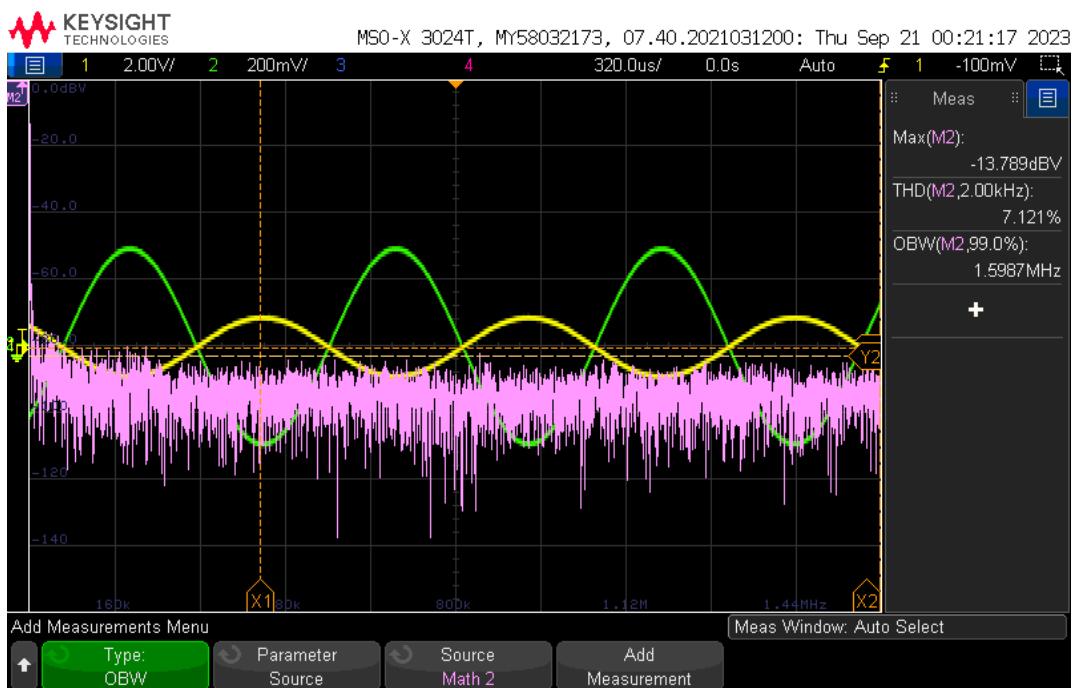4) Total Harmonic Distortion (THD) at  $V_i(t) = 1.8\sin(2\pi 1000t)$




## Non-inverting Configuration


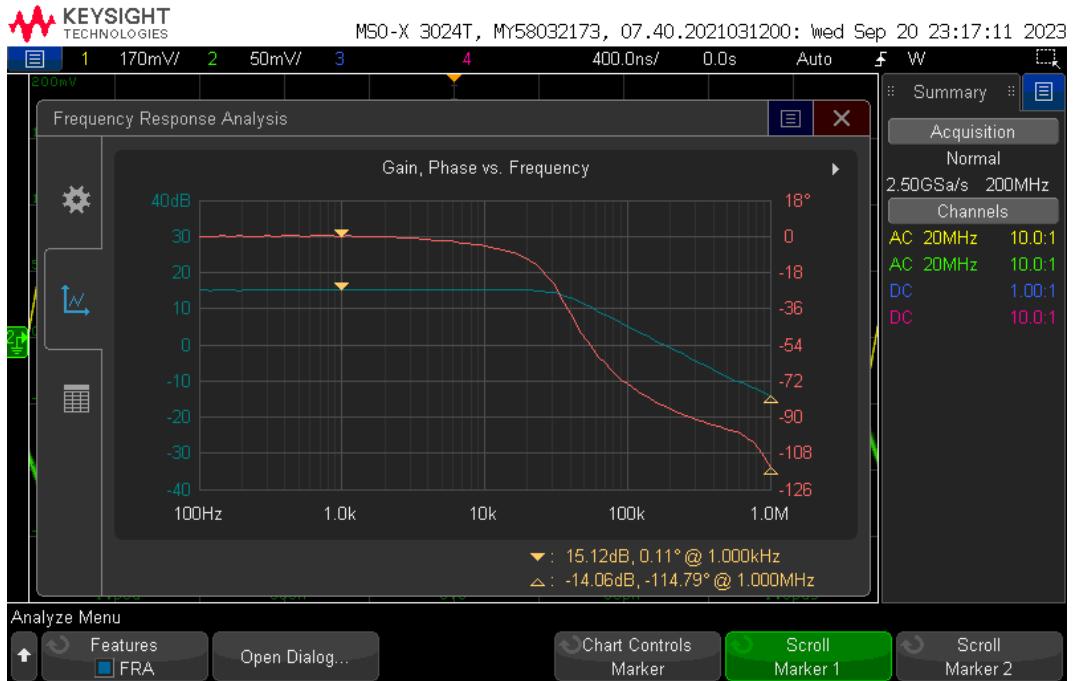
- 5) Bode plot with gain measured at 1kHz.



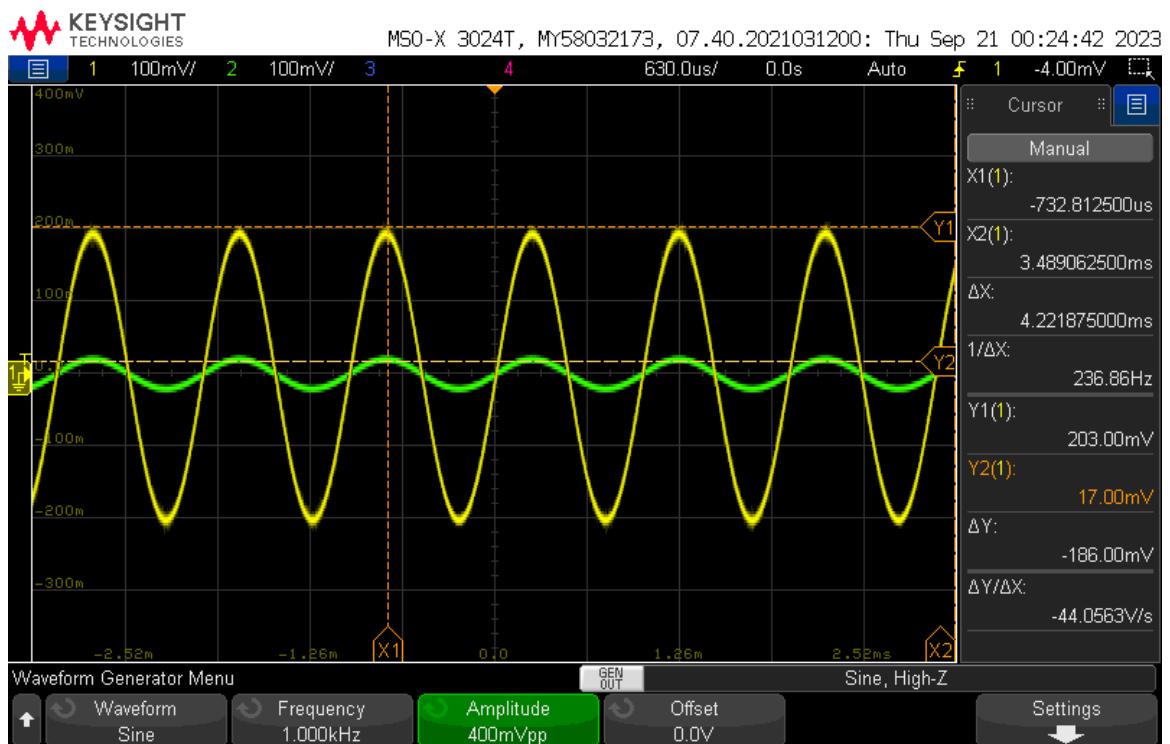- 6) Input  $V_i(t) = 0.2\sin(2\pi 1000t)$  time domain waveform



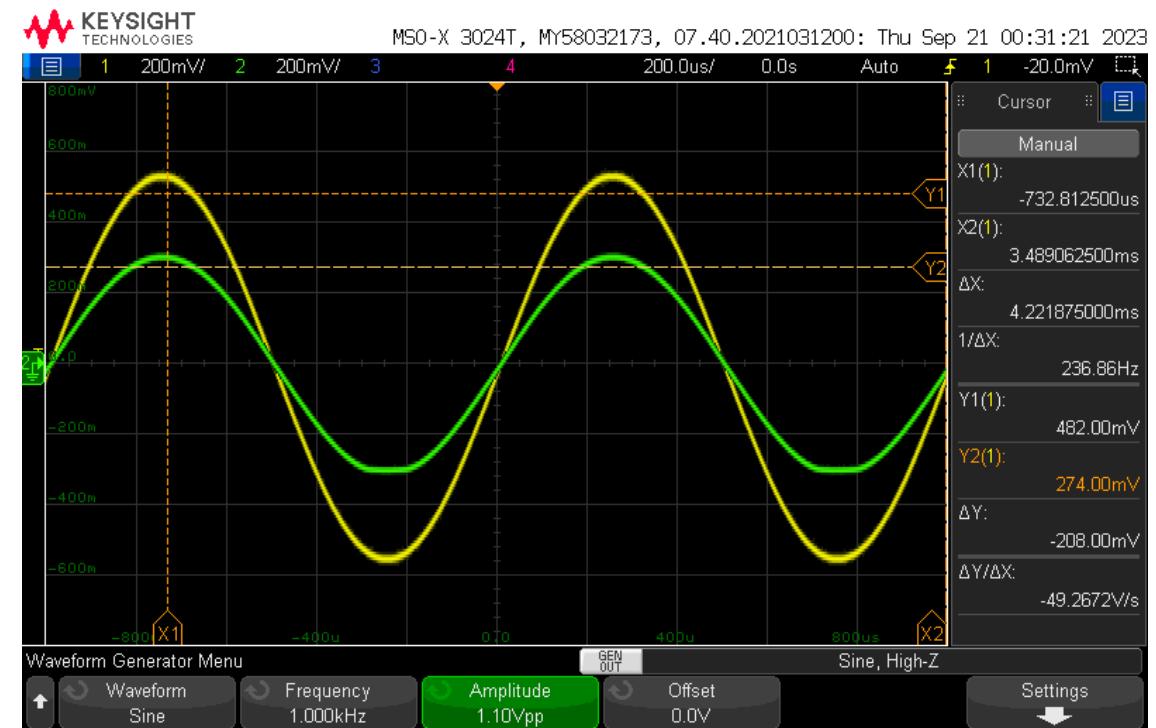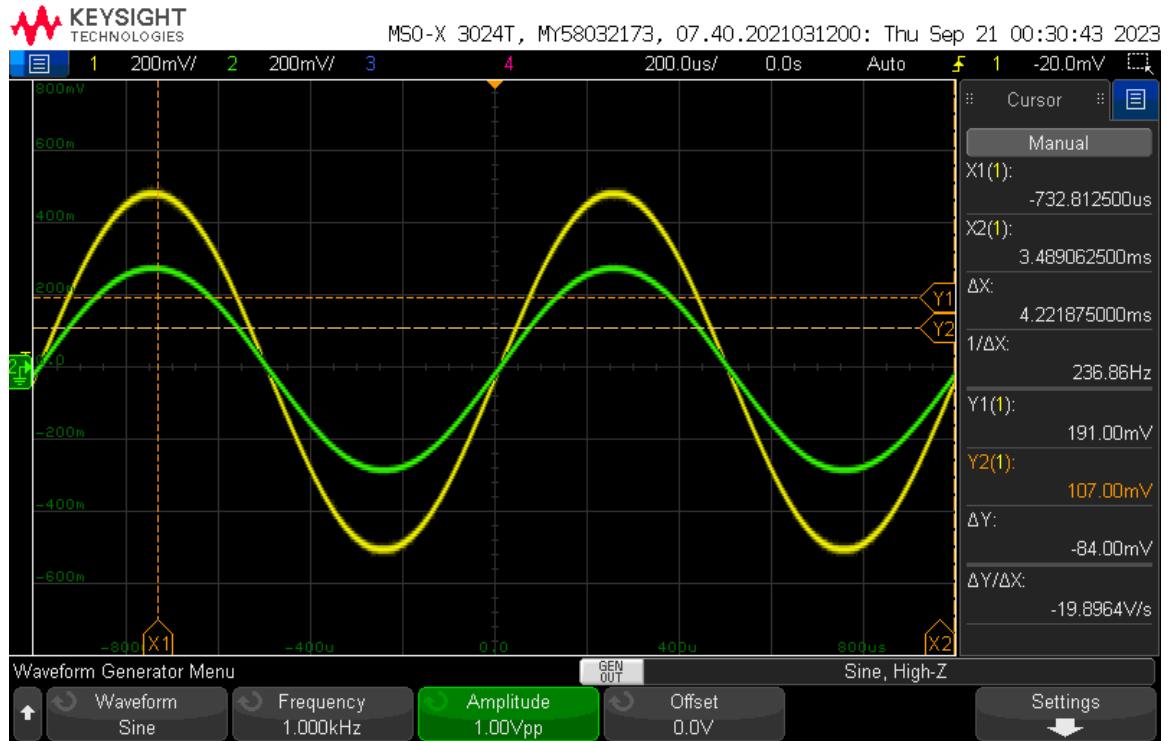7)  $V_{i,max}$  before at 1.0Vpp, after at 1.1Vpp



8) Total Harmonic Distortion (THD) at  $V_i(t) = 1.0\sin(2\pi 1000t)$



## Data Table:

The provided data table is a good way to organize and present our range of calculated, simulated, and measured values. It is divided into two distinct sections: Inverting and Non-inverting Op Amps, which correspond to different stages and aspects of the experiment or analysis. This format simplifies the detection of inconsistencies, allows for easy comparison of results across different methods or frequency domains, and ensures transparency and data integrity. By structuring data in this manner, we can efficiently manage and reference our findings, enhancing the clarity and reliability of our work.

|                               | Simulated  | Measured |
|-------------------------------|------------|----------|
| Inverting Gain @ 1 kHz        | 9.54 dB    | 10.39 dB |
| Inverting Output Voltage      | 591.99 mV  | 197 mV   |
| Inverting Input Voltage       | -200.00 mV | -62 mV   |
| Inverting Voltage Gain        | 791.99 mV  | 259 mV   |
| Inverting Max Input Amplitude | 1.80 V     | 1.80 V   |
| Inverting THD                 | 36.1%      | 7.21%    |

|                                   |           |          |
|-----------------------------------|-----------|----------|
| Non-inverting Gain @ 1 kHz        | 12.04 dB  | 15.12 dB |
| Non-inverting Output Voltage      | 1.20 V    | 203 mV   |
| Non-inverting Input Voltage       | 199.57 mV | 17 mV    |
| Non-inverting Voltage Gain        | 1.00 V    | 186 mV   |
| Non-inverting Max Input Amplitude | 1 V       | 1 V      |
| Non-inverting THD                 | 100%      | 1.55%    |
| Input Offset Current              | 2 nA      | 0.8 nA   |
| DC Offset Voltage                 | 1 mV      | 16.17 mV |

## Results:

In our recent lab experiment, an inadvertent application of a 200mV amplitude instead of the intended 400mV, compounded by the fact that the simulation software we relied on during the prelab was not working correctly, taught us important lessons: the significance of adaptability in the face of unforeseen challenges, the critical importance of precision in measurements, the non-linear nature of scientific progress where setbacks can yield valuable insights, the need for continuous improvement in procedures and communication, and the resilience required to overcome obstacles. While the experiment did not unfold as planned, these lessons will undoubtedly contribute to our growth as engineers and improve the outcomes of our future endeavors.