

PROBLEM 1

- AMPERE'S LAW RELATES MAGNETIC FIELDS TO THE CURRENTS THAT PRODUCE THEM.
- BOTH AC CURRENT AND DC CURRENT THROUGH A COIL OF WIRE CAN CAUSE A VOLTAGE TO BE INDUCED IN THE COIL. FALSE (ONLY AC)
- FOR A COUPLED MAGNETIC SYSTEM WITH TWO COILS, THE MUTUAL INDUCTANCE M CANNOT BE LARGER THAN $\sqrt{L_1 L_2}$ WHERE L_1, L_2 ARE THE SELF INDUCTANCES OF THE TWO COILS. TRUE ($0 \leq k \leq 1$)
- BOTH AC AND DC POWER CAN BE TRANSFERRED THROUGH A POWER TRANSFORMER. FALSE (ONLY AC)
- FOR THE DC MOTOR SYSTEM IN THE FIGURE BELOW, THE COIL SHOULD ROTATE ANTI-CLOCKWISE (IN THE FRONT VIEW) UNDER THE MAGNETIC FIELD. TRUE (LEFT FORCE DOWN, RIGHT FORCE UP)

PROBLEM 2

Magnetic Field Magnitude

how strong or weak a magnetic field is

Magnetic Field Intensity H (unit: A/m) or Magnetic Flux Density B (unit: T)

- Consider ideal linear magnetic material:

$$B = \mu H$$

where μ is the permeability of the material.

- Define relative permeability $\mu_r = \frac{\mu}{\mu_0} \quad \mu_0 = 4\pi \times 10^{-7} \text{ H/m}, \quad \mu_r \approx 1 \text{ for air}$

Magnetic Flux ϕ : measures the total magnetic field passing through a surface A

$$\phi = \int_S B \cdot n da \quad \phi = BA \cos \theta \quad [\text{Wb}]$$

1. In the Magnetic System shown as the figure below, the current $i=10\text{A}$ and $g=0.25\text{cm}$. Depth is 3cm . Neglect fringing. $\mu=\infty$ in iron.

a) (10 points) Draw the equivalent magnetic circuit.

b) (10 points) Find the flux ϕ in the centre leg.

c) (10 points) Find the flux density B in each air gap of the outer legs.

(a) Solution:



$$R_1 = \frac{g}{\mu A_1} = \frac{0.25 \times 10^{-2}}{4\pi \times 10^{-7} \times 12 \times 10^{-4}} = 1.65 \times 10^6 \text{ At/Wb}$$

$$R_2 = \frac{g}{\mu A_2} = \frac{0.25 \times 10^{-2}}{4\pi \times 10^{-7} \times 6 \times 10^{-4}} = 3.31 \times 10^6 \text{ At/Wb}$$

(b) Solution:

$$\phi_1 = \frac{Ni}{R_1 + R_2 + \frac{Z}{2}} = \frac{2000}{3.31 \times 10^6} = 0.602 \times 10^{-3} \text{ Wb}$$

$$(c) \text{ Outer leg: } \phi_2 = \frac{\phi_1}{2} \quad B_{out} = \frac{\phi_2}{A} = 0.5026 \text{ T}$$

13

Example 4: Magnetic Circuits

For the magnetic circuit shown in the figure, all dimensions are in cm.

The relative permeability of the core $\mu_r = 1200$.

Find the flux density B in the airgap.

Step 1 – Establish the direction of the coil mmf

Step 2 – Draw the equivalent circuit



Step 3 – Solve the magnetic circuit using the principles of electric circuits

$$l_{bafe} = 3 \times 0.52 = 1.56 \text{ m} = l_{bcde} \quad l_{be} = 0.52 - 0.005 = 0.515 \text{ m}$$

$$R_{bafe} = \frac{l_{bafe}}{\mu_r \mu_0 A} = \frac{1.56}{1200 \times 4\pi \times 10^{-7} \times 4 \times 10^{-4}} = 2.58 \times 10^6 = R_{bcde}$$

$$R_{be} = \frac{l_{be}}{\mu_r \mu_0 A} = \frac{0.515}{1200 \times 4\pi \times 10^{-7} \times 4 \times 10^{-4}} = 0.82 \times 10^6$$
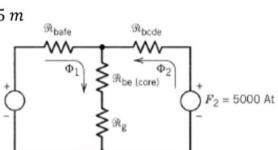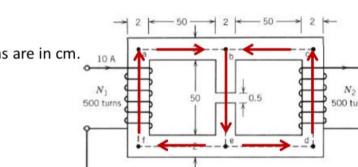
$$R_g = \frac{l_g}{\mu_0 A} = \frac{0.005}{4\pi \times 10^{-7} \times 4 \times 10^{-4}} = 9.94 \times 10^6$$



Apply magnetic version of "KVL" and "Ohm's Law"

Procedure for Solving Magnetic Circuits

• Step 1: Establish the direction of the coil mmf using right-hand rule

• Step 2: Draw equivalent magnetic circuit

• Step 3: Find reluctances

$$\cdot R = \frac{l}{\mu A}, \quad A = \omega \cdot t$$

• Step 4: Solve the magnetic circuits

$$\cdot KCL + KVL + \text{Magnetic Ohm's Law} \quad Ni = R\phi$$

• Step 5: Once flux (ϕ) is calculated, you can find B and H

$$\cdot \phi = BA \rightarrow B = \frac{\phi}{A}$$

$$\cdot B = \mu H \rightarrow H = \frac{B}{\mu}$$


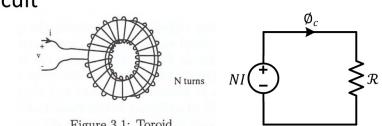


Figure 3.1: Toroid

B : magnetic flux density
 H : magnetic field intensity
 ϕ : magnetic flux

EXTRA EXAMPLE

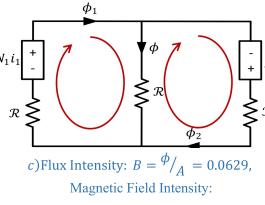

$$\text{Reluctance: } R = 2 \times \frac{l_g}{\mu_0 A} = 9.95 \times 10^6 \text{ At/Wb}$$

Loop Equations:

$$N_1 i_1 = R\phi_1 + R(\phi_1 - \phi_2) = 2R\phi_1 - R\phi_2$$

$$N_2 i_2 = R\phi_2 + R(\phi_2 - \phi_1) = -R\phi_1 + 2R\phi_2$$

$$\phi_1 = \frac{(2N_1 + N_2)i}{3R} = 1.51 \times 10^{-4} \text{ Wb}$$

$$\phi_2 = \frac{(N_1 + 2N_2)i}{3R} = 1.01 \times 10^{-4} \text{ Wb}$$

$$\phi = \phi_1 - \phi_2 = 5.03 \times 10^{-5} \text{ Wb}$$

Example 3: Magnetic Circuits

For the magnetic circuit shown in the figure: length of the airgap $g = 0.1\text{cm}$ and the cross sectional area $A = 4 \text{ cm}^2$. Assume $\mu_r = \infty$ for iron core. Find the flux density B in each airgap.

Step 1 – Establish the direction of the coil mmf (right hand rule)

Step 2 – Draw the equivalent circuit

Step 3 – Solve the magnetic circuit using the principles of electric circuits

Assume $\mu_r = \infty$ for iron core

$$R_C = \frac{l_g}{\mu_r \mu_0 A} = 0$$



$$\text{KCL: } \phi_1 + \phi_2 + \phi_3 = 0$$

$$\frac{250 - F_{ab}}{R} + \frac{50 - F_{ab}}{R} + \frac{-150 - F_{ab}}{R} = 0 \quad F_{ab} = 50$$

$$R = \frac{g}{A \mu_0} = 2 \times 10^6 \quad \phi_1 = \frac{250 - F_{ab}}{R} = 1 \times 10^{-4} \quad B_1 = \frac{\phi_1}{A} = 0.25 \text{ T}$$

$$\phi_2 = 0 \quad B_2 = 0$$

$$\phi_3 = -1 \times 10^{-4} \text{ (opposite direction)} \quad B_3 = 0.25 \text{ T}$$

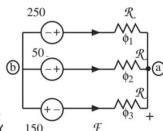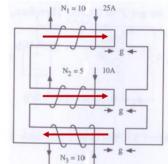


PROBLEM 3 - SELF INDUCTANCE

Self-Inductance

Time-varying current of a coil produces a time-varying flux linkage, which **induces a voltage on itself**
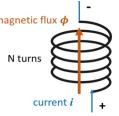
$$v_1 = \frac{d\lambda_1}{dt} = L \frac{di_1}{dt}$$




Mutual Inductance

Time-varying current of a coil produces a time-varying flux linkage, which **induces a voltage on another coil**



$$v_2 = \frac{d\lambda_{21}}{dt} = M \frac{di_1}{dt}$$

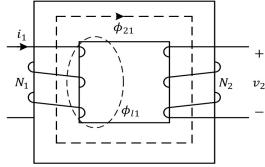- In both cases, the induced voltage equals to the changing rate of the flux linkage.
- Inductance is the linear coefficient between voltage and the changing rate of the current.
- Mutual Inductance is the basis of Transformer.



Equations with Mutually Coupled Coils

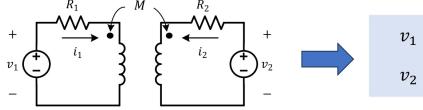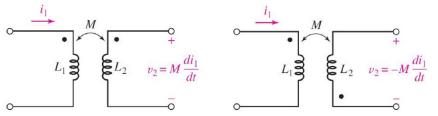- If a reference current enters a dotted terminal of a coil, the induced voltage on the other coil will be positive at the dotted terminal



$$\begin{aligned} v_1 &= i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 &= i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{aligned}$$

EXAMPLE #2

Solution. (a) Time domain

$$\begin{aligned} v_1 &= i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \Leftrightarrow 2\sqrt{2} \cos(2t) = i_1 + \frac{di_1}{dt} + \frac{di_2}{dt} \\ 0 &= i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \Leftrightarrow 0 = i_2 + \frac{di_2}{dt} + \frac{di_1}{dt} \end{aligned}$$

$$\text{Phasor: } V_1 = R_1 I_1 + jw L_1 I_1 + jw M I_2 \Leftrightarrow 2 = I_1 + jI_1 + jI_2$$

$$0 = R_2 I_2 + jw L_2 I_2 + jw M I_1 \Leftrightarrow 0 = I_2 + jI_2 + jI_1 \Leftrightarrow I_1 = j(1+j)I_2$$

$$(b) 2 = (1+j)I_1 + jI_2 = ((1+j)^2 + j)I_2$$

$$\Leftrightarrow I_2 = -0.8 - 0.4j A = 0.8944 \angle -153.4349^\circ A$$

$$I_1 = j(1+j)I_2 = 1.2 - 0.4i A = 1.2649 \angle -18.4349^\circ A$$

$$i_1(t) = \sqrt{2} \times 1.2649 \cos(t - 18.4349^\circ) = 1.7888 \cos(t - 18.4349^\circ) A$$


$$i_2(t) = \sqrt{2} \times 0.8944 \cos(t - 153.4349^\circ) = 1.2649 \cos(t - 153.4349^\circ) A$$

- Equivalent circuit with all quantities referred to **winding 1**:

- Impedances are divided by a^2
- Voltage is divided by a
- Current is multiplied by a



Opposite Operation

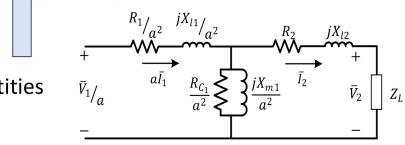

Example (Transformer)

A 10kVA, 2400/240V transformer has $R_c = 340\Omega$ and $X_m = 250\Omega$ referred to the **LV side**. And the transformer has $R_{eq} = 9\Omega$ and $X_{eq} = 15\Omega$ referred to the **HV side**. The transformer is supplying a load of 8kVA on the LV side at 0.94PF lagging at 230V.

- Draw the approximate equivalent circuit referred to the HV side (mark the components and parameters).
- Find the transformer efficiency.
- Find the voltage regulation of the transformer.

Solution: (a) 2400/240 \rightarrow step-down transformer and turn ratio $a = 2400/240 = 10$

Equivalent circuit referred to HV side (**Primary**) $R_{1eq} = a^2 R_c = 34000 \Omega$ $X_{m1} = a^2 X_m = 25000 \Omega$

$$R_{1eq} = 9\Omega, \quad X_{1eq} = 15\Omega$$

$$(b) \text{Power factor angle } \theta = \cos^{-1} 0.94 = 19.95^\circ$$

$$\bar{V}_1 = 230 \angle 0^\circ V \quad \text{Apparent power } S = 8000 VA$$

$$\text{RMS Current } I_2 = \frac{8000}{230} = 34.78A \quad I_2 = 34.78 \angle -19.95^\circ A$$

$$KVL: \bar{V}_1 = (R_{1eq} + jX_{1eq}) \frac{\bar{I}_1}{a} + a\bar{V}_2 = (9 + 15j)(3.478 \angle -19.95^\circ) + 2300 \angle 0^\circ = 2347.2 + 38.36j V = 2347.5 \angle 0.9369^\circ$$

$$P_c = \left(\frac{I_1}{a}\right)^2 R_{1eq} = 3.478^2 \times 9 = 108.9W \quad P_t = \frac{V_1^2}{R_{c1}} = \frac{2347.5^2}{34000} = 162.1W \quad \eta = \frac{P_{out}}{P_{out} + P_c + P_t} = \frac{7520}{7791} = 96.52\%$$

$$(c) \text{With load, } V_{load} = V_2 = 230V \quad \text{With no load, the secondary is open circuit, and no current namely } I_2 = 0A$$

$$V_{no\ load} = V_1/a = 234.75V$$

$$\text{Voltage Regulation} = \frac{V_{no\ load} - V_{load}}{V_{load}} = \frac{234.75 - 230}{230} = 2.07\%$$

Coupling Coefficient k


$$\bullet k \triangleq \frac{M}{\sqrt{L_1 L_2}} \text{ (the amount of coupling)}$$

$$\bullet 0 \leq k \leq 1 \text{ and } 0 \leq M \leq \sqrt{L_1 L_2}$$

1) When $k = 0$: No coupling: $M = 0$

2) When $k = 1$: Perfect coupling: ideal coupling with zero leakage. Then, $M = \sqrt{L_1 L_2}$

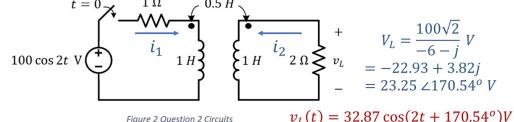2. (20 points) The circuit below shows a set of coupled coils.



$$\begin{aligned} v_1 &= \frac{d\lambda_1}{dt} = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ v_2 &= \frac{d\lambda_2}{dt} = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt} \end{aligned}$$

Figure 2 Question 2 Circuits

(a) (10 points) Write the loop equations in both time domain and phasor domain for $t \geq 0$.

(b) (10 points) Solve for $v_L(t)$ using phasors.

Solution (a) Time domain:


$$\begin{aligned} v_1 &= i_1 R_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \Rightarrow 100 \cos(2t) = i_1 + \frac{di_1}{dt} + 0.5 \frac{di_2}{dt} \\ v_2 &= i_2 R_2 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \Rightarrow 0 = i_2 + \frac{di_2}{dt} + 0.5 \frac{di_1}{dt} \end{aligned}$$

Phasor domain:


$$\begin{aligned} w &= 2 \\ V_1 &= i_1 R_1 + jw L_1 i_1 + jw M i_2 \Rightarrow 50\sqrt{2} = i_1 + j2i_1 + ji_2 = (1+j2)i_1 + ji_2 \\ V_2 &= i_2 R_2 + jw L_2 i_2 + jw M i_1 \Rightarrow 0 = 2i_2 + j2i_2 + ji_1 = (2+j2)i_2 + ji_1 \end{aligned}$$

$$\begin{aligned} \text{Solution (b)} \quad i_1 &= -\frac{(2+j2)}{j} i_2 \\ 50\sqrt{2} &= -\frac{(1+j2)(2+j2)}{j} i_2 + ji_2 \\ i_2 &= \frac{50\sqrt{2}}{-6-j} A \\ V_L &= i_2 R_2 = \frac{100\sqrt{2}}{-6-j} V \end{aligned}$$

PROBLEM 4

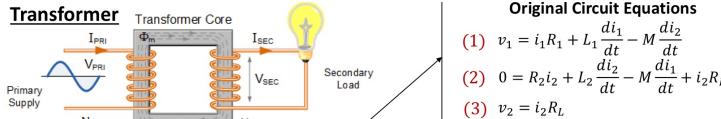

Practical Transformer

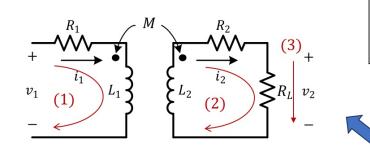

- R_1 & R_2 : winding resistances,
- L_1 , L_2 , M : self and mutual inductances
- a : N_1/N_2 ; turn ratio

Transformer Short-Circuit (SC) Test

• Performed on the High-Voltage (HV) side with Low-Voltage (LV) side short

• Measurements:

✓ (RMS) Voltage measurement V_{oc}

✓ (RMS) Current measurement I_{oc}

✓ Active Power measurement P_{oc}

• Parameters:

• V_{oc} : applied RMS voltage


• I_{oc} : short-circuit RMS current on the HV side

• P_{oc} : wattmeter reading (active power)

• Obtain R_{eq} and X_{eq} by $R_{eq} = \frac{V_{oc}}{I_{oc}}$, $Z_{eq} = \frac{V_{oc}}{I_{oc}}$

$$X_{eq} = \sqrt{V_{oc}^2 - R_{eq}^2}$$

EXTRA EXAMPLE.

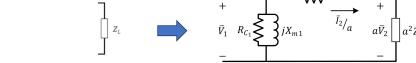

the HV side. Mark all numerical values, but

$$R_{1eq} = 0.1778\Omega, \quad X_{1eq} = 0.9162\Omega$$

$$R_{c1} = 25 \times 115.2 = 2880\Omega, \quad X_{m1} = 25 \times 15.1288 = 378.22\Omega$$

To obtain 1) magnetizing reactance X_m and 2) resistive core loss R_c

Approximate Transformer Circuit

I_R R_{c1} I_{oc} X_m Z_{eq}

I_R R_{c1} I_{oc} X_m