

ECEN 214 - Lab Report

Lab Number: 7

Lab Title: AC Response of a 1st Order RC Circuit

Section Number: 502

Student's Name: Jeweliana Mendez and Joaquin Salas

Student's UIN: 231000889 and 731000141

Lab Date: April 7, 2023

Due Date: April 14, 2023

TA: Pranabesh Bhattacharjee

Introduction:

In this lab, we were prompted to learn more about the response of a 1st order circuit to various periodic inputs. This was done by changing the theory within the lab manual by making a triangular wave into a 1st order RC low pass. We continued to do this for triangular, square and sine waveforms.

Task 1:

Task one consisted of building the circuit within figure 7.3 within the lab manual. To do this, we used a resistor with $15.1\text{ k}\Omega$ and the capacitor with 10 nF . This created once over resistor times capacitor to equal 2000π . We then created a triangle waverorm with a peak to peak of 2 volts and frequency of 250 Hz. After we record the input frequency.

Task 2:

Task two consisted of following the same procedure as task one, except creating a square waveform instead of a triangular waveform. We then ran the square waveform with the back to back 1st order filter and make the cutoff frequency to 1 kHz. After, the cutoff frequency and input frequency was recorded.

Task 3:

Task three consisted of building circuit 7.5 from the lab manual. Once this was done, R_1 and C_1 equaled 250 Hz. We also make the $10\text{ k}\Omega$ potentiometer equal to $5\text{ k}\Omega$ even. After that we made a triangular waveform and recorded its frequency and voltage division.

Measured Data & Waveforms:


Task 1:

Input = Green Output = Yellow

$R = 15.1\text{ k}\Omega$

$C = 10\text{ nF}$

Input Frequency = 850 Hz

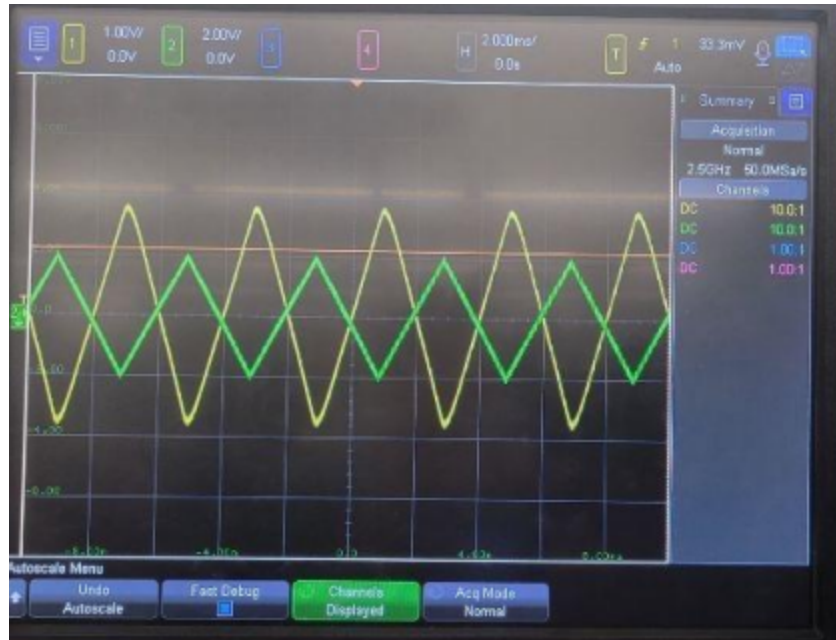

Waveform 1: Triangle Waveform



Waveform 2: Triangle to Sinusoidal


Task 2:

$$R_1 = 15.1k\Omega \quad R_2 = 5.1k\Omega$$

$$C_1 = 10nF \quad C_2 = 39nF$$

Input Frequency = 1.25 kHz

Cutoff Frequency = 1 kHz

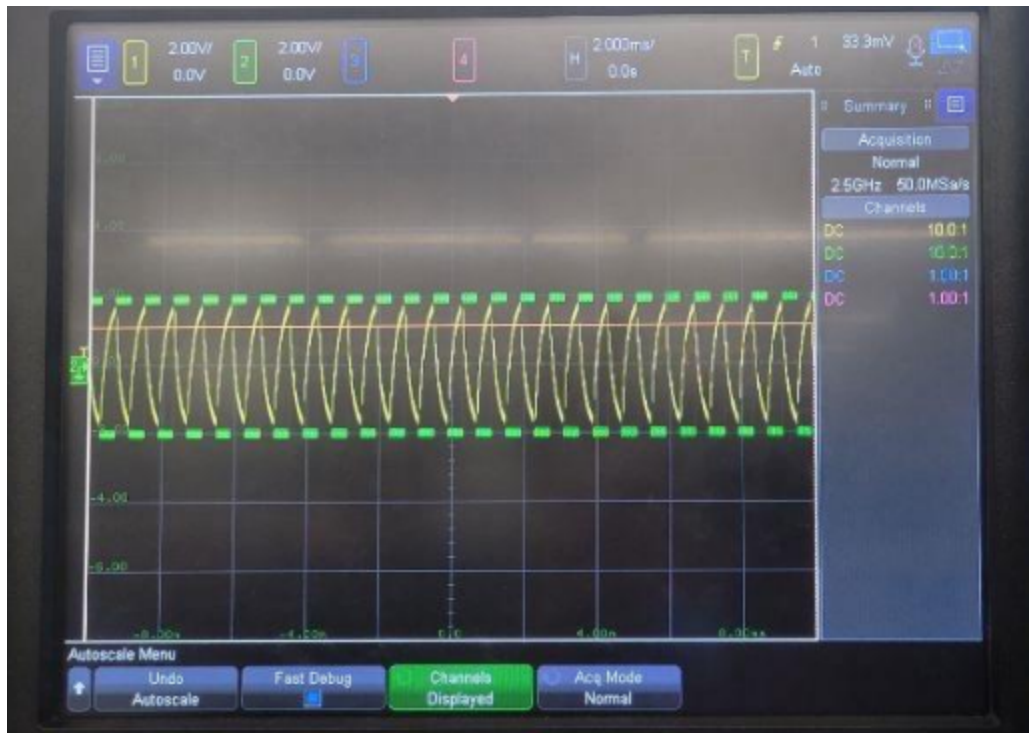

Waveform 3: Square at 1.25 kHz



Waveform 4: Square at 250 Hz



Waveform 5: Square to Sine (Cutoff)

Task 3:

$$R_1 = 200 \text{ k}\Omega \quad R_2 = 100 \text{ k}\Omega$$

$$C_1 = 10 \text{ nF} \quad C_2 = 10 \text{ nF}$$

$$\text{Frequency} = 1.5 \text{ kHz}$$

$$V_1 = 670 \text{ mV} \quad V_2 = 1.24 \text{ V} \quad V_4 = 2.34 \text{ V}$$



Waveform 6: Triangle Waveform



Waveform 7: Square Waveform



Waveform 8: Sine Waveform

Sample Calculations:

The only calculations were within the prelab when calculating output voltage and RC values.

$$V_{in}(t) = A \cos(\omega t + \theta)$$

$$V_{out}(t) = \frac{A}{\sqrt{1+(\omega RC)^2}} \cos(\omega t + \theta - \tan^{-1}(\omega RC))$$

Discussion:

Overall, the graphs were as expected, however if there were any differences, it would be due to the components. Some of the components were faulty, so we had to switch them out for new components. The lab however was still a success in matching the expected values and graphs.

