

Lecture # 4

ECEN 438/738 Power Electronics


Spring 2025 Semester



Dr. Prasad Enjeti,
Electrical & Computer Engineering
Texas A&M University
<http://enjeti.tamu.edu>

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

ECEN 438/738 Power Electronics

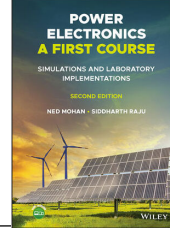

Power Electronics A First Course: 2nd Edition

Free Textbook Online Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/?ar>

Chapter 1

Power Electronics: An Enabling Technology


Copyright © 2012 by John Wiley & Sons, Inc. All rights reserved.

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

ECEN 438/738 Power Electronics

Free Textbook Access Link: <https://go.oreilly.com/TAMU/library/view/-/9781119818564/?ar>

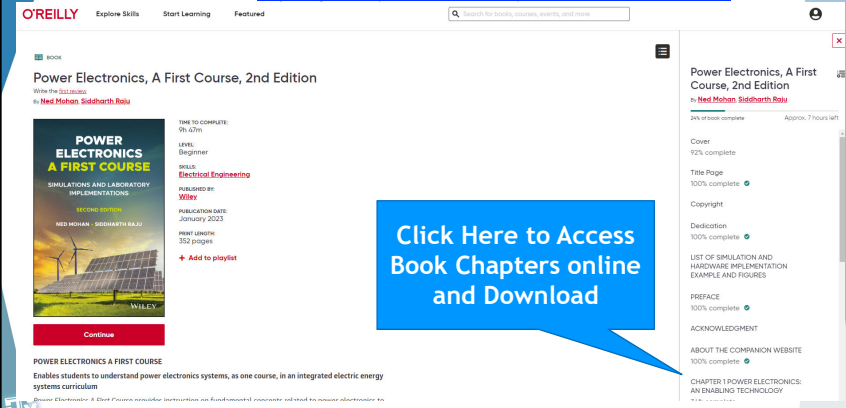Power Electronics, A First Course, 2nd Edition
By Ned Mohan, Siddharth Raju



TIME TO COMPLETE: 9h 47m
LEVEL: Beginner
COURSE: Electrical Engineering
PUBLISHED BY: Wiley
PUBLICATION DATE: January 2023
PAPER LIBRARY: 352 pages
[Add to playlist](#)

[Continue](#)

POWER ELECTRONICS A FIRST COURSE
Enables students to understand power electronics systems, as one course, in an integrated electric energy systems curriculum

Power Electronics, A First Course, 2nd Edition
By Ned Mohan, Siddharth Raju


94% stress complete Approx. 7 hours left

Cover: 92% complete
Title Page: 100% complete
Copyright: 100% complete
Dedication: 100% complete
LIST OF SIMULATION AND HARDWARE IMPLEMENTATION EXAMPLES AND FIGURES: 100% complete
PREFACE: 100% complete
ACKNOWLEDGMENT: 100% complete
ABOUT THE COMPANION WEBSITE: 100% complete
CHAPTER 1 POWER ELECTRONICS: AN ENABLING TECHNOLOGY: 100% complete

Click Here to Access
Book Chapters online
and Download

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

A simple dc-dc converter example

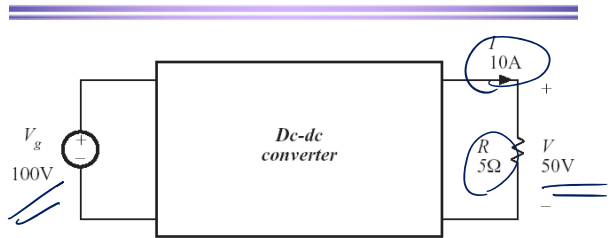


Input source: 100V
Output load: 50V, 10A, 500W
How can this converter be realized?

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

Linear Regulator

Dissipative realization

Resistive voltage divider

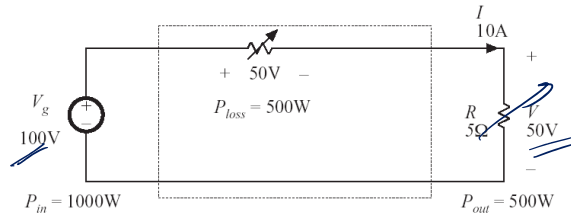


$$\text{Efficiency} = P_{\text{out}} / (P_{\text{out}} + P_{\text{loss}}) = 500 / 1000 = 50\%$$

Quiz # If the required output voltage is 10V and the current is $I = 10\text{A}$, calculate the efficiency.

Linear Regulator


Dissipative realization

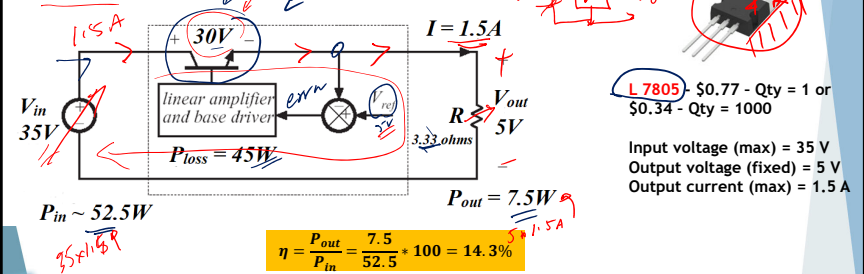Series pass regulator: transistor operates in active region








Devices available to the circuit designer

Power Electronics

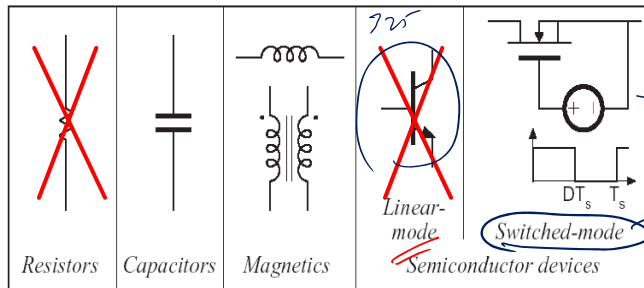

DC - DC Buck Converter

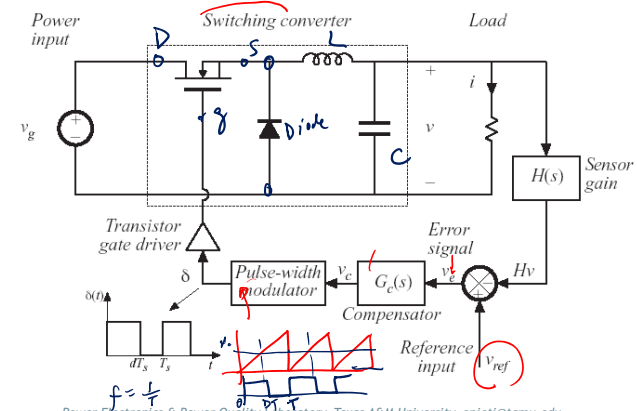

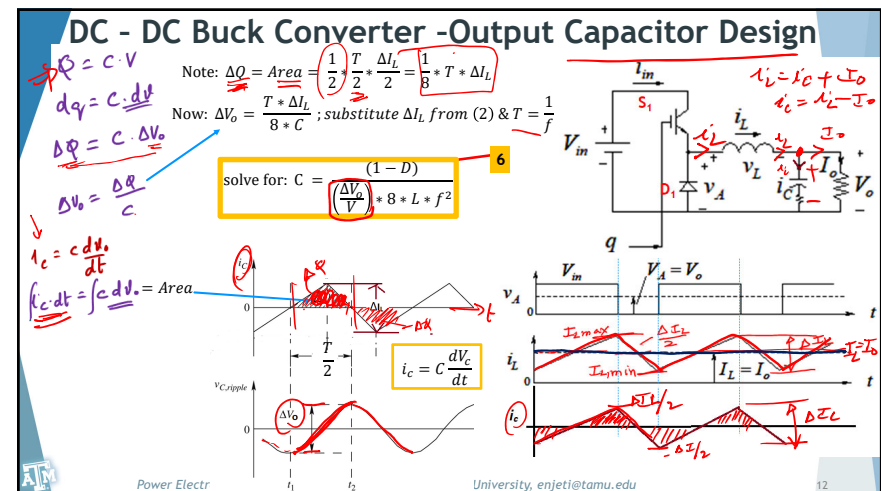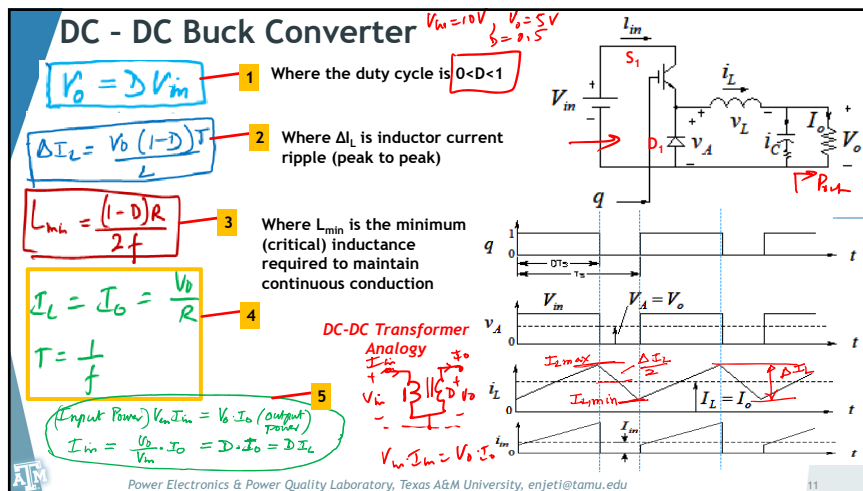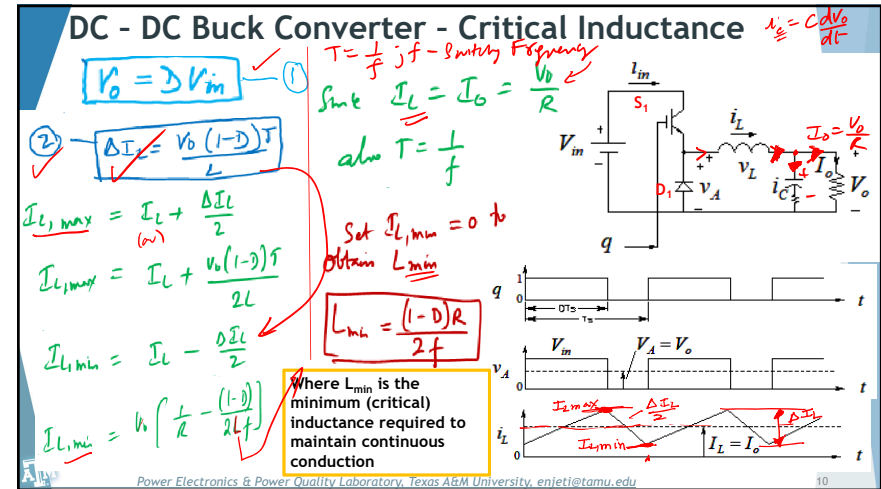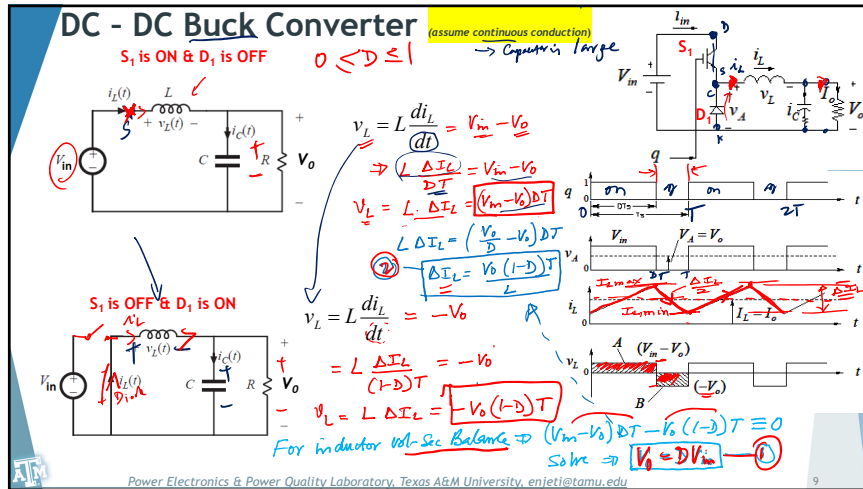

DC - DC Buck Converter

1 Where the duty cycle is $0 < D < 1$

2 Where ΔI_L is inductor current ripple (peak to peak)

3 Where L_{min} is the minimum (critical) inductance required to maintain continuous conduction

4

5

6

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

DC - DC Buck Converter - Design Example # 1

Input voltage $V_{in} = 3.3V$
 Output voltage $V_o = 1.2V$; voltage ripple not to exceed 2%
 Output current $I_o =$ Varies between 4A to 6A
 Switching Frequency $f = 500kHz$

a) Specify the inductor value such that the peak-to-peak variation in inductor current ΔI_L does not exceed 40% of the average value (I_L).
 b) Find the capacitor value C that meets the specification.
 c) Also determine the required rms current rating of the inductor and the capacitor.

$V_o = D V_s \Rightarrow D = \frac{1.2}{3.3} = 0.364$

$\Delta I_L = \frac{V_o (1-D) T}{L}$

$L = \frac{V_o (1-D)}{\Delta I_L f}$

Case # 1; $I_o = 4A = I_L$

$\Delta I_L = (40\%) \times 4A = 0.4 \times 4 = 1.6A$

$L = \frac{1.2 \times (1 - 0.364)}{1.6 \times 500,000} = 0.954 \mu H$

Case # 2; $I_o = 6A$

$\Delta I_L = (40\%) \times 6A = 2.4A$

$L = \frac{1.2 \times (1 - 0.364)}{2.4 \times 500,000} = 0.636 \mu H$

Therefore choose the largest inductor to meet the specifications i.e. $L = 0.954 \mu H$
 Lets round this off to $L = 1 \mu H$ for practical purposes

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

DC - DC Buck Converter - Design Example # 1

Input voltage $V_{in} = 3.3V$
 Output voltage $V_o = 1.2V$; voltage ripple not to exceed 2%
 Output current $I_o =$ Varies between 4A to 6A
 Switching Frequency $f = 500kHz$

a) Specify the inductor value such that the peak-to-peak variation in inductor current ΔI_L does not exceed 40% of the average value (I_L).
 b) Find the capacitor value C that meets the specification.
 c) Also determine the required rms current rating of the inductor and the capacitor.

$C = \frac{(1-D)}{(\frac{\Delta V_o}{V_o}) \times 8 \times L \times f^2}$

$C = \frac{(1-0.364)}{(0.02) \times 8 \times 1 \mu H \times (500,000)^2} = 16 \mu F$

rms current of the inductor current I_L

$I_{L,rms} = \frac{\Delta I_L}{2} \frac{1}{\sqrt{3}} = 0.44 A$

$I_{L,rms} = \sqrt{I_L^2 + \left(\frac{\Delta I_L}{2\sqrt{3}}\right)^2}$

From equation (2) find $\Delta I_L = 1.53A$; Substitute and obtain $I_{L,rms} = 6.02 A$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

RMS of different waveforms - basics

$I_{rms} = \frac{I}{\sqrt{2}}$

$I_{rms} = \sqrt{D} \cdot I$

$I_{rms} = \sqrt{I^2 + \left(\frac{\Delta I}{2\sqrt{3}}\right)^2}$

$I_{rms} = \sqrt{I^2 + \left(\frac{\Delta I}{2\sqrt{3}}\right)^2}$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu

DC - DC Buck Converter - Design Example # 2

Input voltage V_{in} = 7.5V to 36V
 Output voltage V_o = 3.3V : voltage ripple not to exceed 2%
 Output current I_o = 0.5A
 Switching Frequency f = 300kHz

a) Specify the inductor value such that continuous conduction is achieved from 25% load to 100% load
 b) Find the capacitor value C that meets the specification.
 c) Also determine the required rms current ratings of the MOSFET and the Diode

Solution: # 1 Input voltage = 7.5V

$D = \frac{3.3}{7.5} = 0.44$ 25% load, $I_o = 0.125A$
 Load resistance $R_{25\%} = \frac{3.3}{0.125} = 26.5 \text{ ohms}$
 $L_{min-@25\%-load} = \frac{(1 - 0.44) * 26.5}{2 * 300,000} = 24.6 \text{ micro-H}$

Input voltage = 36V
 $D = \frac{3.3}{36} = 0.0917$
 $L_{min-@25\%-load} = \frac{(1 - 0.0917) * 26.5}{2 * 300,000} = 40 \text{ micro-H}$

Pick the largest $L = 40 \text{ micro-H}$
 $R = \frac{3.3}{0.5} = 6.6\Omega$
 $L_{min} =$

$C = \frac{(1 - D)}{\left(\frac{\Delta V_o}{V_o}\right) * 8 * L * f^2}$
 Use the smallest D to get the larger C to meet the spec.
 $C = \frac{(1 - 0.0917)}{(0.02) * 8 * 40 * 10^{-6} * (300,000)^2} = 1.58 \text{ micro-f}$

Power Electronics & Power Quality Laboratory, Texas A&M University, enjeti@tamu.edu